
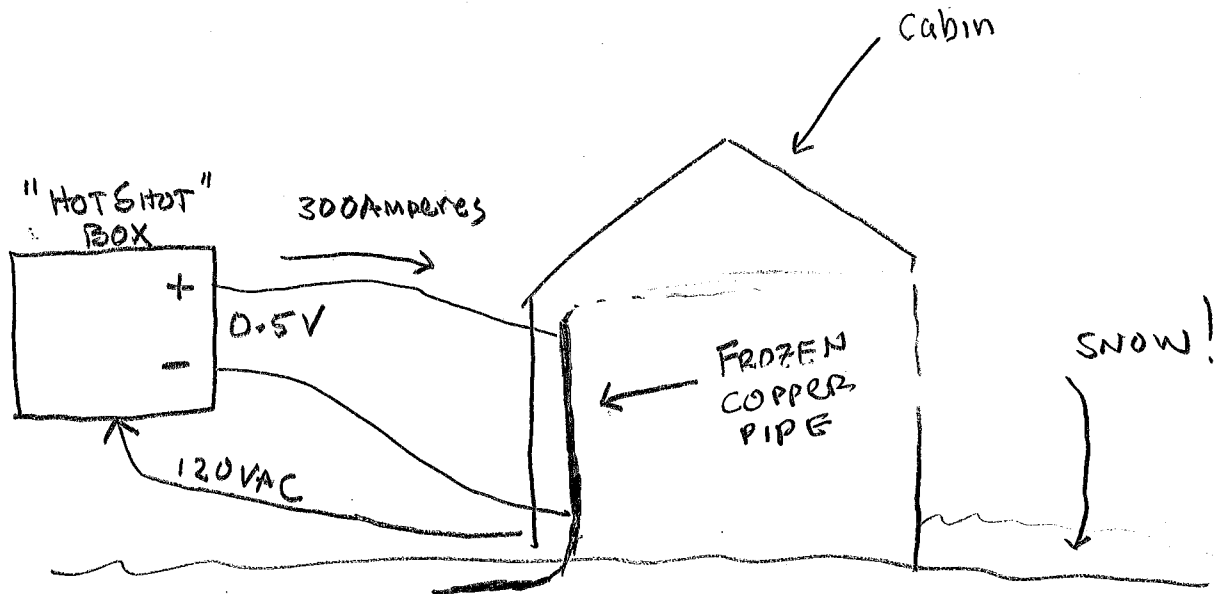


# LECTURE #1

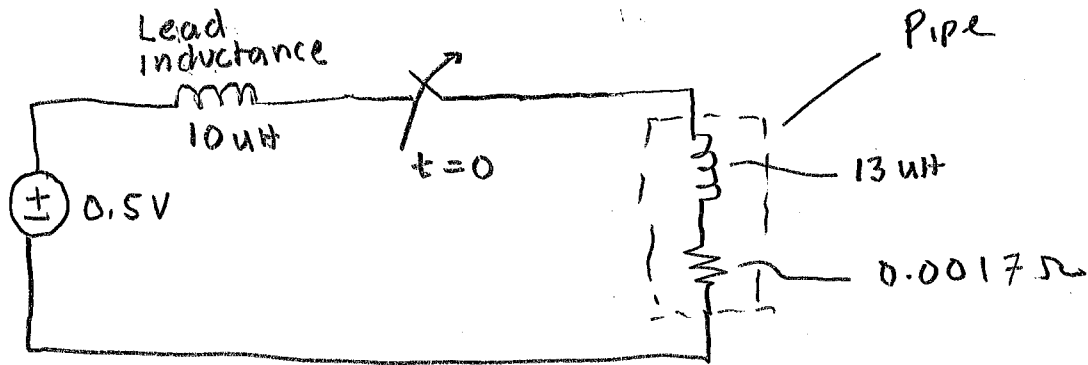

- IF you don't drain the pipes in the winter, they Freeze.
- The "Hot shot" box delivers Direct current (DC) at 0.5V
- The high current causes resistive heating in the frozen pipe and melts the ice.
- How does the Hot shot box convert 120 VAC (from wall outlet) to 0.5V at 300 A ?
- Why were there big sparks happening when the plumber disconnected the machine to the pipes ?

Make a model



With the switch closed,

$$i(0^-) = \frac{0.5V}{0.0017 \Omega} = 294 A$$

$$L I^2 R = 294^2 \times 0.0017 = 147W \text{ in pipe}$$


We know  $V_L = L \frac{di}{dt}$

Opening switch causes current to stop immediately,

Or  $V_L = L \frac{di}{dt} = L \times -\infty = -\infty$

The high voltage across the inductors causes sparks even though the <sub>Source</sub> voltage was only 0.5 VDC!

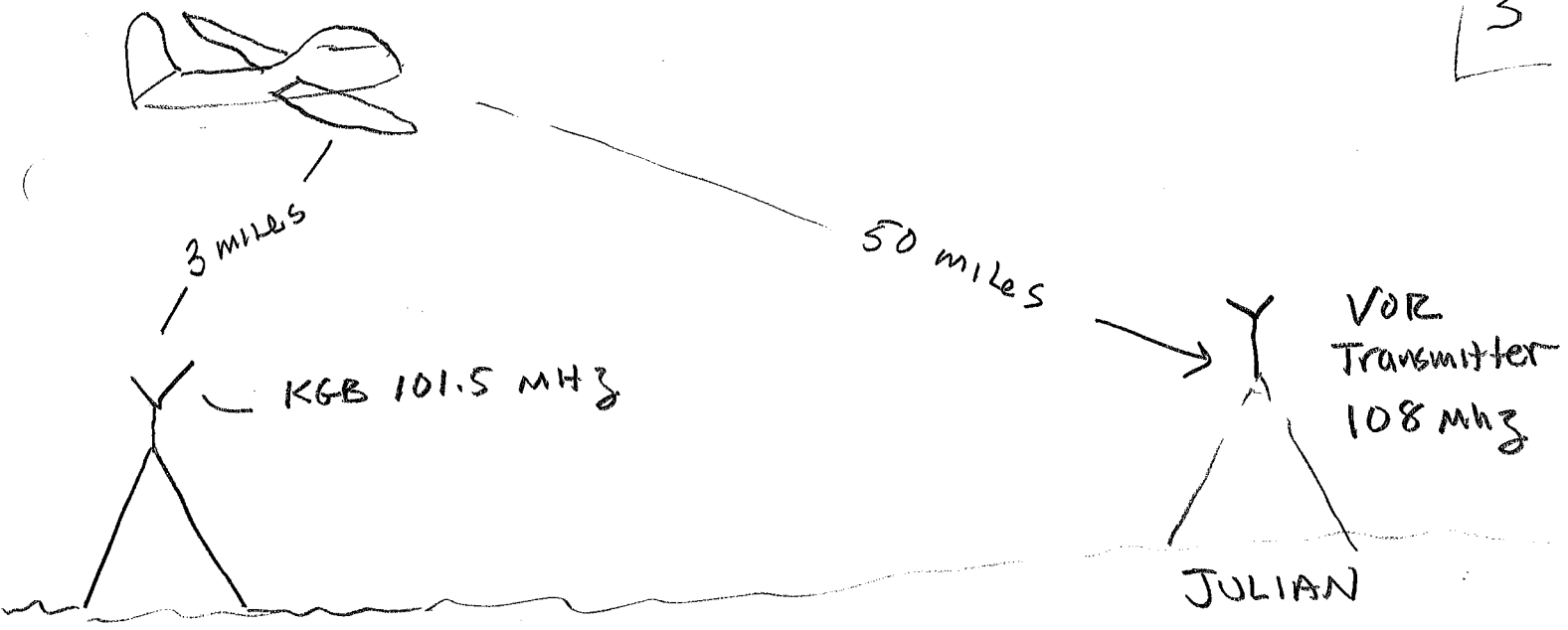- The same idea is used to make a spark in the spark plugs in your car.
- The same idea is responsible for injury and death when jump starting cars incorrectly.






Signal strength is proportional to  $\frac{K_p}{d^2}$

$$\frac{\text{Power from KGB}}{\text{Power from Vor}} = \frac{K_p/3^2}{K_0/50^2} = \frac{50^2}{3^2} = 278$$

This is the difference between the horn playing and a conversation

So how can the aircraft "hear" the VOR station?

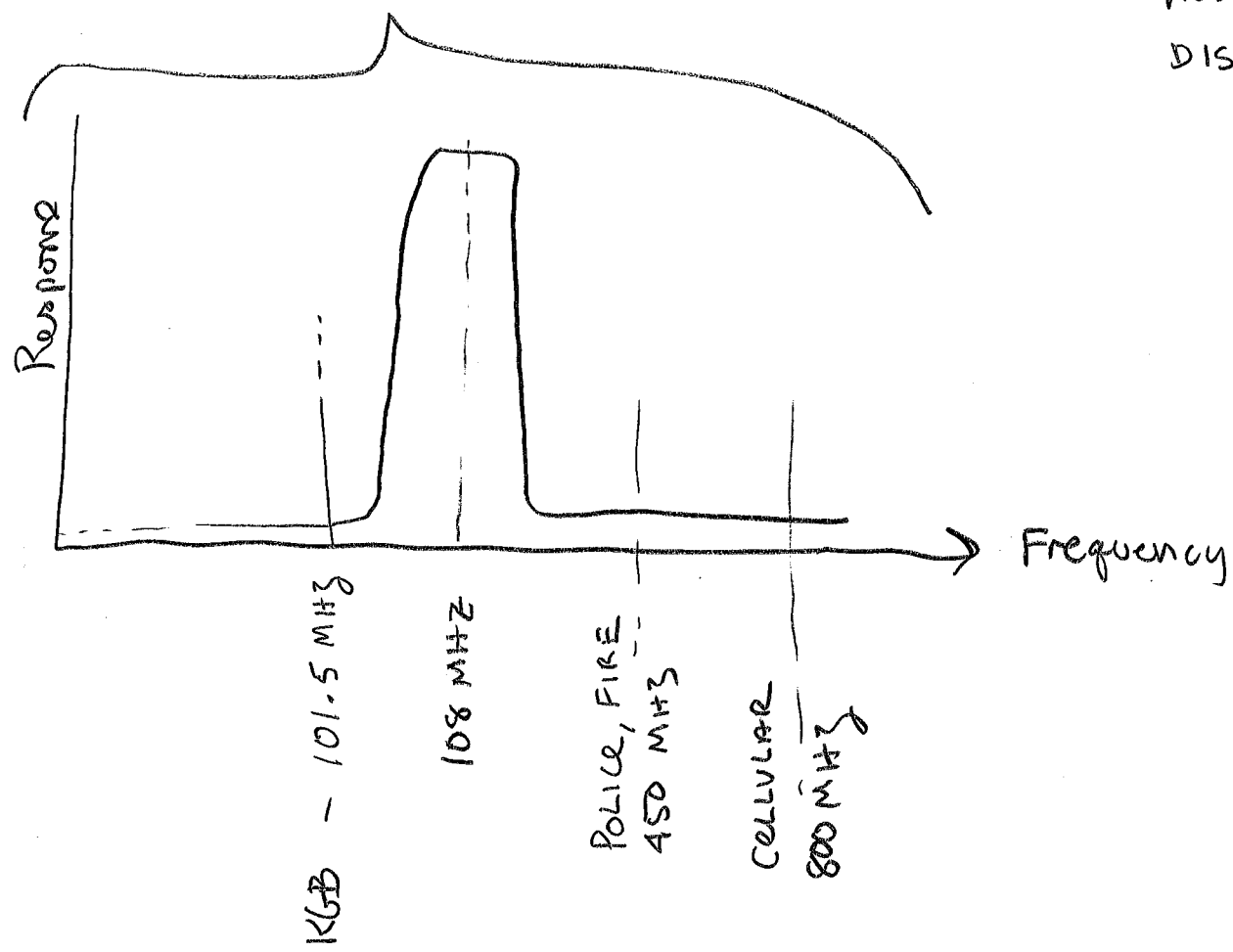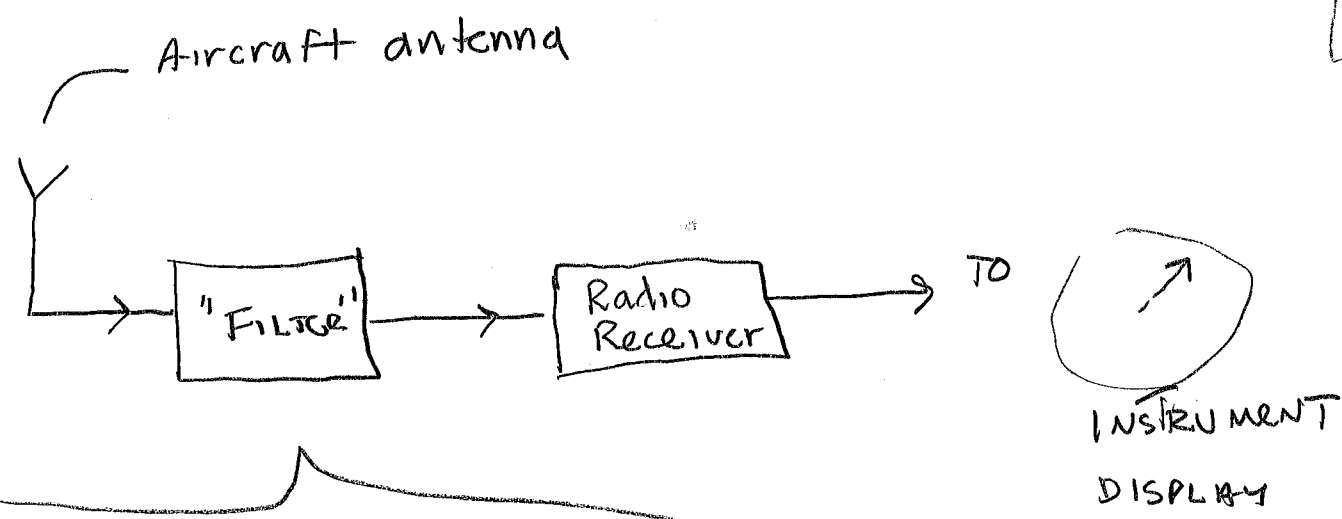

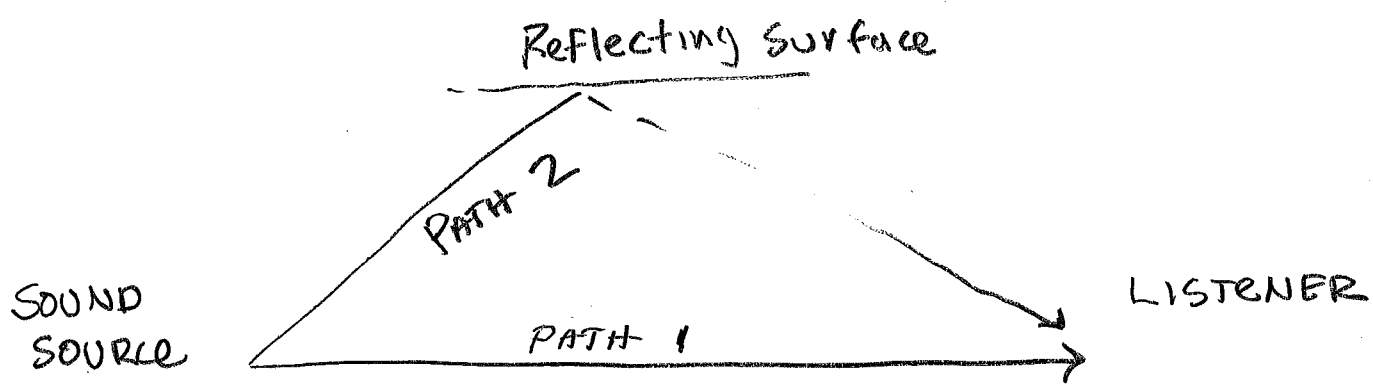

Path 1: Listener hears  $A \cos(2\pi f t)$

Path 2: Listener hears  $A \cos(2\pi f(t + \tau))$

Where  $\tau$  is the time difference between the two paths.

Path 1 plus Path 2


$$S(t) = A (\cos(2\pi f t) + \cos(2\pi f(t + \tau)))$$

$$\underbrace{\hspace{10em}}_{\cos(2\pi f t + 2\pi f \tau)}$$

Say  $\tau = \frac{1}{2f}$  or  $f = \frac{1}{2\tau}$

$$\cos(2\pi f t + \pi) = -\cos(2\pi f t)$$

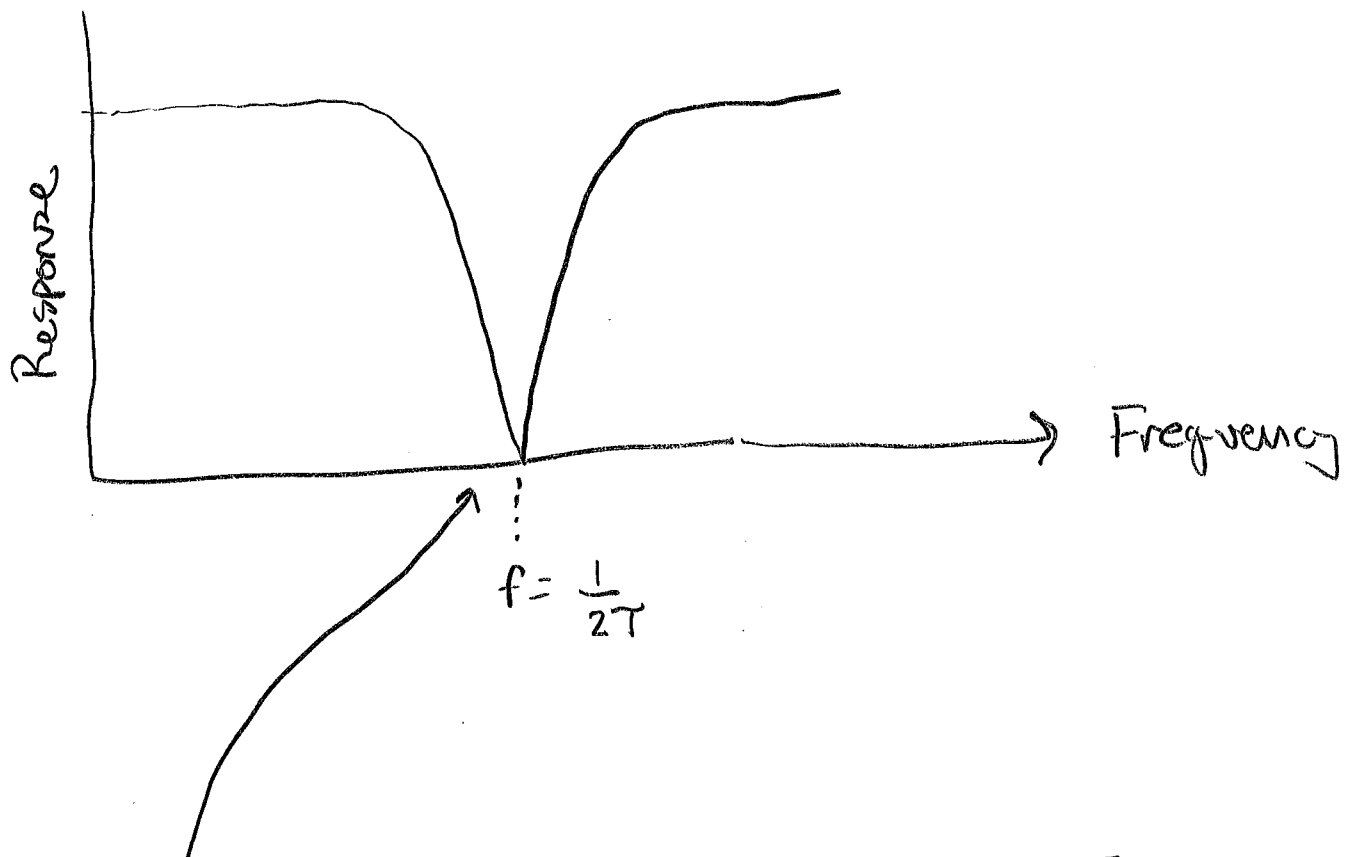
$$S(t) = A (\cos(2\pi f t) - \cos(2\pi f t)) = 0$$



what if someone plays this note?

IN EE 310 we will use Laplace transforms to analyze and solve much more complex and interesting systems.
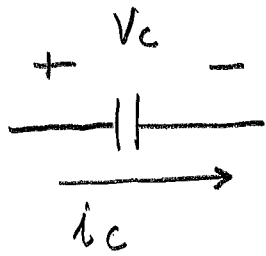
# Lecture #1 - INITIAL AND FINAL CONDITIONS




$$i_c = C \frac{dv}{dt}$$

"stores energy in electric field"

"Passive Sign Convention"

see Fig 6.3 and 6.23 in text

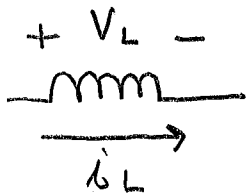

$$V_L = L \frac{di}{dt}$$

"stores energy in magnetic field"

In chapters 8 and 16 we will analyze behavior

- We will start with the circuit at steady state  $\rightarrow$  voltages and currents not changing with time.
- we will suddenly change the circuit topology by changing a switch or applying a voltage.
- we will observe voltages and currents immediately after the switch changes
- we'll get thuds (drop a beam bag) and boings (drop a piece of copper pipe)

## Capacitors and inductors store energy

Energy in capacitor =  $\frac{1}{2} CV^2$  Joules

Energy in inductor =  $\frac{1}{2} LI^2$  Joules

Power =  $W = \frac{\text{Joules}}{\text{sec}}$   $\rightarrow$  rate of energy transfer

Can I instantly change the energy in an inductor or capacitor?

### Terminology

$v(0^-)$  or  $i(0^-)$   $\rightarrow$  current or voltage immediately before switch is changed.

$v(0^+)$  or  $i(0^+)$   $\rightarrow$  current or voltage immediately after switch is changed.

$v(\infty)$  or  $i(\infty)$   $\rightarrow$  current or voltage after all transients have subsided



The Rules

"Verbal"

Equation

Inductor current cannot change instantaneously"

$$i_L(0^+) = i_L(0^-) \quad (1)$$

Capacitor voltage cannot change instantaneously

$$V_C(0^+) = V_C(0^-) \quad (2)$$

Inductor voltage can change instantaneously

$$V_L = L \frac{di}{dt} \quad (3)$$

Capacitor current can change instantaneously

$$i_C = C \frac{dV}{dt} \quad (4)$$

At steady state  $\frac{di}{dt} = 0$  so  
inductor voltage is zero

$$V_L(\infty) = 0 \quad (5)$$

At steady state  $\frac{dV}{dt} = 0$  so

$$I_C(\infty) = 0 \quad (6)$$


$$i_C = 0$$

Example

The switch has been "closed for a long time"

It opens at  $t = 0$ .

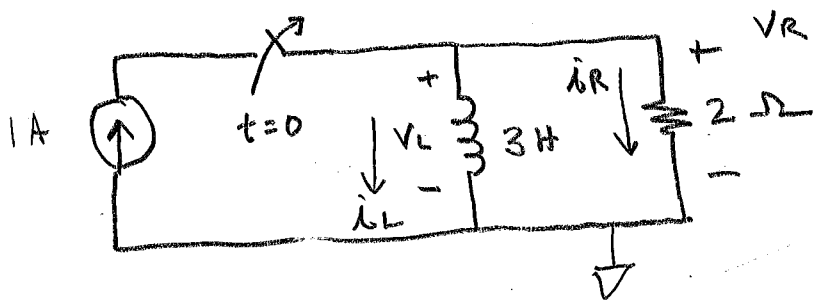Compute  $\frac{di_L}{dt}(0^+)$  and  $V_L(\infty)$



$V_L(\infty) = 0$

$$i_L(0^-) =$$

$$V_L(0^-) =$$

$$V_R(0^-) =$$

When switch opens  $i_L(0^+) = i_L(0^-)$  So  $i_R(0^+) = -1A$


$$V_R(0^+) = -2V$$

$$\text{Therefore } V_L(0^+) = -2V$$


$$\text{Since } V_L = L \frac{di_L}{dt}, \quad \frac{di_L}{dt}(0^+) = \frac{V_L(0^+)}{L}$$

$$= -\frac{2}{3} = -0.66 \text{ A/s}$$

Does the sign look reasonable?

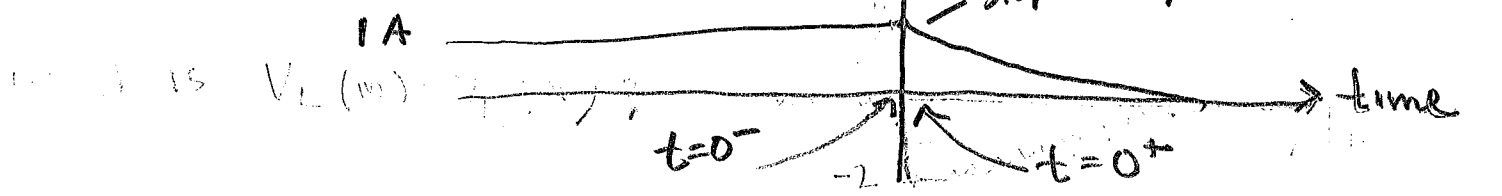

# Example

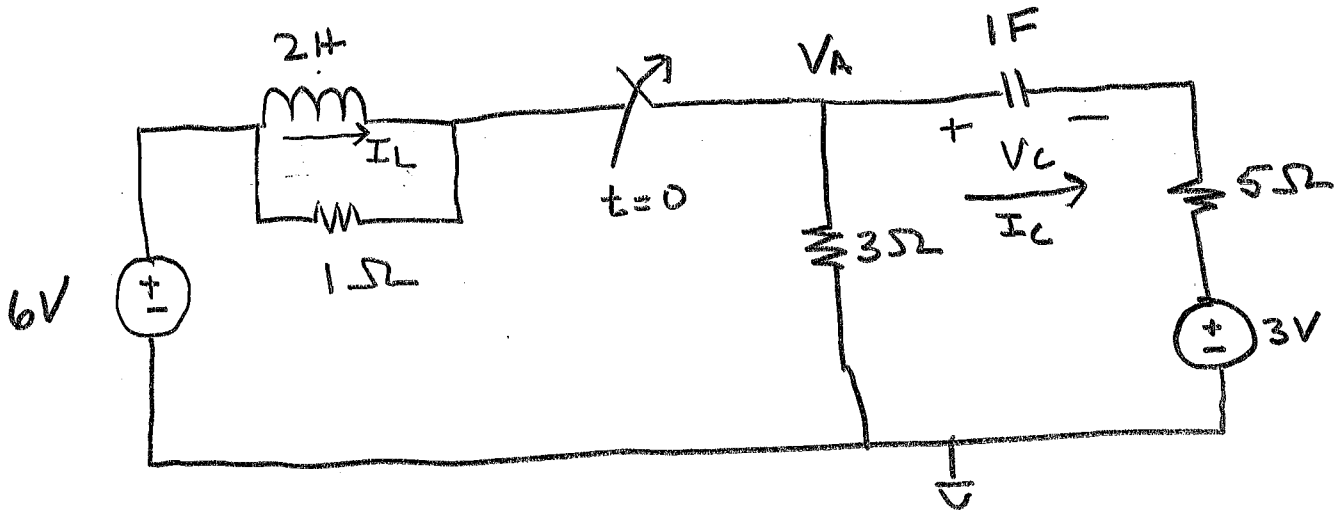

$$\underline{I_L(0^-)} = \frac{6V}{3\Omega} = 2A$$

$$\underline{V_A(0^-)} = 6V$$

$$\underline{V_C(0^-)} = 6 - 3 = 3V$$

$$\underline{I_L(0^+)} = I_L(0^-) = 2A$$

$$\underline{V_C(0^+)} = V_C(0^-) = 3V$$

$$\underline{I_C(0^+)}$$


KVL

$$3I_C + 3 + 5I_C + 3 = 0$$

$$8I_C + 6 = 0$$

$$I_C = \frac{-6}{8} = -0.75A$$

$$\text{SO } I_C(0^+) = -0.75A$$

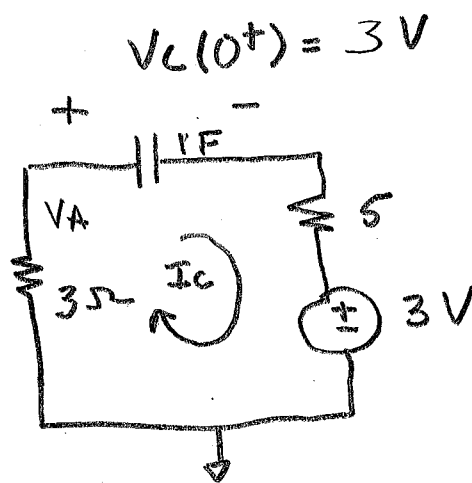

Example - CONT

$V_A(t=0^+)$

$$V_A(0^+) = -I_C(0^+) \times 3\Omega = 0.75 \times 3 = 2.25V$$

$dV_C/dt(0^+)$

$$i = C \frac{dv}{dt} \text{ so } dv = \frac{i}{C} = -\frac{0.75}{1} = -0.75V/s$$