

# LECTURE 10 - INSTANTANEOUS AND AVERAGE POWER

## BACKGROUND CONCEPTS:

ENERGY: "I hiked up the mountain" (Joules)

Power: "I can hike 1000 vertical feet in one hour"  
(Joules/second = Watts)


Work and power: "I hiked up the mountain in an hour"

Your Power bill: kW-hrs  $\rightarrow \frac{J}{s} \times s = \text{Joules}$


Useful relationship: 1 Horsepower = 746 Watts.

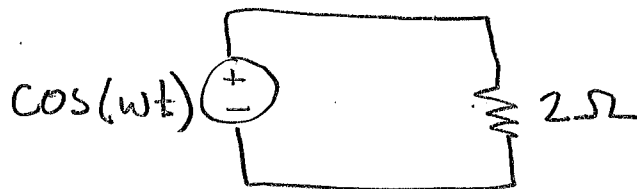
## Instantaneous Power

$$P(t) = V(t) i(t) \quad \leftarrow \text{EQ 11.1}$$


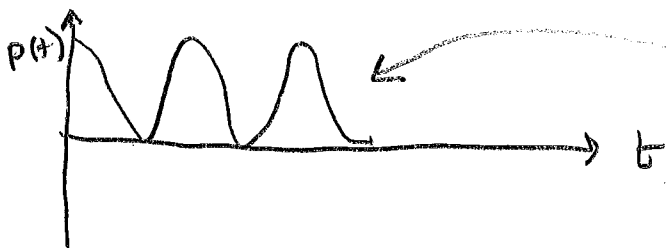
$$P(t) = V(t) i(t) = \cos(\omega t) \times \frac{\cos(\omega t)}{2} = \frac{1}{2} \cos^2(\omega t)$$



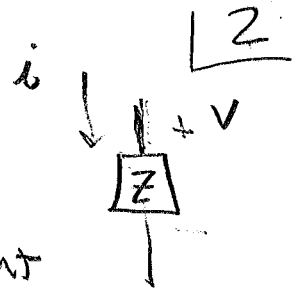

$v(t) = V_m \cos(\omega t + \phi_v)$  — Instantaneous voltage

$i(t) = I_m \cos(\omega t + \phi_i)$  — Instantaneous current


Instantaneous Power is

$$P(t) = v(t)i(t) = V_m \cos(\omega t + \phi_v) \cdot I_m \cos(\omega t + \phi_i)$$

Use the trigonometric identity:

$$\cos(A) \cos(B) = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$
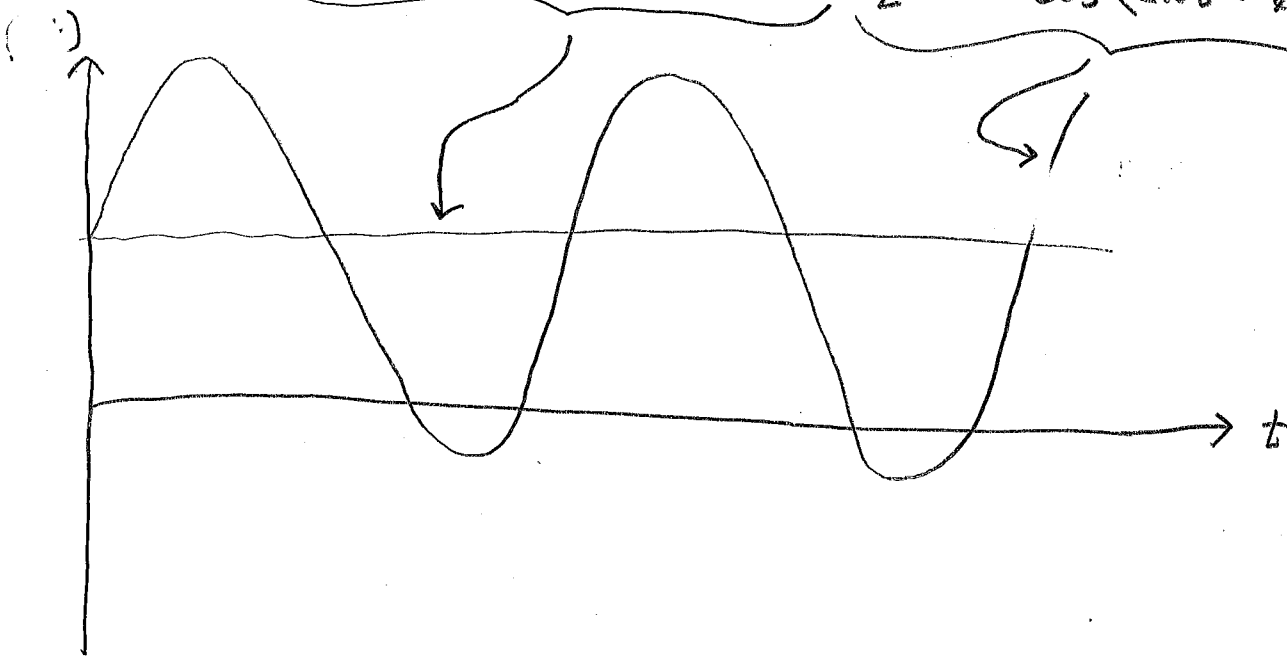
$$\text{So } P(t) = \underbrace{\frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)}_{\text{Constant part}} + \underbrace{\frac{1}{2} V_m I_m \cos(2\omega t + \phi_v + \phi_i)}_{\text{Time varying part}}$$




So instantaneous power has a constant part and a time varying part.

Average Power is the constant part:

$$P = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$$

Definition of average power for a waveform with period  $T$
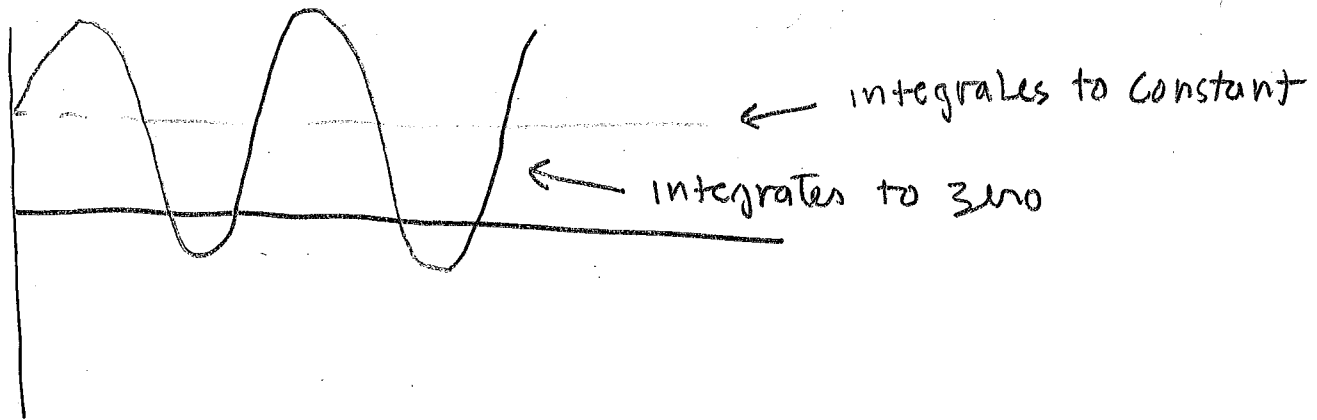
$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T p(t) dt$$



Say  $v(t)$  and  $i(t)$  are expressed as phasors:

$$\frac{1}{2} V \cdot I^* \quad \left\{ \begin{array}{l} \text{complex conjugate} \end{array} \right.$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$

This term is the average power!

$$\text{So } P = \frac{1}{2} \operatorname{Re}\{V \times I^*\} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

EQ 11.10

# Power in Components

14

( Resistor - voltage and current are in phase.

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 \cdot R$$

Why isn't power =  $V \times I$  like it is for DC ??

## INDUCTOR

$$\frac{V}{I} = j\omega L \quad \text{so} \quad V = j\omega L I$$

↑  
Voltage and current are  
90° out of phase

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = 0$$

Inductor is an energy storage element

## Capacitor


$$\frac{V}{I} = \frac{1}{j\omega C} \quad \text{or} \quad V = I \times \frac{1}{j\omega C} = -I \times \frac{1}{\omega C} \times j$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = 0$$

↑  
Voltage and  
current are  
out of phase!

# POWER SUPPLY

DC SOURCE  
V

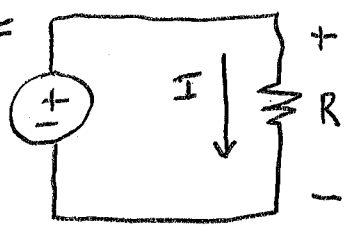

Passive Sign Convention


Power dissipated by resistor is  $V \times I$  (Positive)

Power dissipated by supply is  $V \times (-I) = -VI$  (Negative)

The power supply dissipates negative power.

EXAMPLE:

Compute power dissipated in the circuit

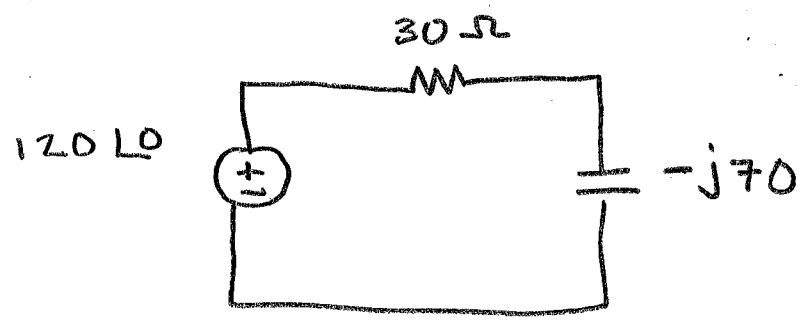

$$I = \frac{V}{Z} = \frac{120 + j0}{30 - j70} = 1.58 \angle 66.8^\circ \text{ A}$$

$$V_R = I_R \times R = 1.58 \angle 66.8^\circ \times 30 \text{ V}$$

$$P = \frac{1}{2} \text{Re}(V \times I^*) = \frac{1}{2} \text{Re}\{1.58 \angle 66.8^\circ \times 30 \times 1.58 \overset{\text{conj}}{\angle -66.8^\circ}\} \text{ W}$$

$$= \frac{1}{2} \text{Re}\{74.89 \angle 0^\circ\} = \underline{\underline{37.44 \text{ W}}}$$

What is supply power?

How many joules are delivered to the resistor

( In 10 seconds?

If the resistor were shaped like a golf ball and you held it in your hand, would you get burned?

Practical power formula

in the previous example, we know only the resistor can dissipate power.

( We also know voltage and current for the resistor are in phase.


so  $P = \frac{1}{2} V_m I_m \overset{1.0}{\cos(\Delta\phi)} = \frac{1}{2} V_m I_m$

$V_m = I_m \cdot R$  so  $P = \frac{1}{2} I_m \cdot R \times I_m$

or  $P = \frac{1}{2} I_m^2 \times R = \frac{1}{2} |I|^2 \cdot R$  EQ 11.10

In the last example,  $|I| = 1.58A$  so  $P = \frac{1}{2} \times 1.58^2 \times 30$   
 $= 37.4 W$

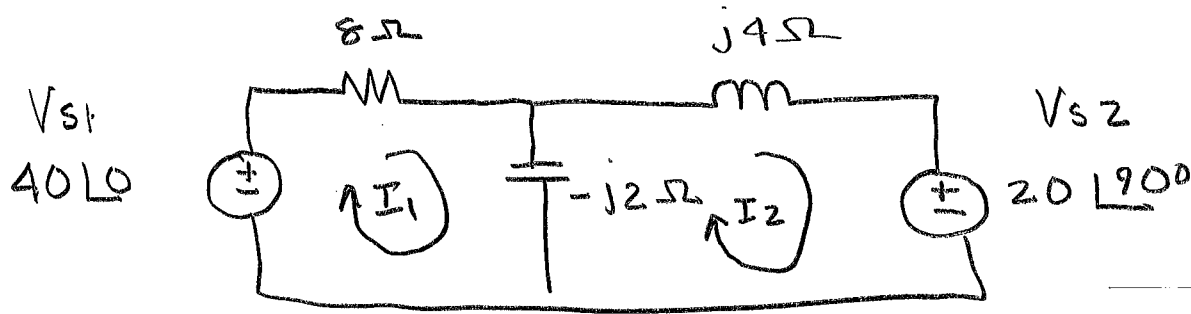Calculate the power absorbed by each of the five elements in the circuit.



Triage the problem

Capacitor power = 0

Inductor power = 0

Resistor power is positive

$P_{s1} + P_{s2} + P_R = 0 \rightarrow$  "Power from source = power dissipated in resistor"

$\downarrow$  Negative power dissipation

If I can get the two mesh currents  $I_1, I_2$  then

$P_R = \frac{1}{2} |I_1|^2 \cdot R \rightarrow$  Power dissipated by source 1

$P_{V_{s1}} = -\frac{1}{2} |V_{s1}| \times |I_1| \cos(\phi_{V_{s1}} - \phi_{I_1})$  Neg. because  $I_1$  leaves  $V_{s1}$

$P_{V_{s2}} = \frac{1}{2} |V_{s2}| \times |I_2| \cos(\phi_{V_{s2}} - \phi_{I_2})$  Pos because  $I_2$  enters  $V_{s2}$

Get  $I_1, I_2$

Lecture 10

18

$$(1) -V_{s1} + 8I_1 - j2(I_1 - I_2) = 0$$

$$(8 - j2)I_1 + j2I_2 = V_{s1}$$

$$(2) -j2(I_2 - I_1) + j4I_2 + V_{s2} = 0$$

$$j2I_1 + (j4 - j2)I_2 = -V_{s2}$$

so

$$\begin{bmatrix} 8 - j2 & j2 \\ j2 & j4 - j2 \end{bmatrix}^{-1} \begin{bmatrix} V_{s1} \\ -V_{s2} \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_{s1} = 40 + j0 \quad V_{s2} = j20$$

$$I_1 = 3 + j4 \quad I_2 = -13 - j4$$

$$I_1 = 5 \angle 53.13^\circ \quad I_2 = 13.6 \angle -162.9^\circ$$

$$P_R = \frac{1}{2} |I_1|^2 \times 8 = 100 \text{ W} \leftarrow = 0$$

$$P(\text{Source 1}) = \frac{1}{2} |V_{s1}| \times |I_1| \cos(0 - \theta_{I_1})$$

$$= \frac{1}{2} \times 40 \times 5 \times \cos(-53.13^\circ) = 60 \text{ W}$$

$$P_{\text{Source 2}} = \frac{1}{2} |V_{s2}| \times |I_2| \times \cos(90 + 162.9^\circ)$$


$$= \frac{1}{2} \times 20 \times 13.6 \times \cos(90 + 162.9^\circ) = -40 \text{ W}$$

check



# Maximum Power Transfer

Consider the Thevenin Source

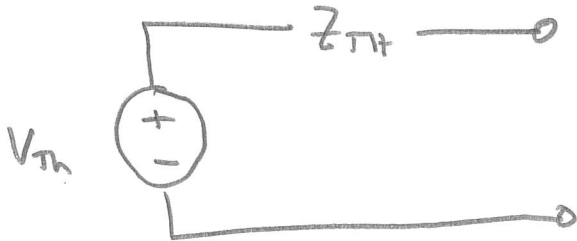

- Load the source with an inductor
- Load the source with a capacitor
- Load the source with an open circuit
- Load the source with a short circuit


How much power dissipated in load?

What is needed to dissipate power??

Big resistor  $\rightarrow$  No power because minimal current

Small resistor  $\rightarrow$  No power because minimal voltage.


For DC, we know

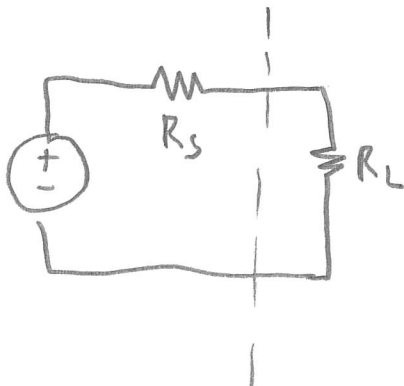

For a source with Thevenin resistance  $R_s$ , max power transfer occurs when


$$R_L = R_s$$

Tricky Interview question

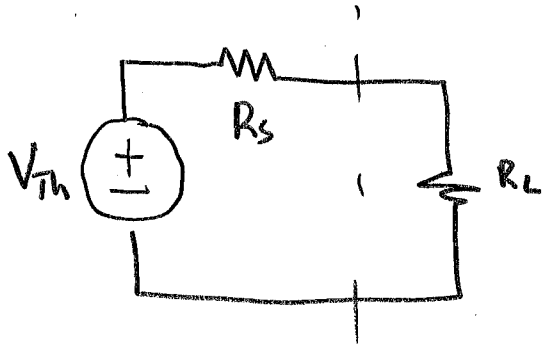

Pick  $R_s$  for maximum power transfer


Maximum power transfer for AC circuits

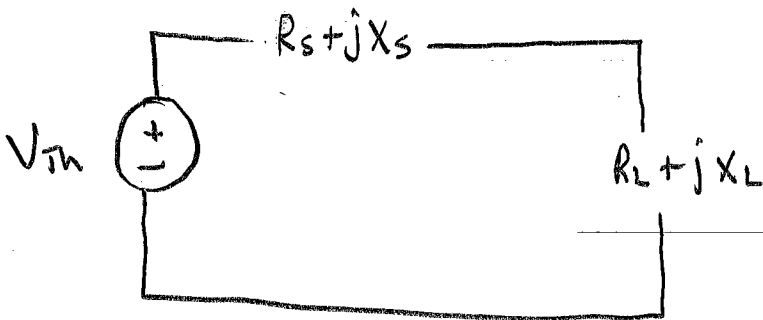

See derivation on Pg 465 of Text.

Intuitive 'derivation'

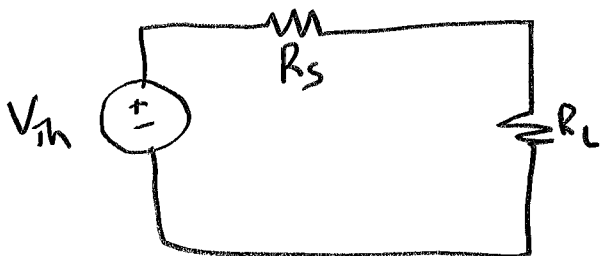- Load power will be dissipated in  $R_L$  only.
- IF  $jX_s + jX_L = 0$  then the circuit becomes



and for max power transfer,  $R_L = R_s$


- IF  $jX_s + jX_L \neq 0$  current will decrease and  $|I|^2 R_L$  will decrease also

$$\text{IF } jX_s + jX_L = 0 \text{ then } jX_s = -jX_L$$

$$\text{OR } Z_L = Z_s^*$$

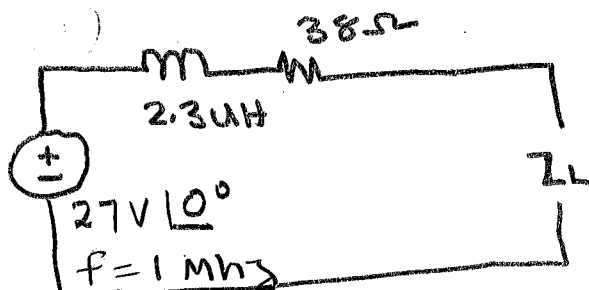Example

Find  $Z_L$  for maximum power transfer.  
Find maximum power delivered to load.



$$Z_s = 38 + Z_{IND}$$

$$= 38 + j2\pi \times 10^6 \times 2.3\mu\text{H}$$

$$= 38 + j14.45\Omega$$

$$\text{So } Z_L = Z_s^* = 38 - j14.45$$


↓  
Negative so we need a capacitor

$$-j14.45 = \frac{1}{j\omega C}$$

$$C = \frac{1}{-j^2 \times 14.45 \times 2\pi \times 1\text{MHz}} = 11.01\text{nF}$$



### Effective Circuit

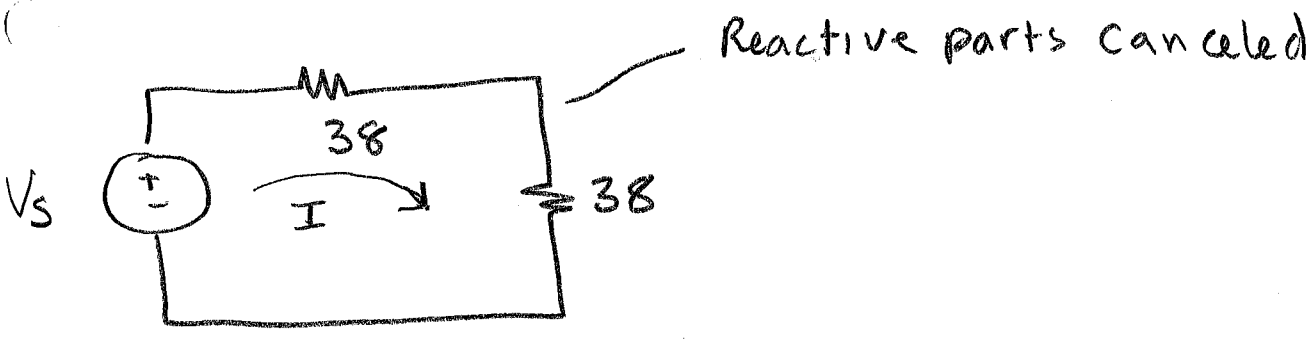

How much power at max power transfer ?

$$I = \frac{V_s}{2R_L} \quad P_{max} = \frac{1}{2} |I|^2 \times R_L$$


$$= \frac{1}{2} \frac{V_s^2}{4R_L^2} \times R_L = \frac{V_s^2}{8R_L} \leftarrow \text{EQ 11.20}$$

For our example, this is

$$\frac{V_s^2}{8R_L} = \frac{27^2}{8 \times 38} = \underline{2.40W}$$

# Supplement for ASSIGN #5

113

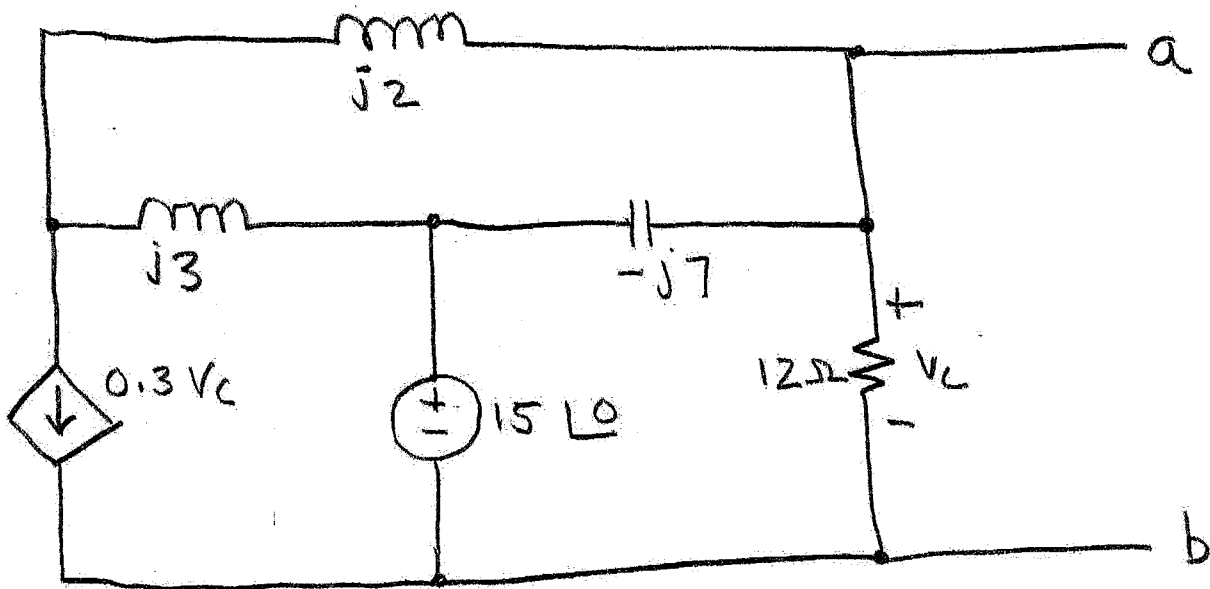

- 1) Determine the load that can be placed between terminals a and b that will receive maximum power transfer from the circuit.
- 2) Determine the power delivered to this load.

Hints: 1) Use KVL or KCL to get  $V_{TH}$

2) For Thevenin impedance, see "case 2" on pg 140

3) I prefer getting  $Z_{TH}$  by computing  $I_{SC}$  then

$$Z_{TH} = \frac{V_{TH}}{I_{SC}}$$