

LECTURE II




1

EFFECTIVE OR RMS VALUES


" For maximum average power transfer, the load impedance Z_L must be equal to the complex conjugate of the Thevenin impedance Z_{Th}^* ←

PG 465

Why this matters

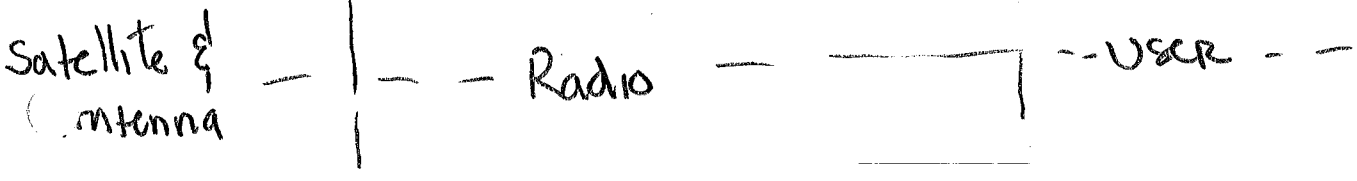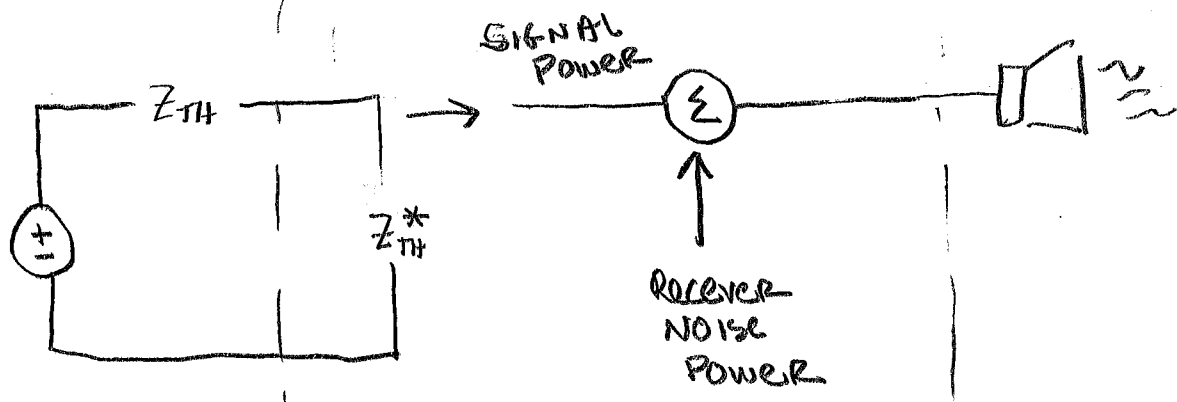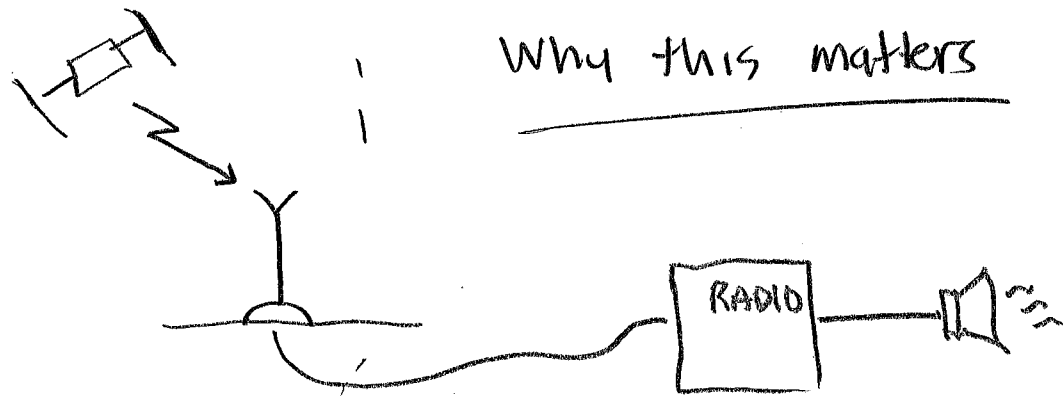


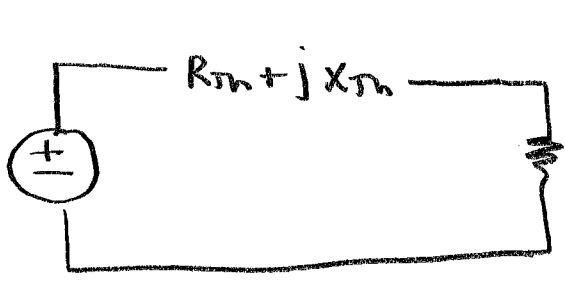Say the Thevenin source is complex, but you can only add a resistor



$$R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |Z_{TH}|$$

EQ 11.21

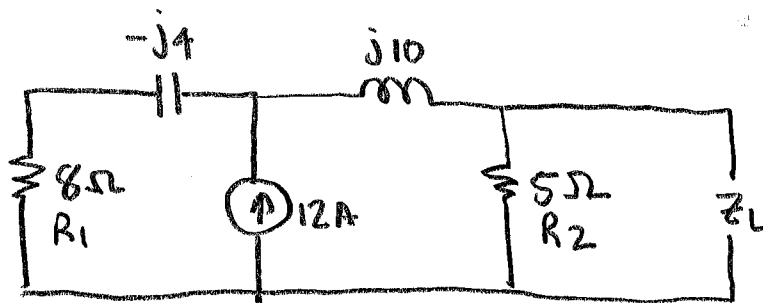

- Find Z_L for maximum power transfer
- Find R_L for maximum power transfer
- Find Load power in both cases

STRATEGY: Represent as thevenin source

$$Z_L = Z_{TH}^*$$

$$Z_L \text{ (resistor only)} = |Z_{TH}| \leftarrow \text{EQ 11.2}$$

$$P_{wr} (Z_L = Z_{TH}^*) = \frac{|V_{Th}|^2}{8R_{TH}} \leftarrow \text{EQ 11.20}$$

P_{wr} (Resistor only) \rightarrow solve for current, use

$$P = \frac{1}{2} |I|^2 R$$

Thevenin Impedance


$$Z_{TH} = R_2 \parallel (8 - j4 + j10) = R_2 \parallel (8 + j6) = 5 \parallel (8 + j6)$$

$$= \frac{5(8 + j6)}{5 + (8 + j6)} = 3.415 + j0.732$$

Thevenin Voltage

$$12 \times \frac{(8 - j4)}{8 - j4 + j10 + 5} \times 5 = 23.41 - j29.27 \text{ V}$$

Current in right branch $\times 5\Omega$

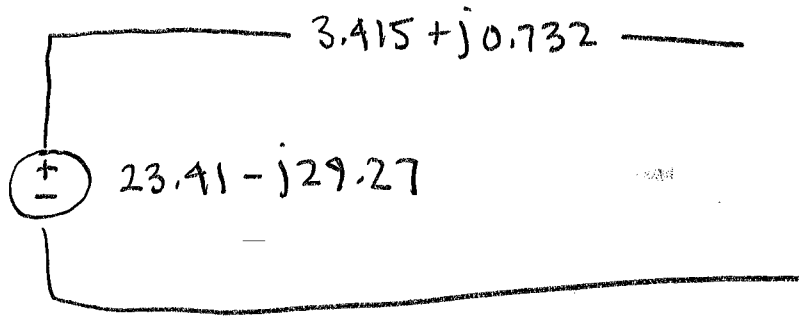


↑
Thevenin representation for Prac Prob 11.5

$$\text{So } Z_L = Z_{Th}^* = \underline{3.415 - j0.732}$$

$$P_{\max} = \frac{|V_{Th}|^2}{8R_{Th}} = \frac{1405}{8 \times 3.415} = \underline{51.42 \text{ W}}$$

For max pwr in resistive load,

$$R_L = |Z_{Th}| = 3.49 \Omega$$

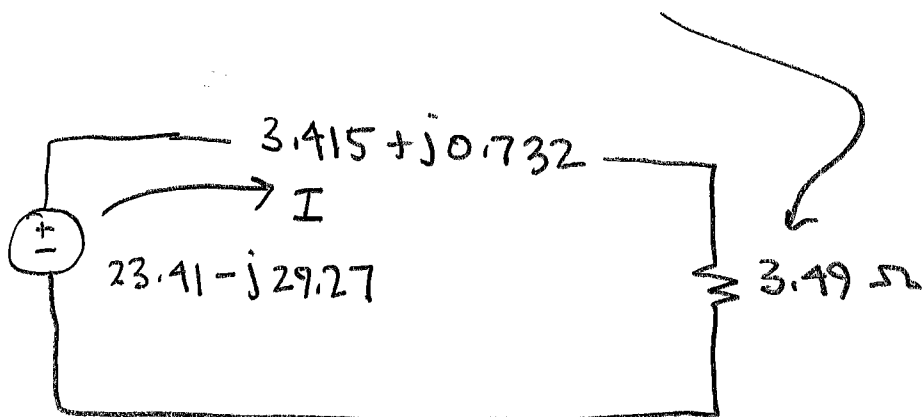

$$I = \frac{23.41 - j29.47}{3.415 + j0.732 + 3.49} = 2.91 - j4.55 = 5.40 \angle -57.4$$

$$\text{So } P = \frac{1}{2} \times |I|^2 R = \frac{1}{2} \times 5.40^2 \times 3.49 = \underline{50.88 \text{ W}}$$

EQ 11.11 ↑

Root Mean Square (RMS) Sec 11.4


LS

from EQ 11.11, $P_R = \frac{1}{2} V_m I_m$

$\frac{1}{2}$ is messy



Here's how engineers like to describe voltages or currents:

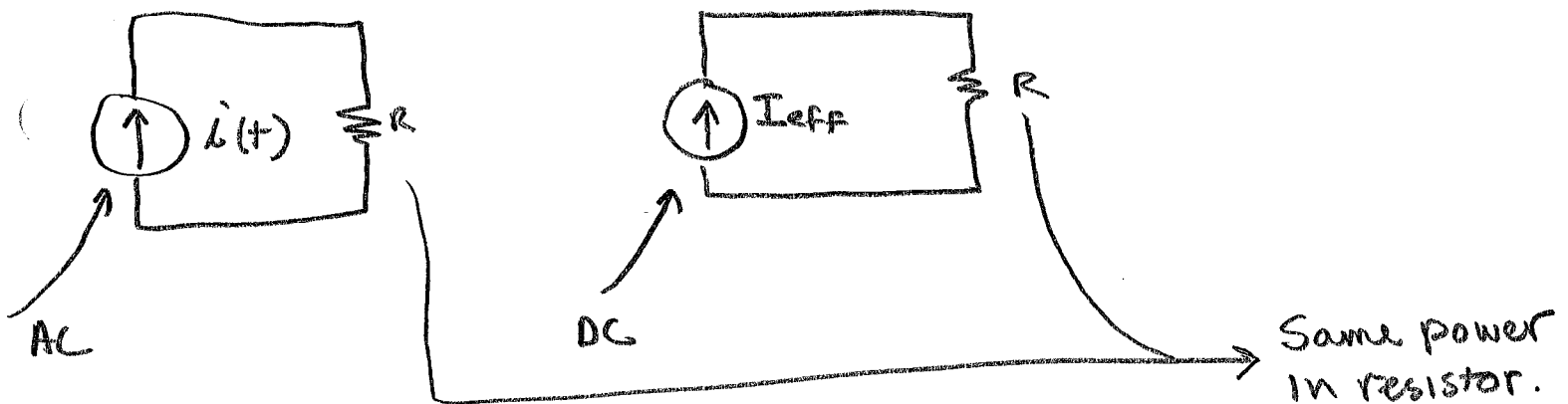"The effective value of a periodic current is the DC current that delivers the same average power to a resistor as the periodic current" (Page 467)



Mathematically
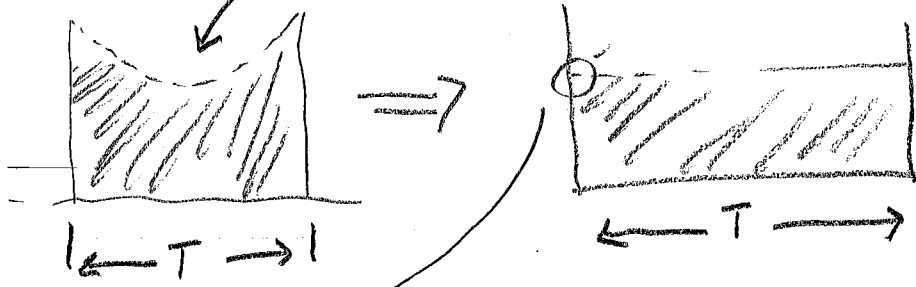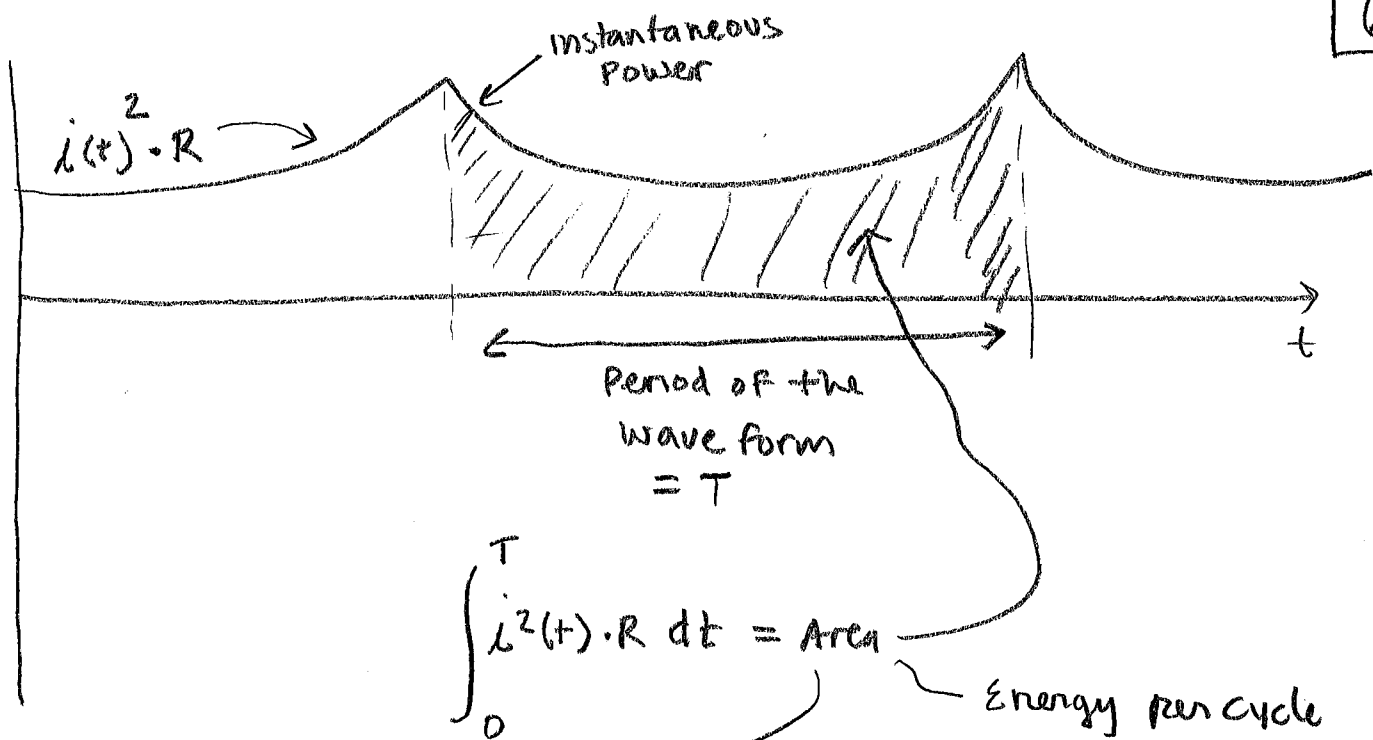
$$\text{Avg Power} = \frac{1}{T} \int_0^T i(t)^2 \cdot R \, dt = I_{eff}^2 \cdot R$$



$$y = \frac{\text{area}}{T} = \frac{1}{T} \int_0^T i^2(t) \cdot R dt = \text{Average Power}$$

Now we relate AC and DC


Average Power

$$I_{\text{eff}}^2 \cdot R = \frac{R}{T} \int_0^T i^2(t) dt$$

So $I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$

Root of the Mean Square

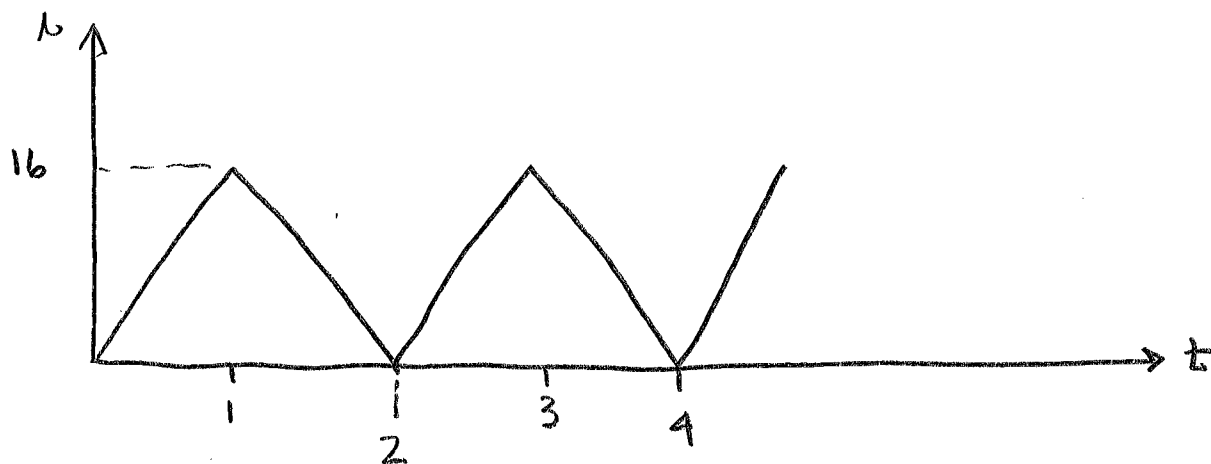Find the rms value of the current. If this current flows through a $9\ \Omega$ resistor, calculate the average power.



$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

Slope of line is $16\ \text{A/s}$ so $i = 16t$ ($0 \leq t \leq 1$)

$$\text{So } i^2(t) = 256 t^2$$


By inspection, the integral from 1 to 2 = integral from 0 to 1

$$\text{So } I_{\text{eff}} = \sqrt{\frac{1}{2} \times 2 \int_0^1 256 t^2 dt}$$

Period

double the integral and integrate from 0 to 1 instead of 0, 2

$$I_{\text{eff}} = \sqrt{256 \times \left. t^3/3 \right|_0^1} = \sqrt{256/3} = \underline{9.23\ \text{A}}$$

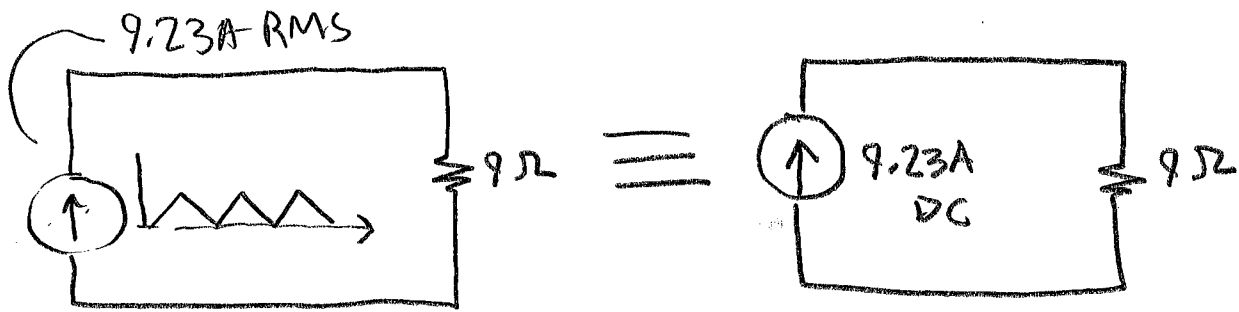


$$I_{RMS}^2 \times R = 9.23^2 \times 9 = 768 \text{ W}$$

$$I^2 R = 9.23^2 \times 9 = 768 \text{ W}$$

periodic

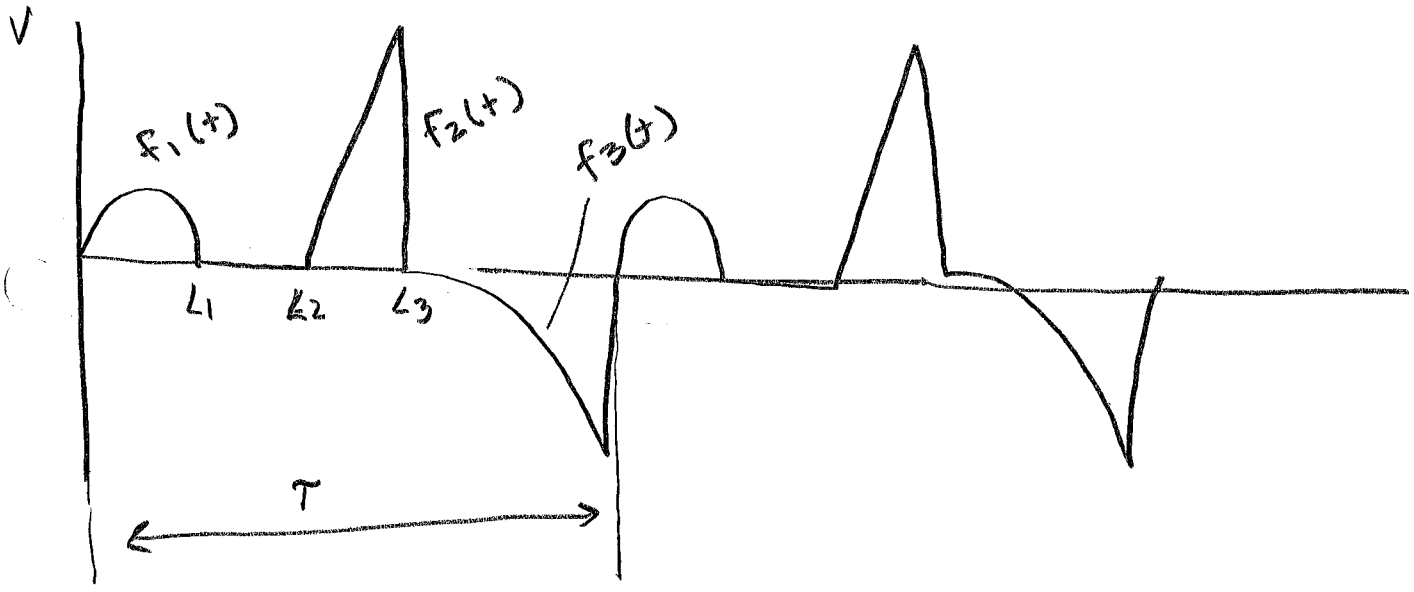
Example shows that if we can integrate the waveform we can compute the RMS value.



$$V_{RMS} = \sqrt{\frac{1}{T} \left[\int_0^{L_1} f_1^2(t) dt + \int_{L_2}^{L_3} f_2^2(t) dt + \int_{L_3}^T f_3^2(t) dt \right]}$$

... even this awful waveform has an rms value

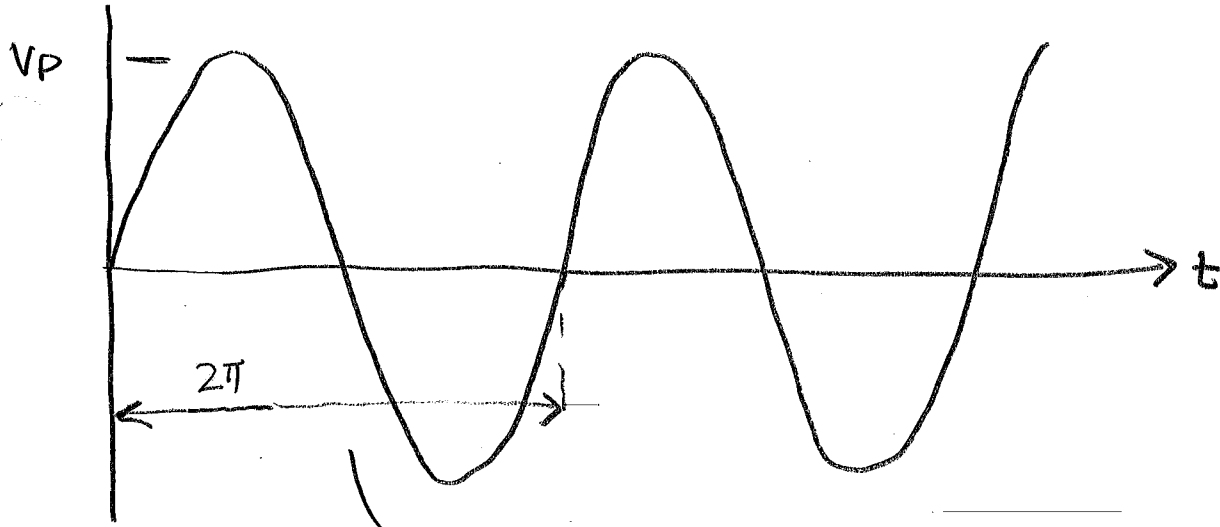NOTE RMS depends on shape and amplitude only



Express period using phase

Sinusoidal voltage (or current)

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_p^2 \sin^2(\phi) d\phi}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_p^2 \cdot \frac{1}{2} (1 - \cos(2\phi)) d\phi}$$

Zero by inspection

$$V_{rms} = V_p \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \frac{1}{2} d\phi - \frac{1}{2\pi} \int_0^{2\pi} \frac{1}{2} \cos(2\phi) d\phi}$$

or integrate!

$$V_{rms} = V_p \sqrt{\frac{1}{2\pi} \times \frac{1}{2} \times 2\pi - \frac{1}{2\pi} \cdot \frac{1}{2} \cdot \left| \frac{1}{2} \sin(2\phi) \right|_0^{2\pi}}$$


$$V_{rms} = V_p \times \frac{1}{\sqrt{2}}$$

EQ 11.29

When we describe household voltage, it's 120 VAC, which is an RMS value

$$V_{rms} = \frac{1}{\sqrt{2}} \times V_{pk} = 0.707 \times V_{pk}$$
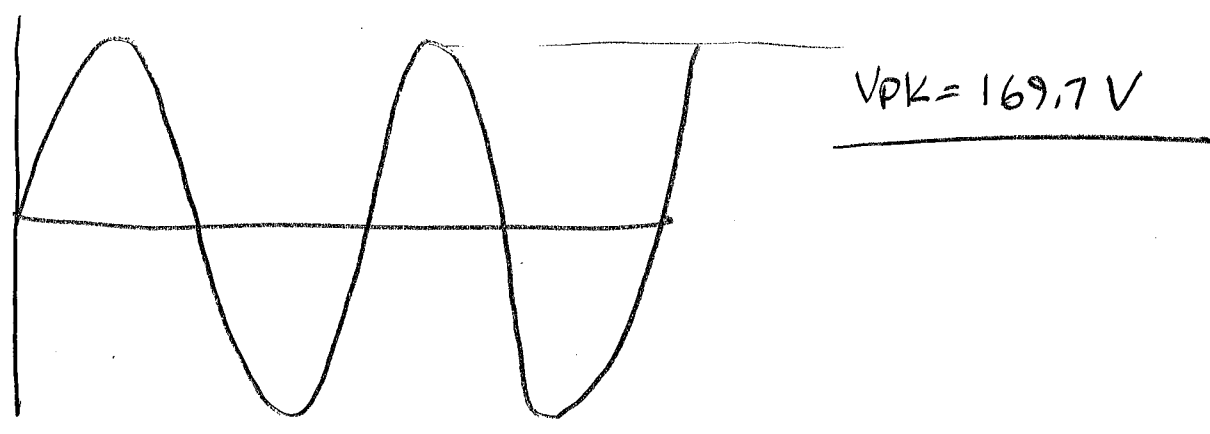
$$\text{So } V_{pk} = \sqrt{2} \times V_{rms} = \sqrt{2} \times 120 = 169.7 \text{ V}_{pk}$$



Remember $P_R = \frac{1}{2} V_m \cdot I_m$ for a resistor?

$$V_m = \sqrt{2} \times V_{rms}, \quad I_m = \sqrt{2} \times I_{rms}$$

$$\text{So } P_R = \frac{1}{2} \sqrt{2} V_{rms} \times \sqrt{2} I_{rms} = V_{rms} \times I_{rms}$$

This holds because

$$P_R = \frac{1}{2} V_m \cdot I_m \rightarrow \text{EQ 11.11}$$


and

$$P = V_{rms} \times I_{rms} \rightarrow \text{EQ 11.30 with } \cos \phi = 1$$

were developed for sinusoidal signals.

Find the effective value of the signal.

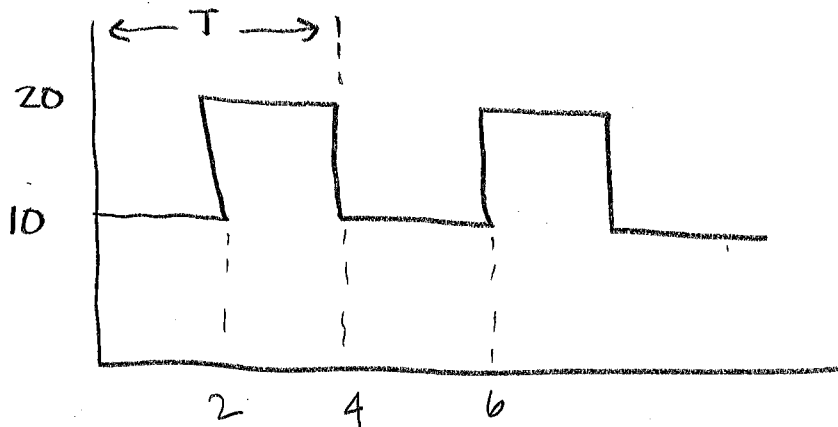Find the peak value of a sinusoidal signal that will deliver the same power to a resistor.




$$V_{rms} = \sqrt{\frac{1}{4} \int_0^2 10^2 dt + \frac{1}{4} \int_2^4 20^2 dt}$$

$$V_{rms} = \sqrt{\frac{1}{4} \int_0^2 100 dt + \frac{1}{4} \int_2^4 400 dt}$$



$$= \sqrt{\frac{1}{4} [200 + (400 \times 4 - 400 \times 2)]} = 15.811 V_{rms}$$

b) Since $V_{rms} = 15.811 V$, V_{pk} for a sine wave with this rms value is $15.811 \times \sqrt{2} = 22.36 V$

COMPUTE V_{rms} Here

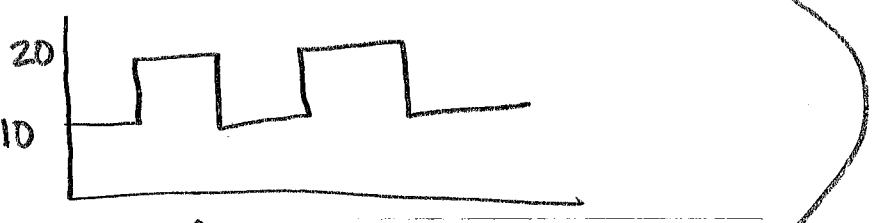

$C = 100F$

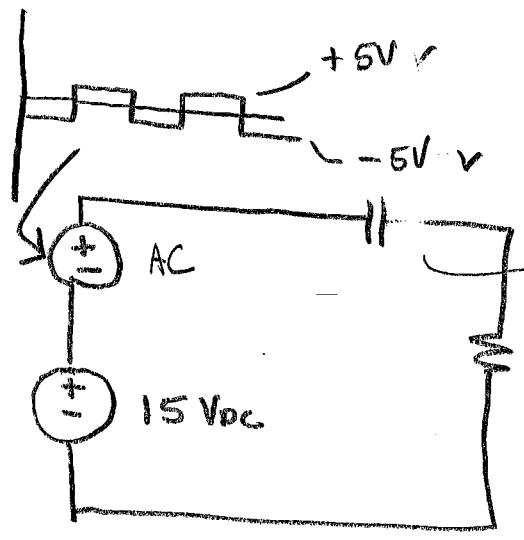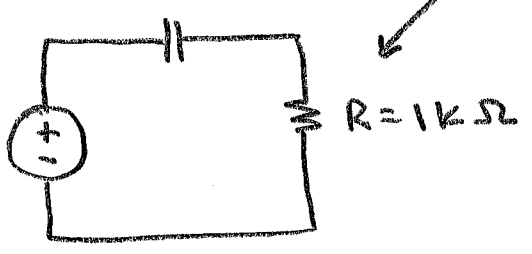


Split source

$$\frac{1}{j\omega C}$$


$$\sqrt{\frac{1}{T} \int_0^T s^2 dt}$$

$$= \sqrt{\frac{T}{T} 25} = 5 V$$


OSCILLOSCOPE COUPLING

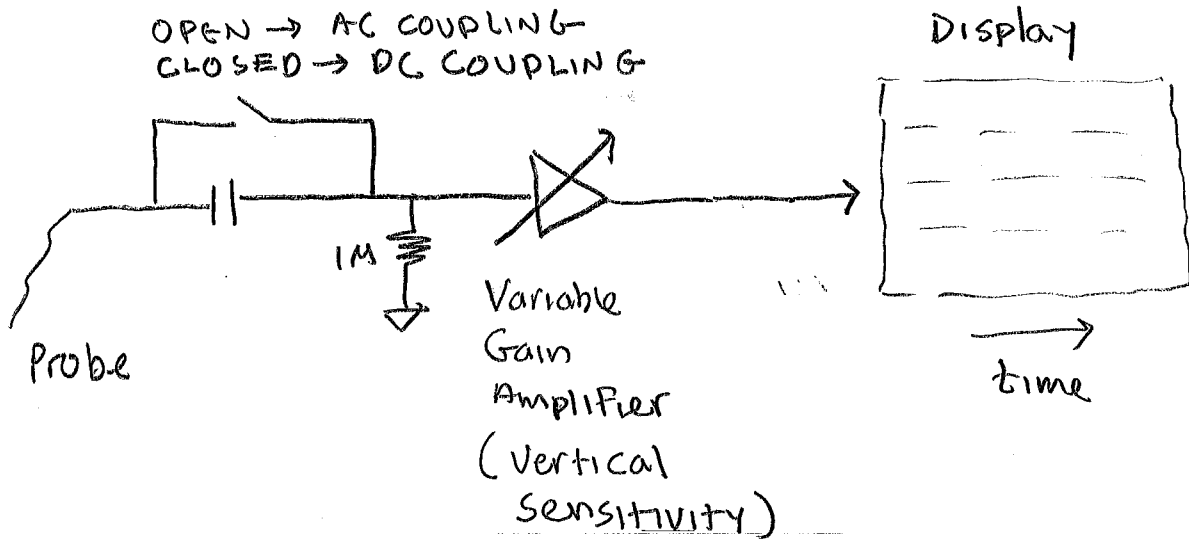

SIGNALS

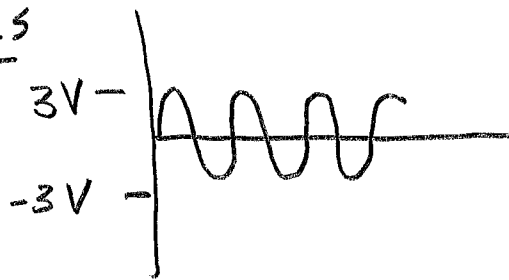

What scale?
What coupling?

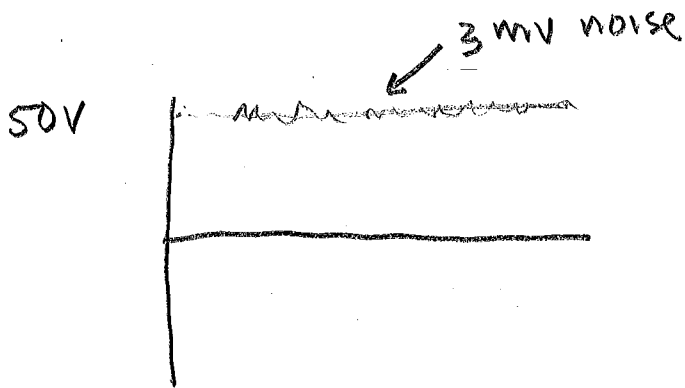

What scale?
What coupling?