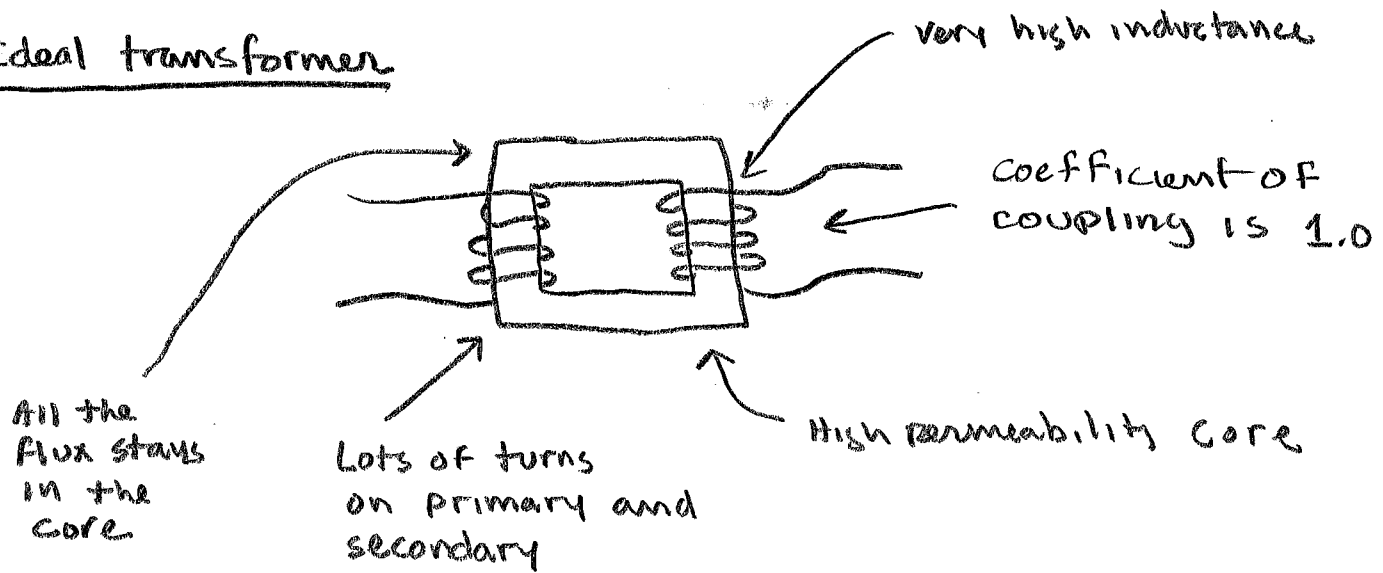


LECTURE 19 - IDEAL TRANSFORMERS

ideal transformer



$$\begin{cases} \textcircled{1} V_1 = j\omega L_1 I_1 + j\omega M I_2 \\ \textcircled{2} V_2 = j\omega M I_1 + j\omega L_2 I_2 \end{cases} \left. \begin{array}{l} \text{Transformer phasor Equations} \\ 13.49a, 13.49b \end{array} \right\}$$

Substituting $\textcircled{1}$ into $\textcircled{2}$ gives (solve $\textcircled{1}$ for I_1)

$$\textcircled{2} \quad V_2 = j\omega L_2 I_2 + \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$$

and since $k=1$, $M = \sqrt{L_1 L_2}$ so


$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1}$$

these cancel

$$V_2 = \frac{\sqrt{L_1 L_2}}{L_1} V_1 = \sqrt{\frac{L_2}{L_1}} V_1 = n V_1$$

where $n = \sqrt{\frac{L_2}{L_1}} = \text{Turns ratio} = \frac{N_2}{N_1}$

We can also show this by

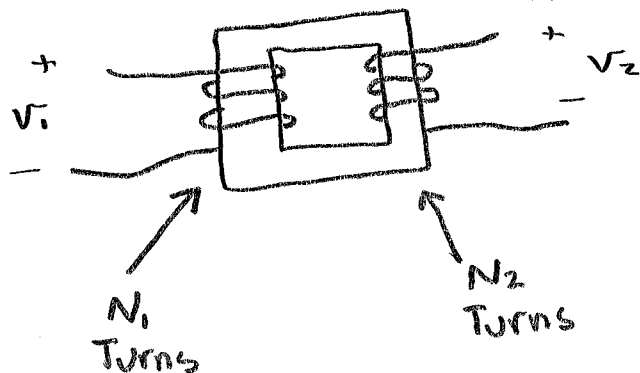


$$v_1(t) = N_1 \frac{d\phi_1}{dt}, \quad v_2(t) = N_2 \frac{d\phi_2}{dt}$$

$k=1$ so

$$\frac{d\phi_1}{dt} = \frac{d\phi_2}{dt} = \frac{d\phi}{dt}$$

and
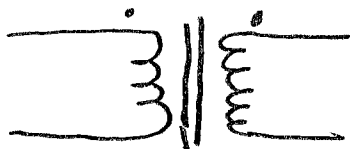
$$\frac{v_2(t)}{v_1(t)} = \frac{N_2 \frac{d\phi}{dt}}{N_1 \frac{d\phi}{dt}} = \frac{N_2}{N_1} = n$$



Symbol for ideal transformer

Ideal transformer absorbs no power so


$$V_1(t) \cdot i_1(t) = V_2(t) \cdot i_2(t) \quad \text{EQ 13.53}$$

in phasor form

$$V_1 I_1 = V_2 I_2$$

$$\text{or } \frac{V_2}{V_1} = \frac{I_1}{I_2} = n \quad \text{EQ 13.55}$$

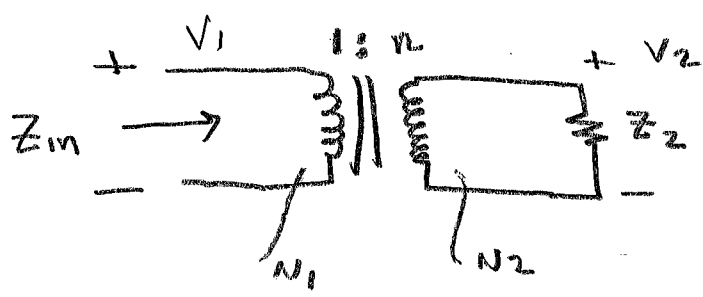We can develop a formula for reflected impedance



Since $V_2 = nV_1$ and $I_2 = \frac{I_1}{n}$


$$\downarrow$$

$$V_1 = \frac{V_2}{n} \quad I_1 = nI_2$$

$$\frac{V_1}{I_1} = Z_{in} = \frac{V_2/n}{nI_2} = \frac{V_2}{I_2} \times \frac{1}{n^2} = \frac{1}{n^2} Z_2$$

Sanity check:

14

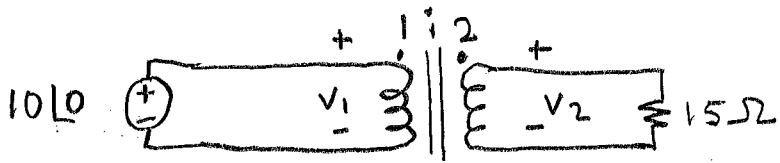

$$n = \frac{N_2}{N_1} = 2, \quad \frac{V_2}{V_1} = 2 \quad \text{so} \quad V_2 = 2 \times 10 = 20 \text{ V}$$

$$\text{So } I_2 = \frac{20 \text{ V}}{15 \Omega} = 1.33 \text{ A}, \quad P_2 = \frac{1}{2} I_2^2 \times 15 = 13.33 \text{ W}$$

$$Z_{pri} = \frac{Z_L}{n^2} = \frac{15}{2^2} = 3.75 \Omega$$

$$I_1 = \frac{10}{3.75} = 2.67 \text{ A}$$


$$\frac{I_2}{I_1} = \frac{1.33}{2.67} = \frac{1}{2} = \frac{1}{n}$$

checks

$$P_1 = \frac{1}{2} \frac{V_s^2}{Z_{pri}} = \frac{1}{2} \times \frac{10^2}{3.75} = 13.33 \text{ W}$$

checks


Find V_o

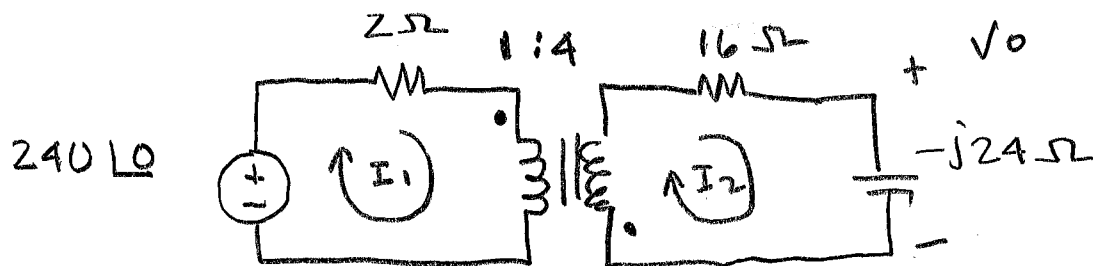

STRATEGY 1

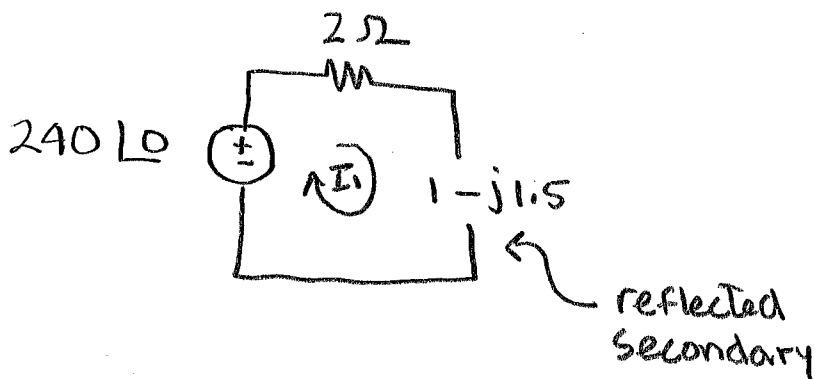- 1) Reflect load to transformer input
- 2) Compute current I_1
- 3) Use relationship $\frac{I_2}{I_1} = \frac{-1}{n}$ to get I_2 ↙ note dots
- 4) $V_o = I_2 Z_L = I_2 \times -j24$

Load is $16 - j24$, reflects to $\frac{16 - j24}{n^2} = \frac{16 - j24}{4^2} = 1 - j1.5 \Omega$



$$I_1 = \frac{240 \angle 0}{1 - j1.5 + 2} = 64 + j32 \text{ A}$$


Now reflect I_1 to I_2 , $I_2 = I_1 \times \frac{1}{n} = (64 + j32) \times \frac{1}{4}$
 $I_2 = -16 - j8$

and $V_o = I_2 \times Z_L = -(16 + j8) \times -j24 = 429.33 \angle 116.56 \text{ V}$

strategy 2

1) solve for mesh currents I_1, I_2

2) $V_o = I_2 Z_c$

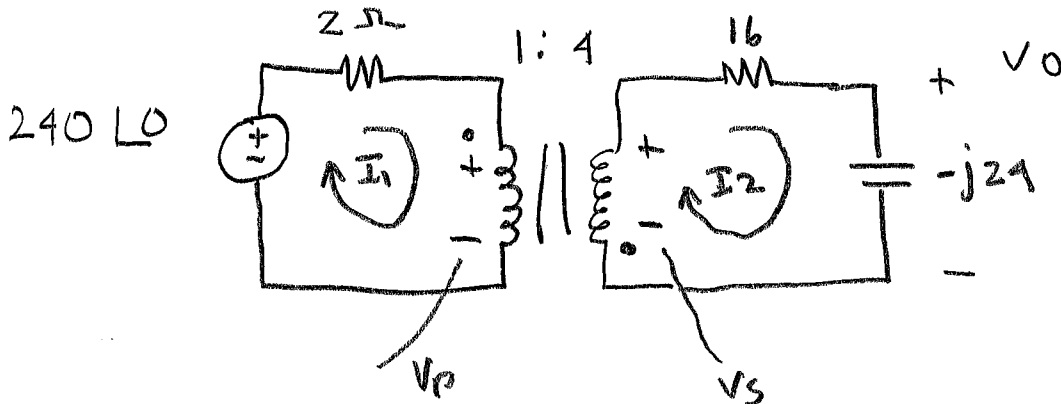

$$\begin{cases} \textcircled{1} -V_{in} + 2I_1 + V_p = 0 \\ \textcircled{2} -V_s + 16I_2 - j24I_2 = 0 \end{cases} \left. \begin{array}{l} 2 \text{ EQ} \\ \text{UNKNOWN S, } V_p, V_s, I_1, I_2 \end{array} \right\}$$

Notes that

watch that dot!

$$V_p = -\frac{V_s}{n} \quad \text{and} \quad I_1 = -nI_2$$

So

$$\textcircled{1} -V_{in} - 2nI_2 - \frac{V_s}{n} = 0 \rightarrow -2nI_2 - \frac{1}{n}V_s = V_{in}$$

$$\textcircled{2} -V_s + 16I_2 - j24I_2 = 0 \rightarrow (16 - j24)I_2 - V_s = 0$$

So


$$\begin{bmatrix} I_2 \\ V_s \end{bmatrix} = \begin{bmatrix} -2n & -1/n \\ 16 - j24 & -1 \end{bmatrix}^{-1} \begin{bmatrix} V_{in} \\ 0 \end{bmatrix} \quad \text{and} \quad I_2 = -16 - j8$$

Just like before.

$$\text{So } V_o = I_c \times Z_c = -(16 + j8) \times -j24 = 429.33 \angle 116.56^\circ$$


Practice problem 13.8 Strategy #3

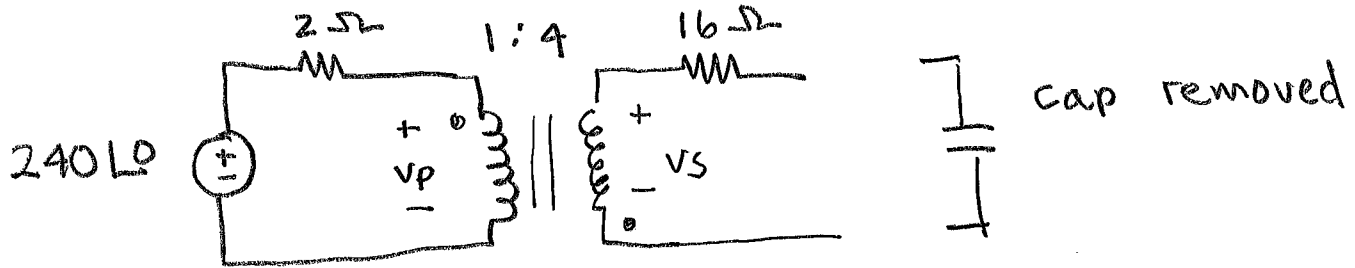- 1) Represent everything to the left of the capacitor as a Thevenin source
- 2) Load circuit with capacitor and use voltage divider




No current in primary or secondary so $V_p = 240V$
 $V_s = -n \times V_p = -4 \times 240 = -960V = V_{TH}$.

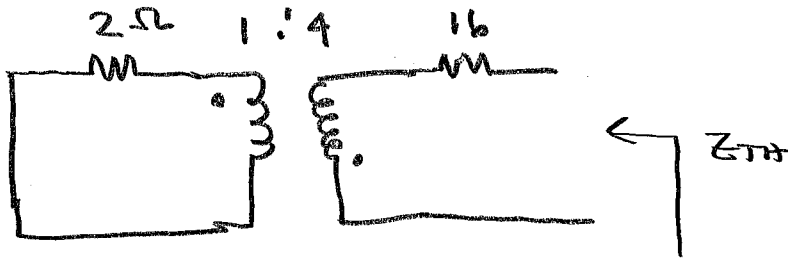Get Z_{TH} by shorting voltage source and measuring impedance looking into Thevenin source



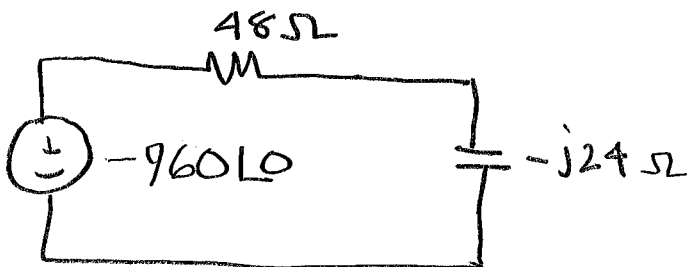
$$Z_{TH} = 16 + 2 \times n^2 = 16 + 2 \times 4^2 = 48\Omega$$



$$V_o = -960 \times \frac{-j24}{-j24 + 48}$$

$$= 429.33 \angle 116.56^\circ$$

EXAMPLE - ELECTRIC POWER DISSIPATION

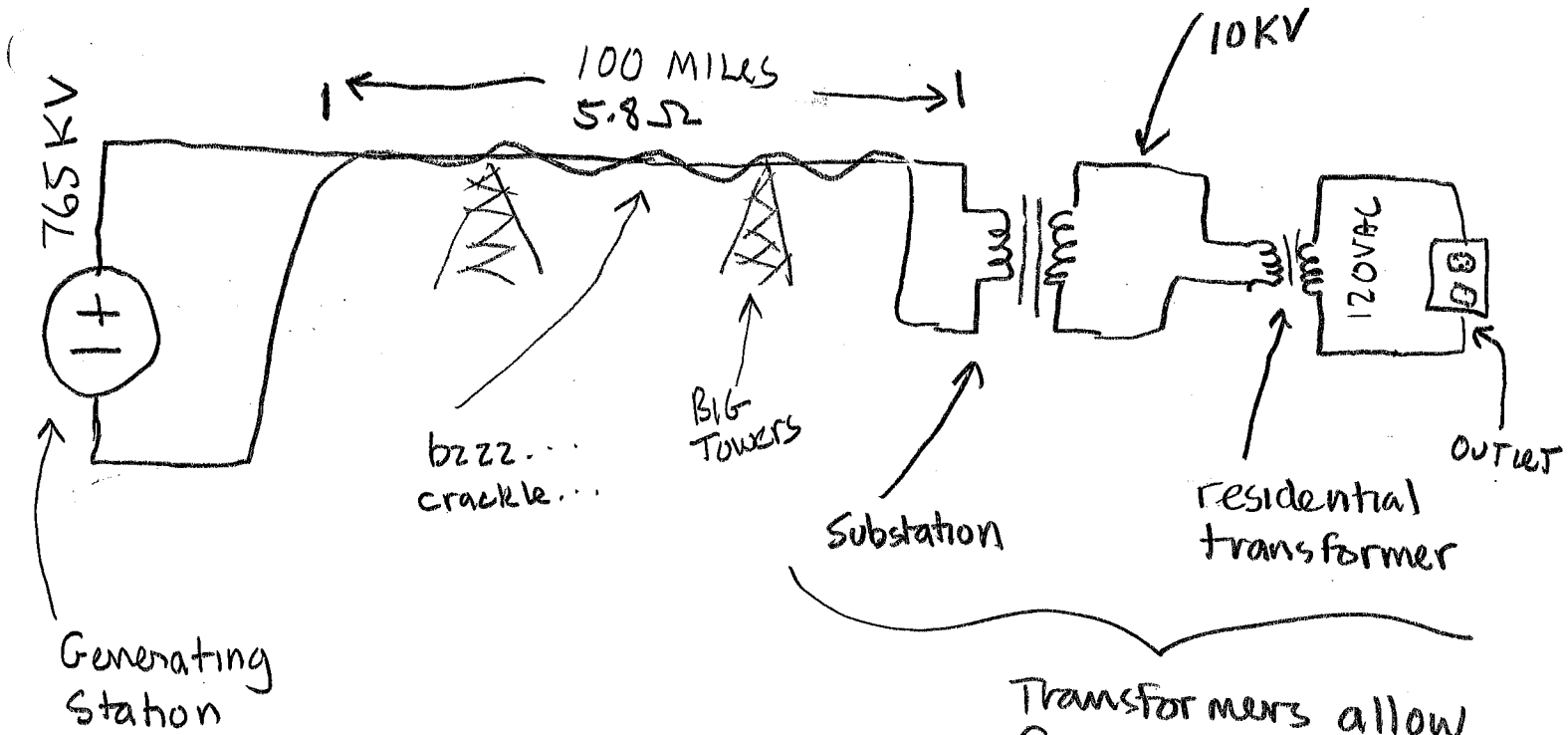

Substation transformer

$$\frac{V_2}{V_1} = \frac{10\text{KV}}{765\text{KV}} = \frac{N_2}{N_1} = \frac{1}{76.5}$$

residential transformer

$$\frac{V_2}{V_1} = \frac{120}{10,000} = \frac{1}{83}$$

Transformers allow easy voltage manipulation

Our system feeds half of San Diego,

Say 316,000 homes at 3.16 kW apiece.

That's 1×10^9 W or a GW

Distance from substation to consumer is insignificant compared to 100 mile transmission distance, so all losses are on 765 kV line.

$$\text{Current (765 kV Line)} = \frac{P}{V} = \frac{1 \text{ GW}}{765 \text{ kV}} = \underline{1307 \text{ A}}$$

$$\text{So loss in 765 kV Line} = I^2 R = 1307^2 \times 5.8 = \underline{9.9 \text{ MW}}$$

$$\text{and } \frac{P_{\text{WR Lost}}}{P_{\text{WR Generated}}} = \frac{9.9 \text{ MW}}{1 \text{ GW}} \times 100 = 1\%$$

Say we distributed at 100 kV, then


$$I = \frac{1 \text{ GW}}{100 \text{ kV}} = 10,000 \text{ A}$$

$$\text{Line Loss} = I^2 R = 10,000^2 \times 5.88 = 588 \text{ MW}$$

$$\text{and } \frac{P_{\text{WR Lost}}}{P_{\text{WR generated}}} = \frac{588 \text{ MW}}{1 \text{ GW}} = 59\%$$


Towers are expensive. This is why they're used

EXAMPLE - Maximum Power Transfer

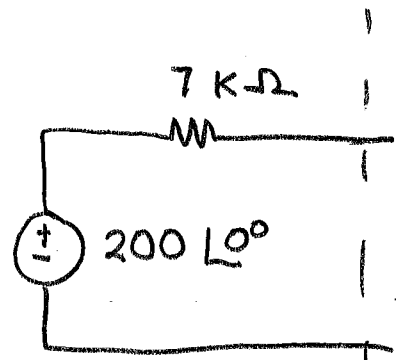

Thevenin Source


?

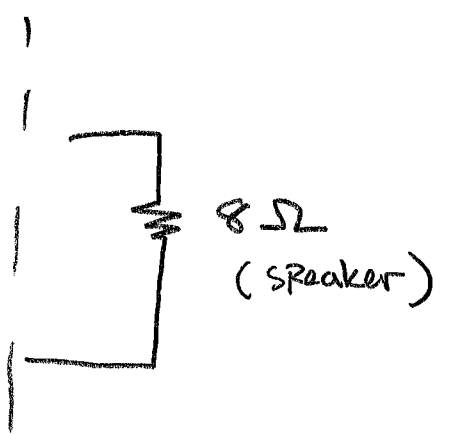

Load

In this problem we are given a source impedance and a load impedance and we need to design the "Matching Network"

Say we connect them with a transformer.

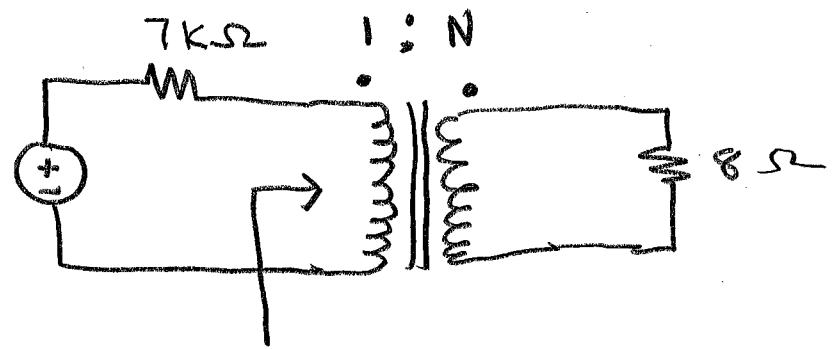

$$Z_{in} = \frac{8\Omega}{N^2}$$

To match we want $Z_{in} = 7k\Omega$ So

$$7k\Omega = \frac{8\Omega}{N^2} \quad \text{or} \quad N = 0.0338 = \frac{1}{29.5}$$