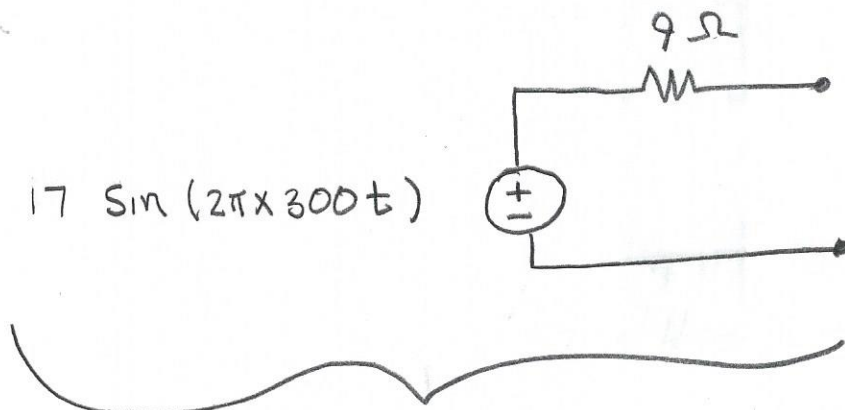



SUPPLEMENTAL PROBLEM - MAGNETIC CIRCUITS

DORR  
SPRING 2017

1/



You are given this source

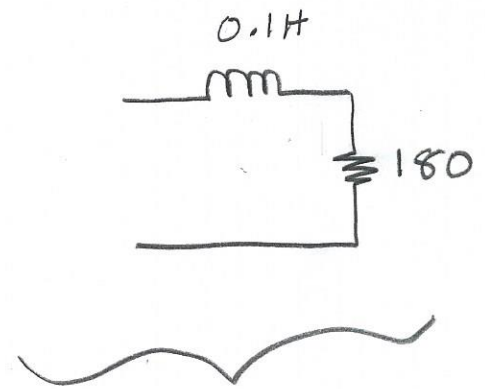


and this load

Use an ideal transformer and one additional component so the load receives maximum power from the source.

The additional component must be placed in series with the  $9\ \Omega$  source resistance. Additional component must be a capacitor or inductor. Find component value and turns ratio.

Hints


1) Here's your circuit:

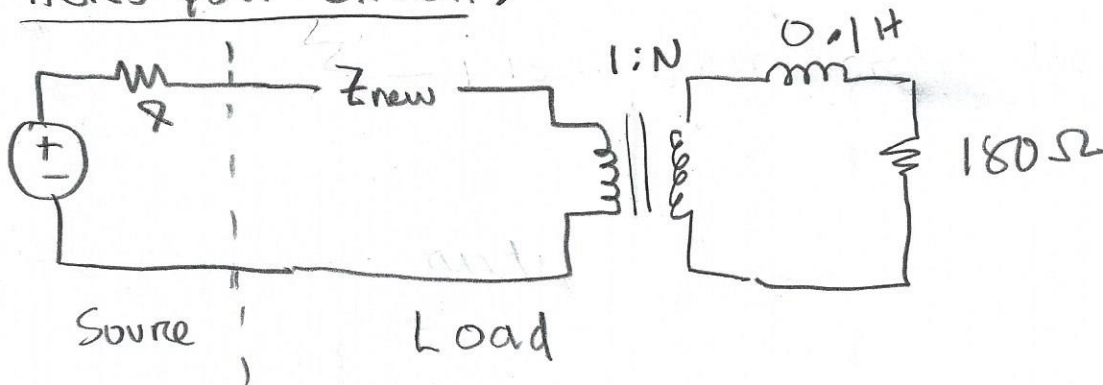

2) Compute turns ratio to match  $9\ \Omega$ , then find the reactive component.


3) The example on the next several pages shows how to do the problem for shunt components

# Example problem for sublement

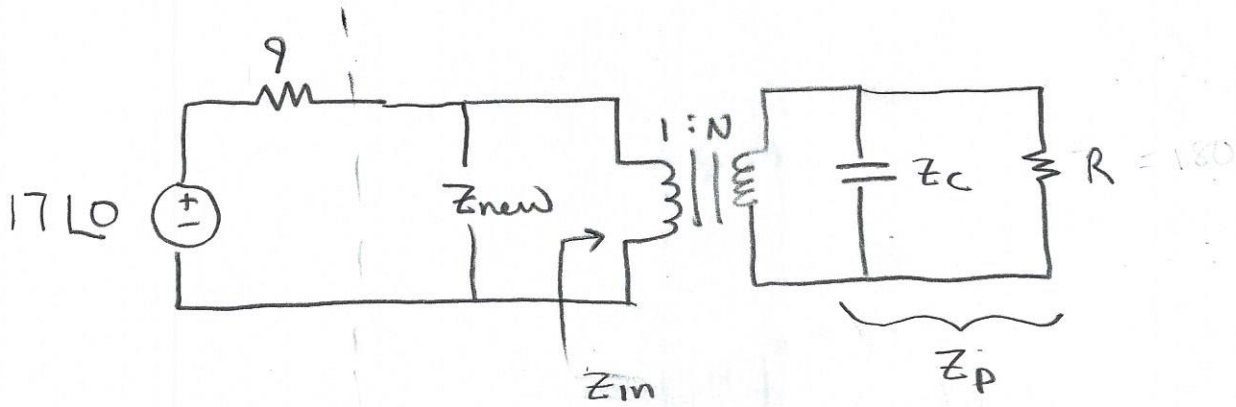


$$Z_p = \frac{Z_C Z_R}{Z_C + Z_R}$$

$$Z_{in} = \frac{Z_p}{n^2}$$

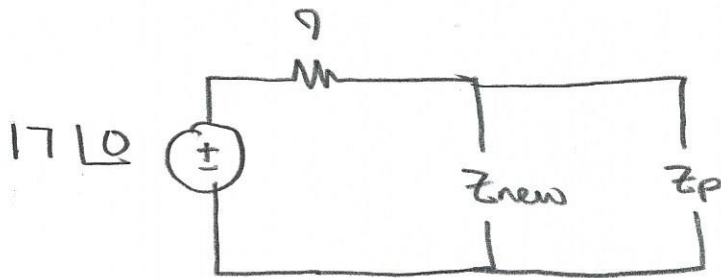

$$\begin{aligned} \frac{Z_p}{n^2} &= \frac{Z_C Z_R}{Z_C + Z_R} \times \frac{1}{n^2} = \frac{\frac{Z_C}{n^2} \times \frac{Z_R}{n^2}}{\frac{Z_C}{n^2} + \frac{Z_R}{n^2}} = \frac{Z_C Z_R \times \frac{1}{n^4}}{Z_C + Z_R \times \frac{1}{n^2}} \\ &= \frac{Z_C Z_R}{Z_C + Z_R} \times \frac{1}{n^2} \end{aligned}$$

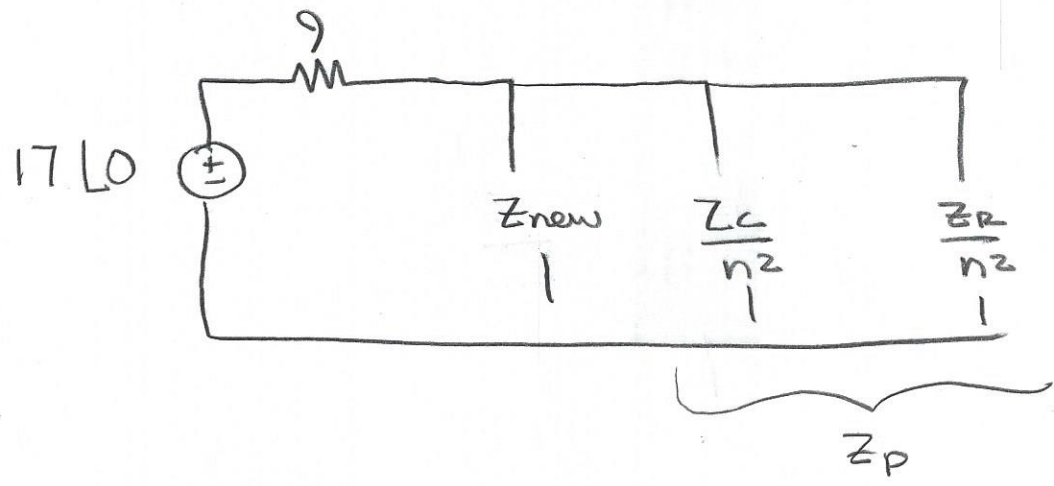So I can represent reflected impedance as shown on the next page



So strategy is to set  $n^2$  so  $\frac{Z_R}{n^2} = 9$

Then set  $Z_{new}$  so  $Z_{new} \parallel \frac{Z_c}{n^2} = \infty$

$$n = \sqrt{\frac{Z_R}{9}} = \sqrt{\frac{R}{9}}$$

$$\text{so } \frac{Z_c}{n^2} = \frac{Z_c}{R/9} = \frac{9Z_c}{R}$$


and  $Z_{new} \parallel \frac{9Z_c}{R} = \infty$

$$\frac{Z_{new} \times \frac{9Z_c}{R}}{Z_{new} + \frac{9Z_c}{R}} = \infty \text{ so } Z_{new} + \frac{9Z_c}{R} = 0$$

or  $Z_{new} = -\frac{9Z_c}{R}$
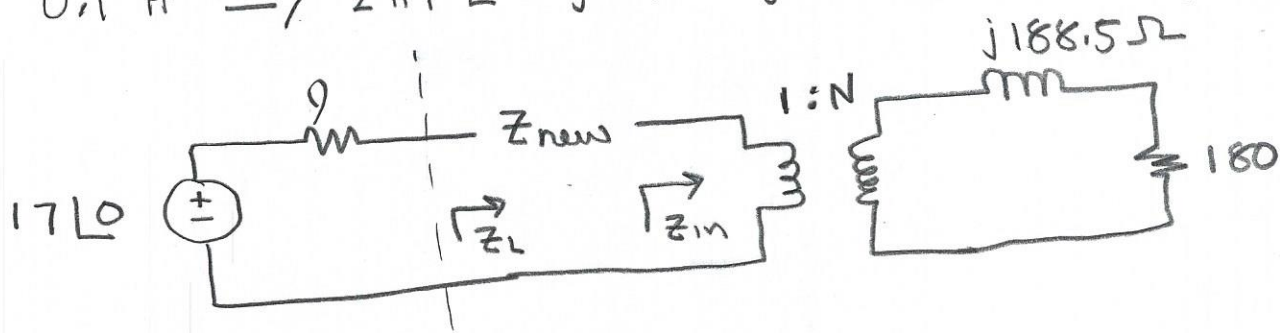
# SUPPLEMENTAL PROBLEM SOLUTION MAGNETIC CIRCUITS

$$0.1 \text{ H} \Rightarrow Z_{\pi} F L = j \omega L = j 2\pi \cdot 300 \times 0.1 = j 188.5 \Omega$$




Reflect load to primary

$$Z_{\text{in}} = \frac{Z_L}{n^2} = \frac{180 + j188.5}{n^2}$$

Set  $n$  so  $\text{Re}(Z_{\text{in}}) = 9 \Omega$  or  $\frac{180}{n^2} = 9 \therefore n = 4.47$

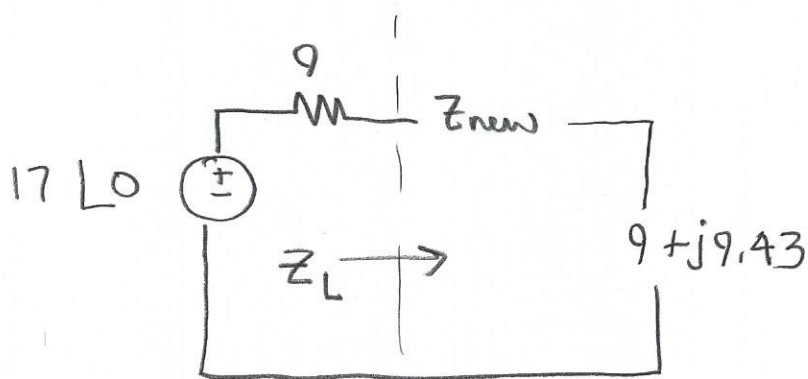Now  $Z_{\text{in}} = \frac{180 + j188.5}{4.47^2} = 9 + j9.43$



so for  $Z_L = Z_{\text{in}}^*$ ,  $Z_L = 9$

so  $Z_{\text{new}} + 9 + j9.43 = 9$  or  $Z_{\text{new}} = -j9.43 \Omega$

$Z_{new}$  must be a capacitor because  $Z_{new} = -j9.43$

$$Z_c = -j9.43 = \frac{1}{j2\pi \times 300 \cdot C}$$

$$C = \frac{1}{2\pi \times 300 \times 9.43} = 56.25 \mu\text{f}$$

