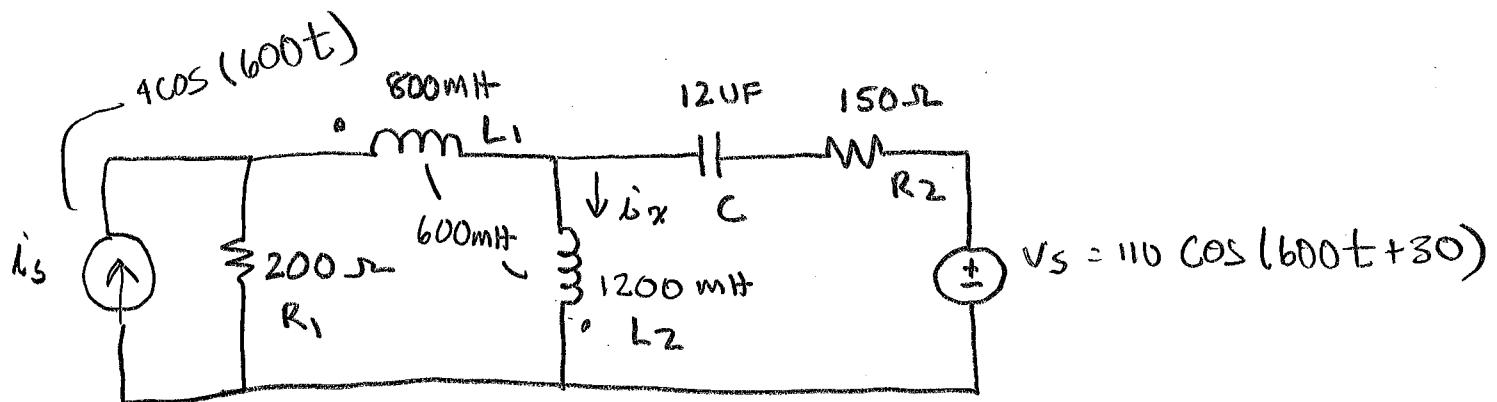


LECTURE 15 - FUN WITH TRANSFORMERS

L1

(3.11)

Find i_x Using mesh analysis




The coils are coupling, but a lot or just a bit?

We know $M \leq \sqrt{L_1 L_2}$ FQ 13.35

and

$$K = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.6}{\sqrt{0.8 \times 1.2}} = 0.6124$$

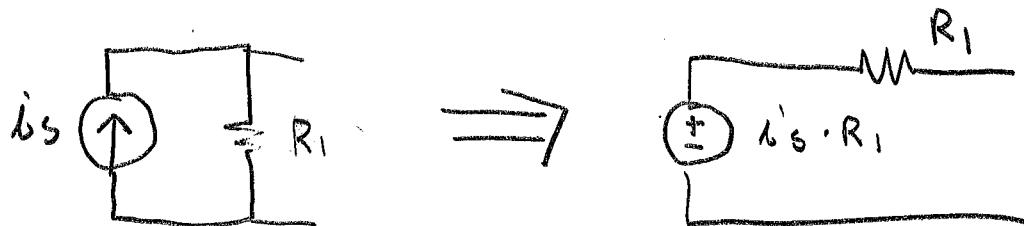for mesh analysis we'll use source transformation



$i_s = 4 \cos(600t)$ → What is Freq in Hz?

a - 600 Hz


b - 3769 Hz

c - none of the above


PR 13.11 CONT


[2]

JWM($I_2 - I_1$)

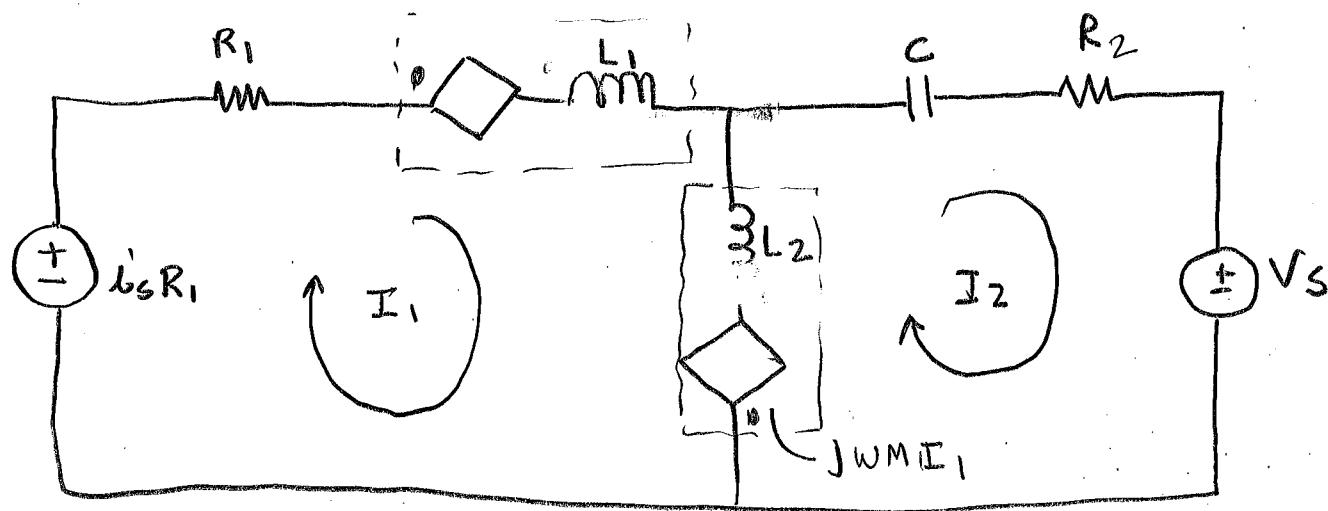

"It is ... time to vote"

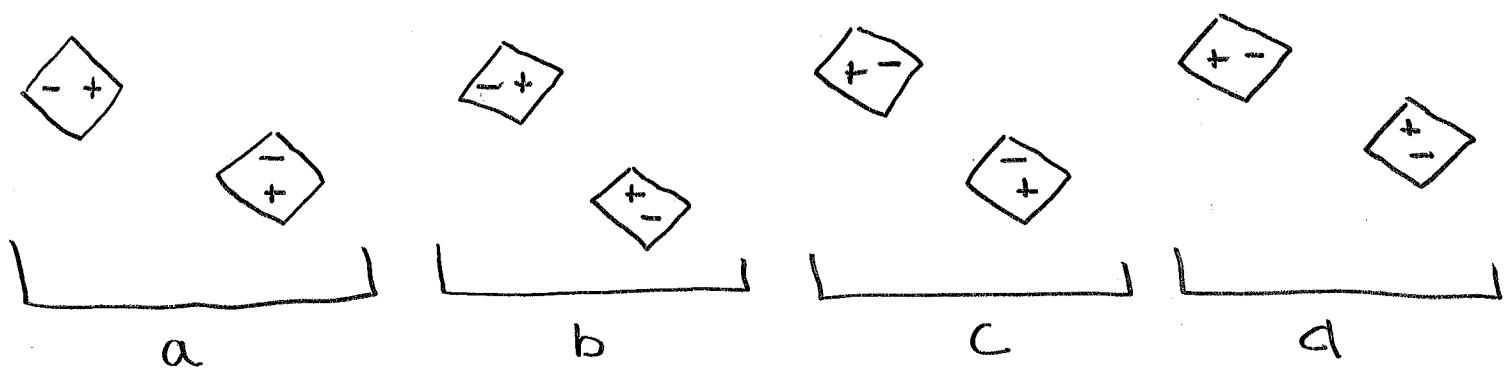

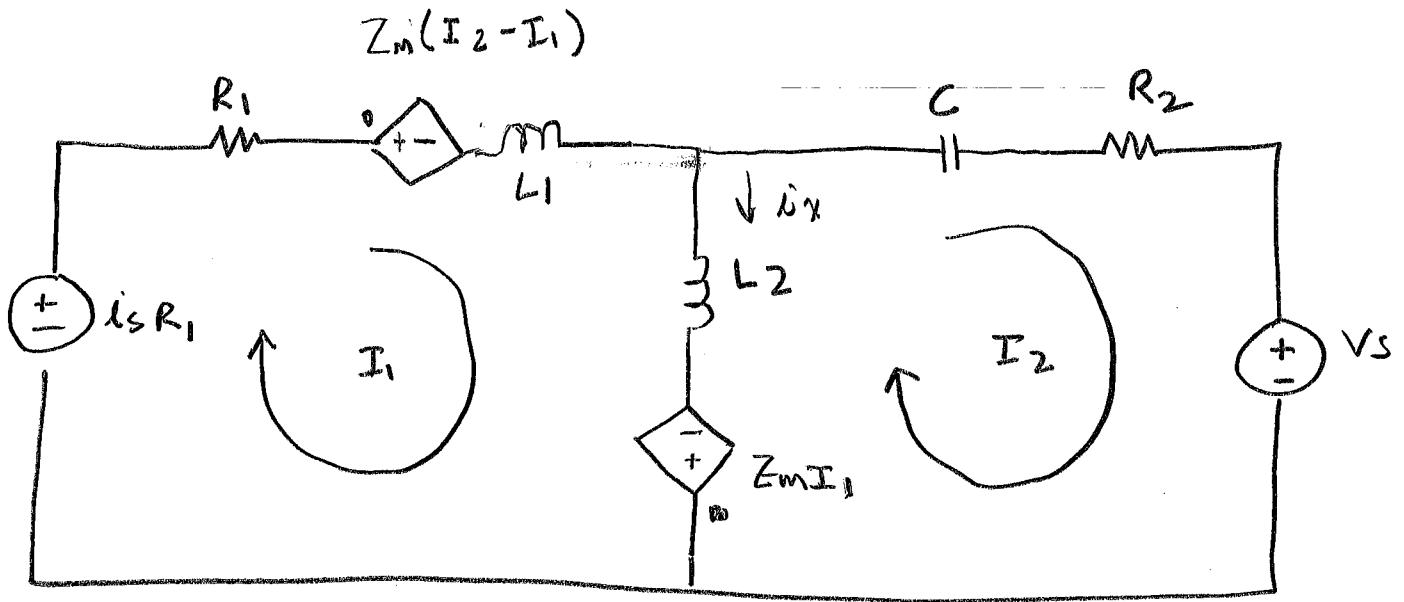

$$\textcircled{1} \quad -I_s R_1 + I_1 R_1 + Z_m (I_2 - I_1) + Z_{L1} I_1 + Z_{L2} (I_1 - I_2) - Z_m I_1 = 0$$

$$I_1 (R_1 - Z_m + Z_{L1} + Z_{L2} - Z_m) + I_2 (Z_m - Z_{L2}) = I_s R_1$$

$$\textcircled{2} \quad Z_m I_1 + (I_2 - I_1) Z_{L2} + I_2 Z_C + I_2 R_2 + V_s = 0$$


$$I_1 (Z_m - Z_{L2}) + I_2 (Z_{L2} + Z_C + R_2) = -V_s$$

$$\begin{bmatrix} R_1 - Z_m + Z_{L1} + Z_{L2} - Z_m & Z_m - Z_{L2} \\ Z_m - Z_{L2} & Z_{L2} + Z_C + R_2 \end{bmatrix}^{-1} \begin{bmatrix} I_s R_1 \\ -V_s \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$\text{and } I_x = I_1 - I_2 = 1.07 \cos(600t - 66^\circ)$$

I disagree with answer in back of book

14

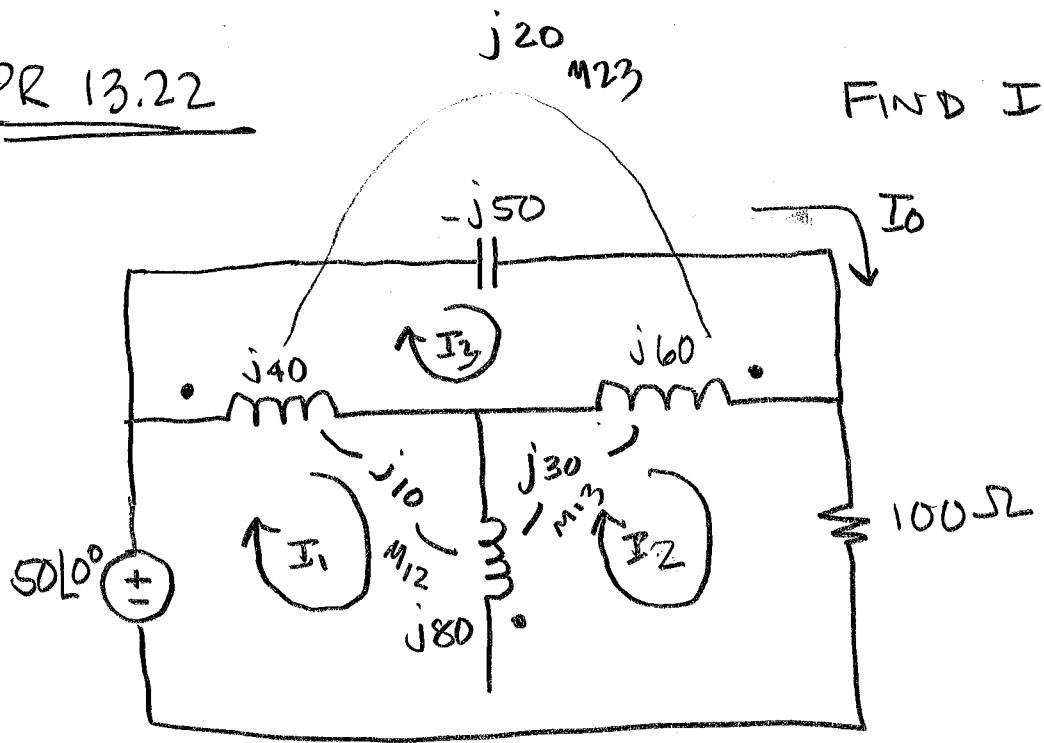PR 13.22FIND I_0 

"Bridged - T" network

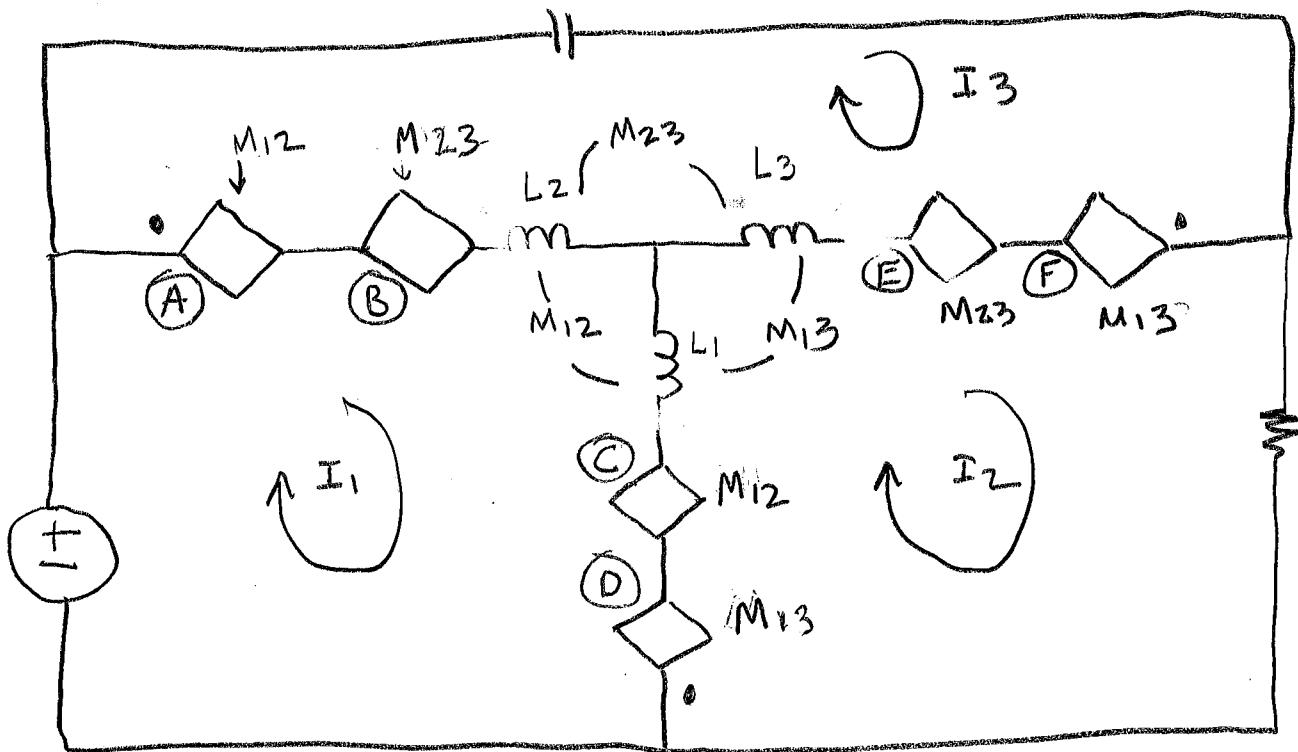

Make current entry dot of "donor" positive

$$\textcircled{A} \rightarrow S M_{12} (I_2 - I_1)$$

$$\textcircled{B} \rightarrow S M_{23} (I_3 - I_2)$$

$$\textcircled{C} \rightarrow S M_{12} (I_1 - I_3)$$

$$\textcircled{D} \rightarrow S M_{13} (I_3 - I_2)$$


$$\textcircled{E} \rightarrow S M_{23} (I_1 - I_3)$$

$$\textcircled{F} \rightarrow S M_{13} (I_2 - I_1)$$

FILL IN THE POLARITY ON THE SOURCES

Practical Problem

16


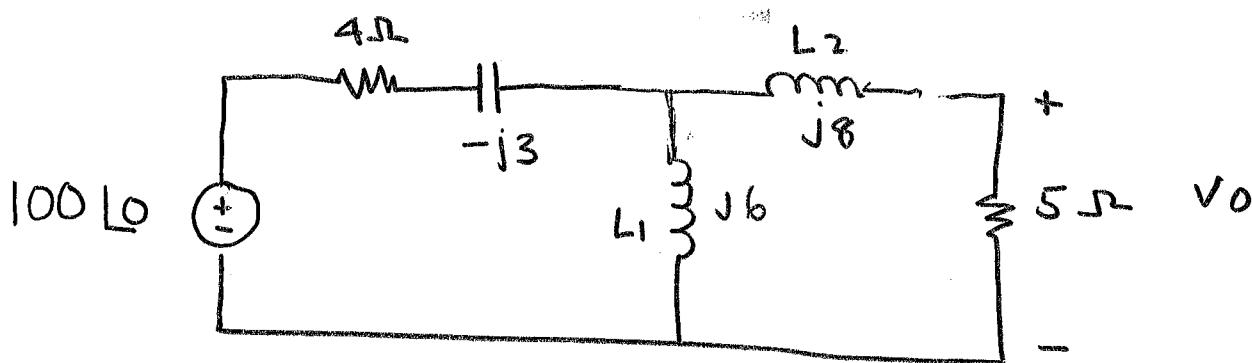


- 1) "There is no mutual inductance." Compute V_0 (design value)
- 2) Measure the output voltage. See if it equals the design value.
- 4) If the output voltage doesn't match the design value, compute the mutual inductance.

Strategy

- 1) Look at the circuit. Hypothesize where dots are
- 2) Compute the expected output with $M = 0$.
This is the design value.
- 3) Measure the output voltage
- 4) Adjust M in equations until we match the measured voltage

L7

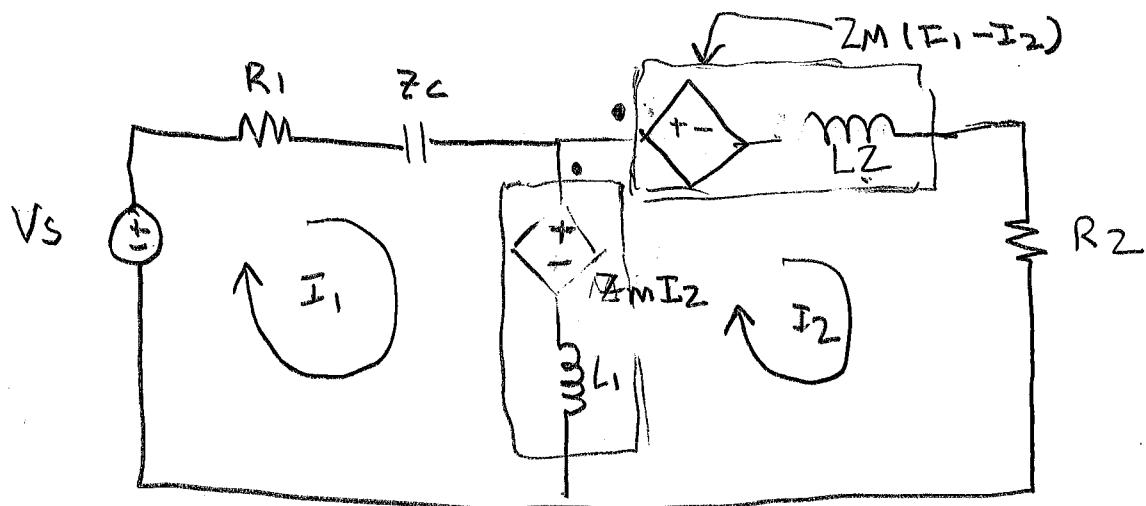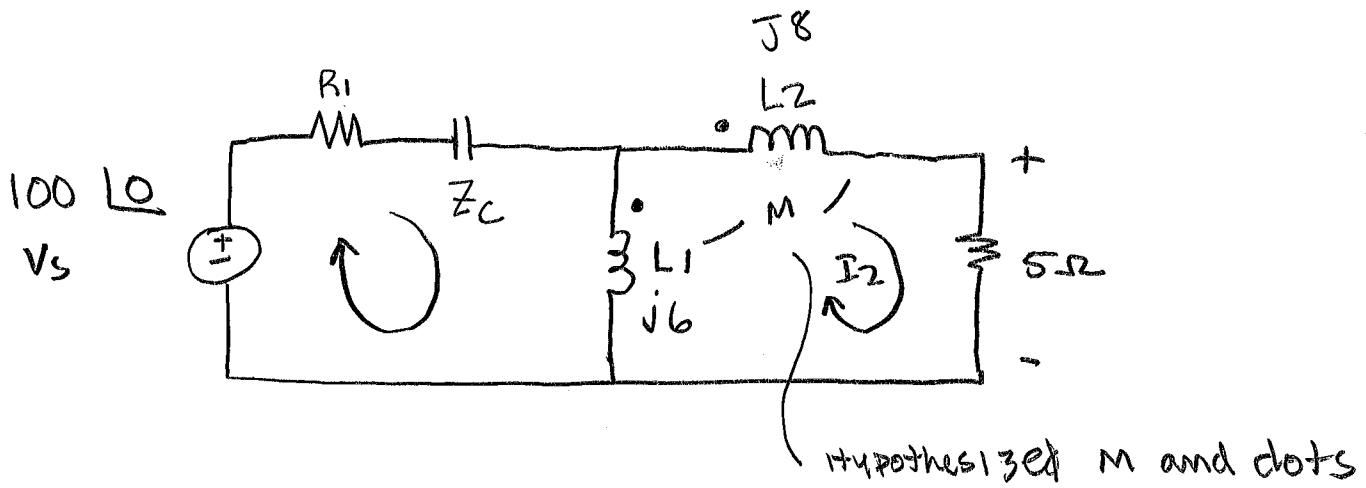

I_2 enters dot of L_2 so it makes dot of L_1 more positive

I_1 enters dot of L_1 so it makes dot of L_2 more positive

note $(I_1 - I_2) Z_M$ for L_2

$$\textcircled{1} \quad -V_s + R_1 I_1 + Z_C I_1 + Z_M I_2 + (I_1 - I_2) Z_{L1} = 0$$

$$I_1 (R_1 + Z_C + Z_{L1}) + I_2 (+Z_M - Z_{L1}) = V_s$$

$$\textcircled{2} \quad (I_2 - I_1) Z_{L1} - Z_M I_2 + I_2 Z_{L2} + Z_M (I_1 - I_2) + I_2 R_2 = 0$$

$$I_1 (-Z_{L1} + Z_M) + I_2 (Z_{L1} - Z_M + Z_{L2} - Z_M + R_2) = 0$$

$$\begin{bmatrix} R_1 + Z_C + Z_{L1} & +Z_M - Z_{L1} \\ -Z_{L1} + Z_M & Z_{L1} - Z_M + Z_{L2} - Z_M + R_2 \end{bmatrix}^{-1} \begin{bmatrix} V_s \\ 0 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


WITH $Z_M = 0$, NO COUPLING

$$V_o = I_2 R_2 = (8.134 + j1.60) \times 5$$

$$40.67 + j8.02$$

$$41.45 \angle 11.15^\circ$$

MEASURE WAVEFORMS BELOW.

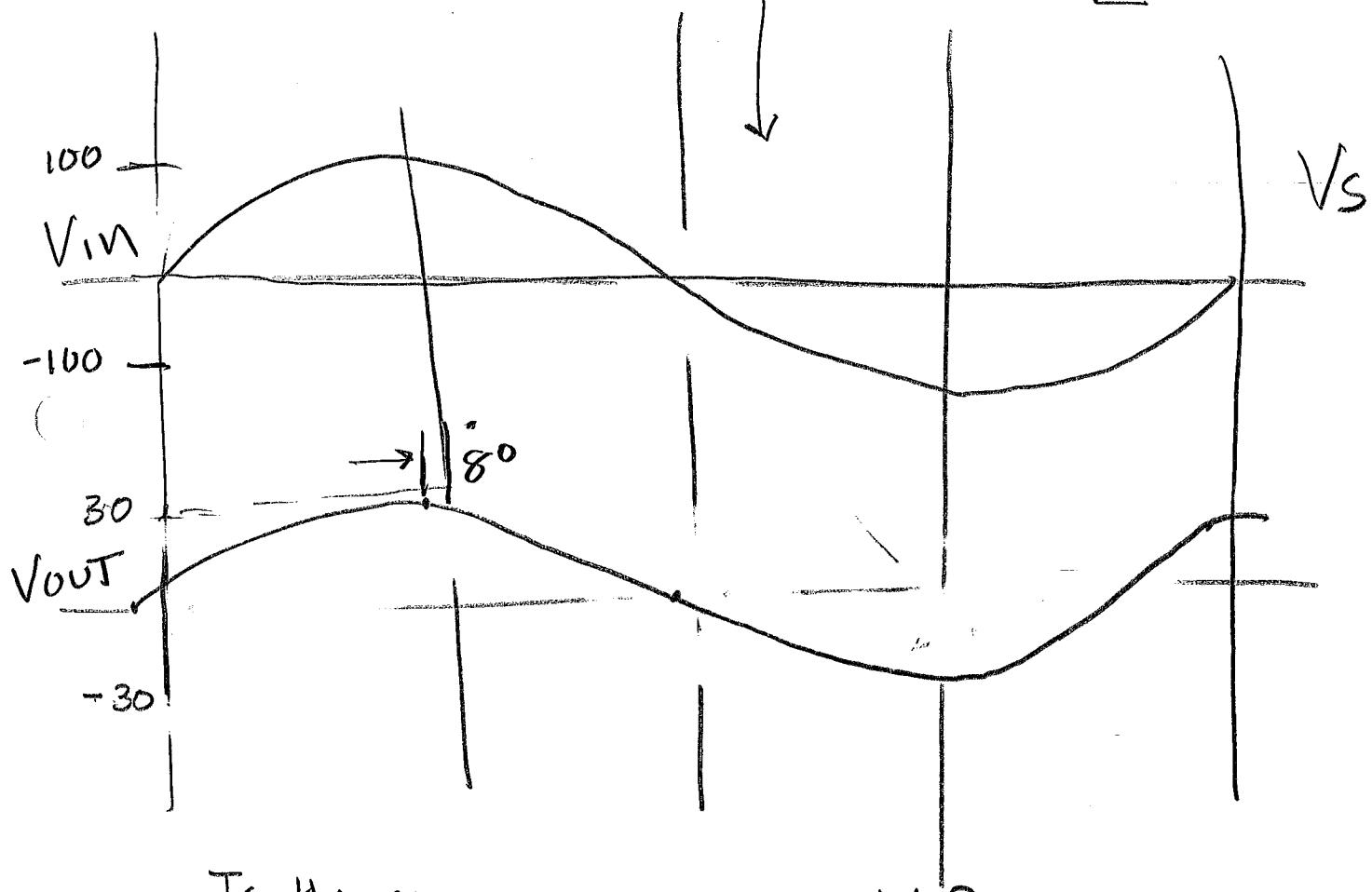

Is the CIRCUIT working right?

18

So what do we do?

(1) remove the components and measure them

- They are ok

2) Hypothesize MUTUAL COUPLING.

- Note desired phase was 11.150° , we got about 8°
That's pretty hard to measure.

- But we expected Amplitude of 41 and we
got about 27. That's easy to see.

ZM	Vol	L Phone
j1	39.3	8.10°
j2	36.1	6.2°
j3	31.7	6.07°
j4	25.34	8.740°
j3.77	27.04	7.79°

Too far

Matches what we saw

can I do this?


$$K = \text{Coefficient} = \frac{M}{\sqrt{L_1 L_2}} \stackrel{?}{=} \frac{jWM}{\sqrt{jWL_1 \cdot jWL_2}}$$

Yes


$$= \frac{jWM}{\sqrt{-jW^2 L_1 L_2}} = \frac{jWM}{jW \sqrt{L_1 L_2}} = \frac{M}{\sqrt{L_1 L_2}}$$

110

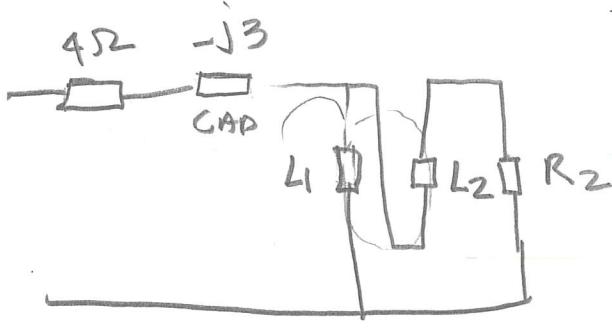
$$\text{so } K = \frac{j 3.77}{\sqrt{j 6 \times j 8}} = \underline{0.5442}$$



Found this layout

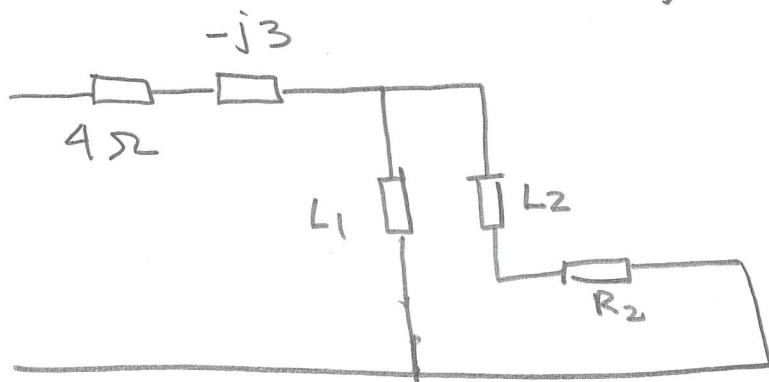


What will this do?

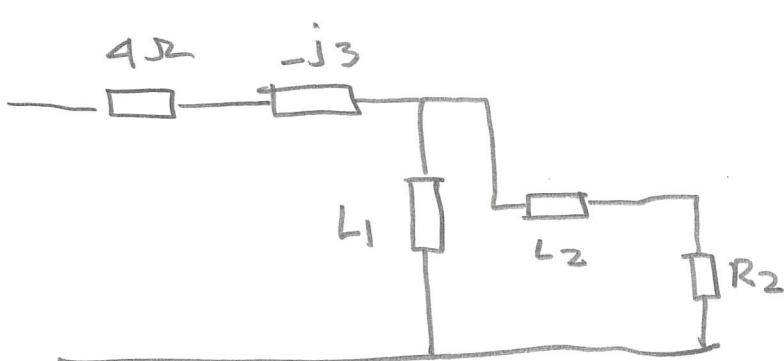

Fixed it!

10½

Center Tapped Transformer

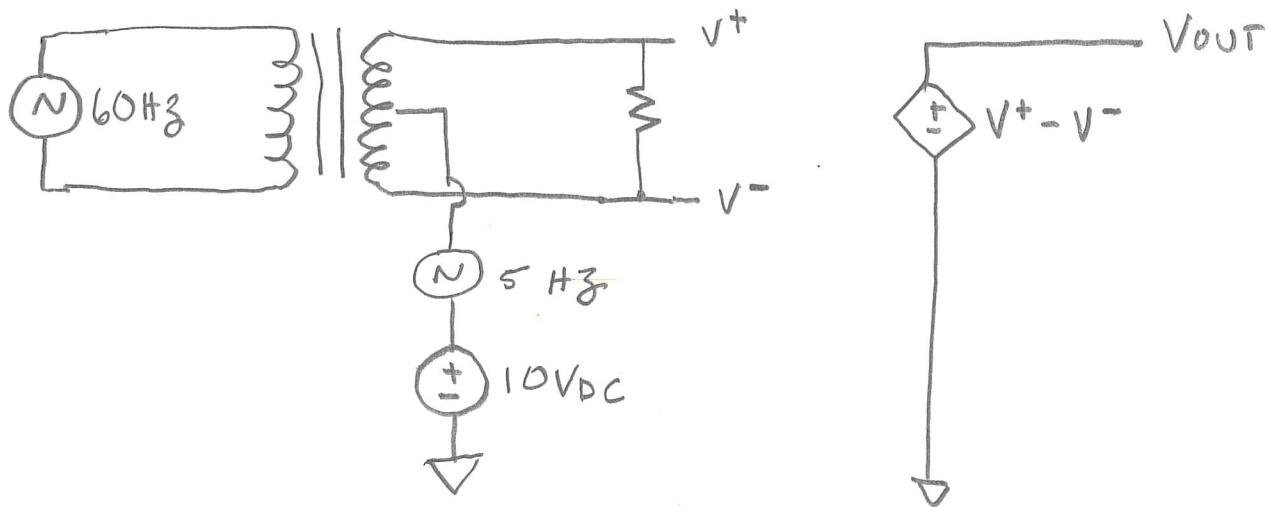


LONGITUDINAL TRANSFORMERS

11


FIND

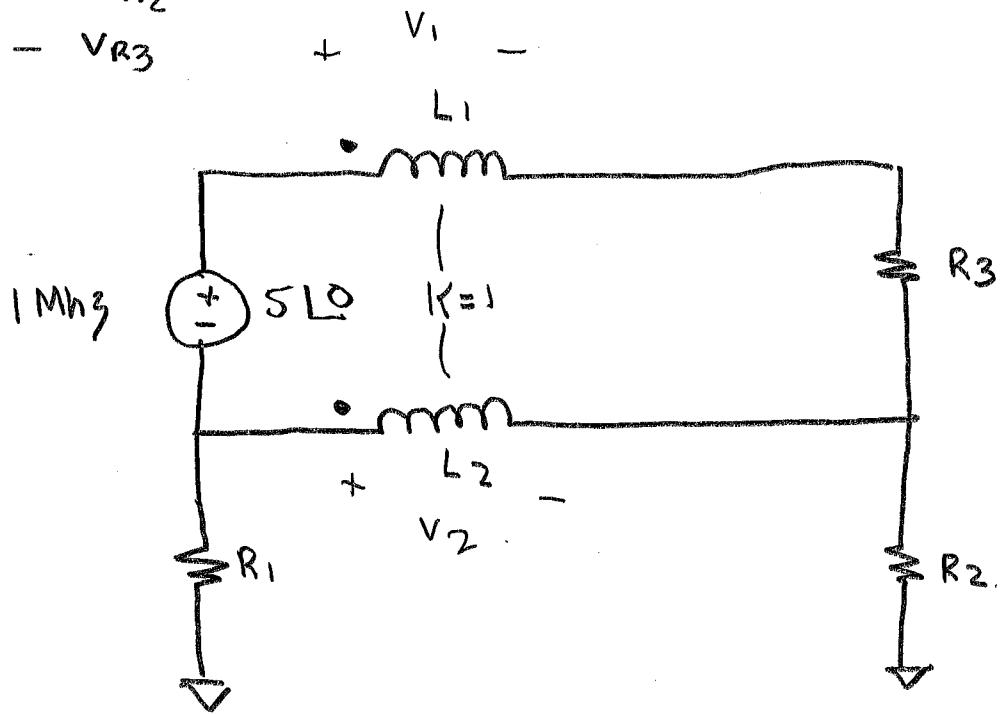- V_1
- V_2
- I_{R_1}
- I_{R_2}
- V_{R_3}



LONGITUDINAL TRANSFORMER - CONT

L12

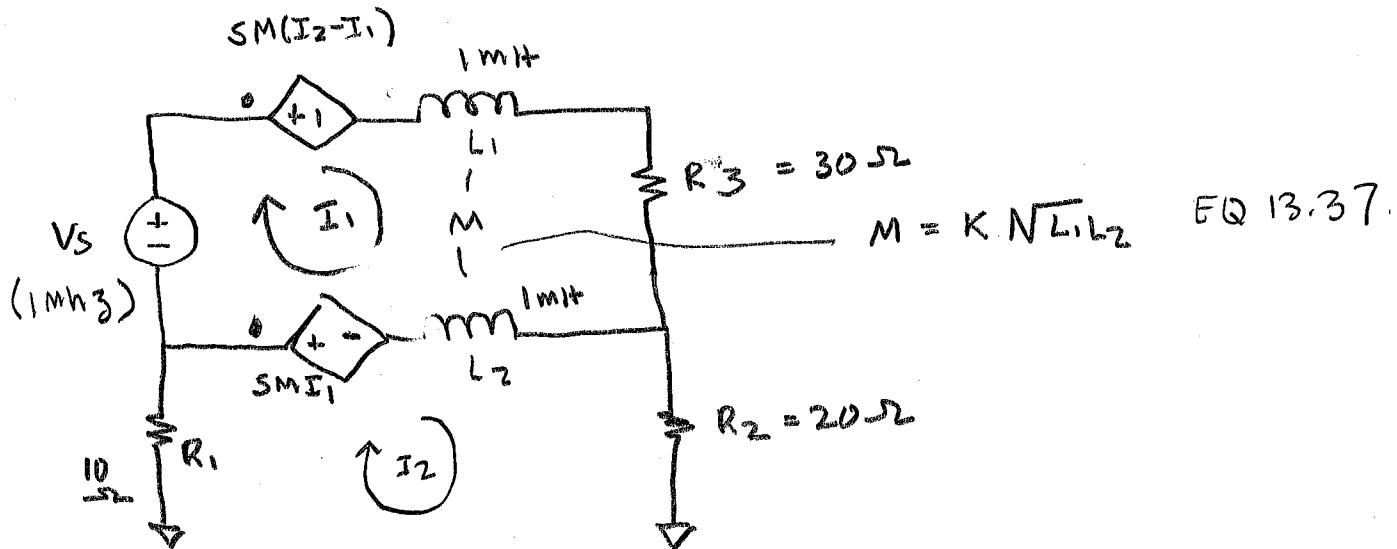

- ① $-V_s + SM(I_2 - I_1) + SL_1 I_1 + R_3 I_1 + SL_2(I_1 - I_2) - SMI_1 = 0$
- ② $-V_s + SMI_2 - SMI_1 + SL_1 I_1 + I_1 R_3 + SL_2 I_1 - SL_2 I_2 - SMI_1 = 0$
- ③ $(-SM + SL_1 + R_3 + SL_2 - SM) I_1 + (SM - SL_2) I_2 = V_s$
- ④ $I_2 R_1 + SMI_1 + SL_2(I_2 - I_1) + I_2 R_2 = 0$
- ⑤ $(SM - SL_2) I_1 + (R_1 + SL_2 + R_2) I_2 = 0$

Substitute values - $S = j2\pi \times 1\text{MHz}$, $R_1 = 10\Omega$, $R_2 = 20\Omega$, $R_3 = 30\Omega$, $L_1 = L_2 = 1\text{mH}$.

$$\begin{bmatrix} -SM + SL_1 + R_3 + SL_2 - SM \\ SM - SL_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

Say $L_1 = L_2 = 1\text{mH}$, $K = 1$ Then $I_1 = 167\text{ mA}$, $I_2 = 0$

$$V_{L1} = SM(I_2 - I_1) + SL_1 I_1 = 0$$

$$V_{L2} = SMI_1 + SL_2(I_2 - I_1) = 0$$

$$V_{R3} = R_3 \times I_1 = 5V \rightarrow \text{Hey, that's } V_s$$

$$V_{R2} = I_2 R_2 = 0, V_{R1} = I_2 R_1 = 0$$

In the previous example we note that

1) $K = 1$

2) Impedance of inductors $= j2\pi f L = j6.28 K \Omega$
is much larger than the resistances.


Can we use ideal transformer model?

We have L_1 and L_2 , what is turns ratio N ?

See top of pg 574
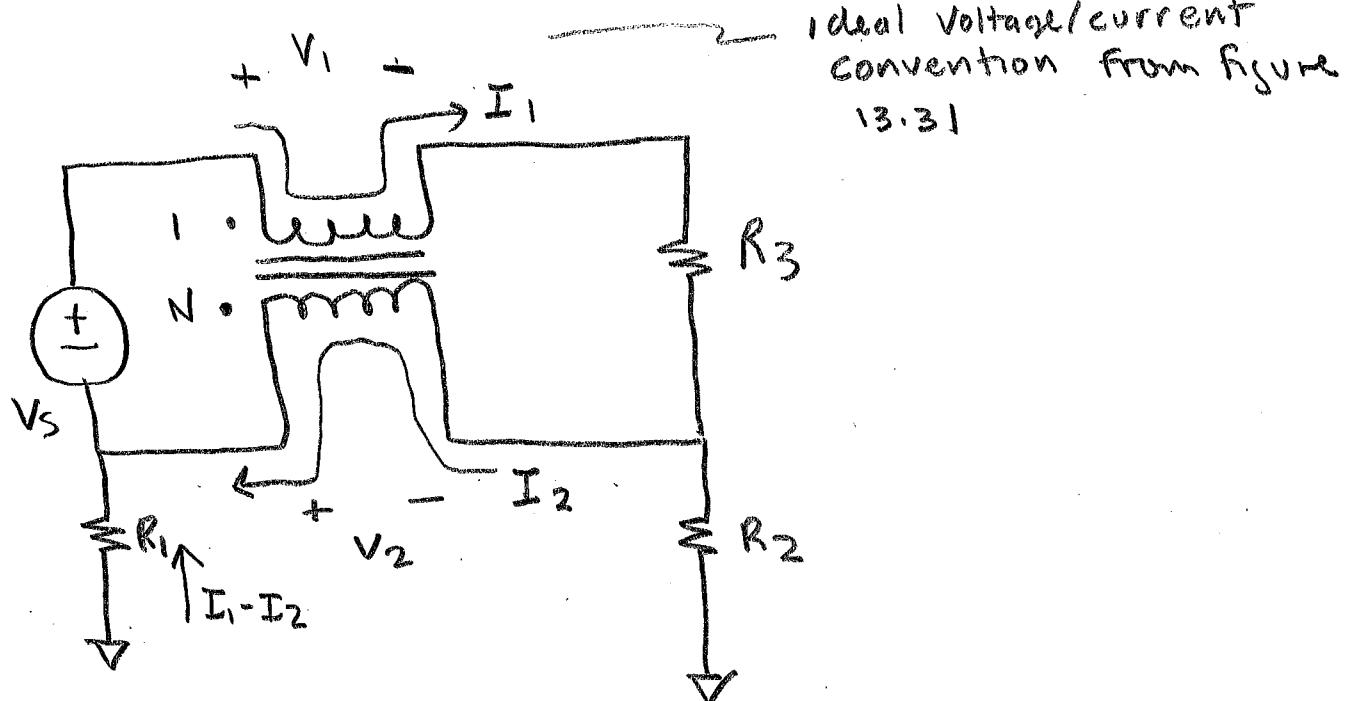
$$n = \sqrt{\frac{L_2}{L_1}} = \sqrt{\frac{1mH}{1mH}} = 1.0$$





① upper mesh

$$-Vs + V_1 + I_1 R_3 - V_2 = 0$$

② lower mesh

$$(I_1 - I_2) R_1 + V_2 + (I_1 - I_2) R_2 = 0$$

} 2 Eqs 4 unknowns

Ideal transformer: $V_2 = N V_1$, $I_2 = I_1 / N$

Since $N = 1$, $I_1 = I_2$


Therefore by KCL, $I_{R_1} = I_{R_2} = 0$

This is called a "Common Mode choice"

V_s is seen at R_3 regardless of the values of R_1 and R_2 !

Professor Dorr's secret notes for problem 13.22

A

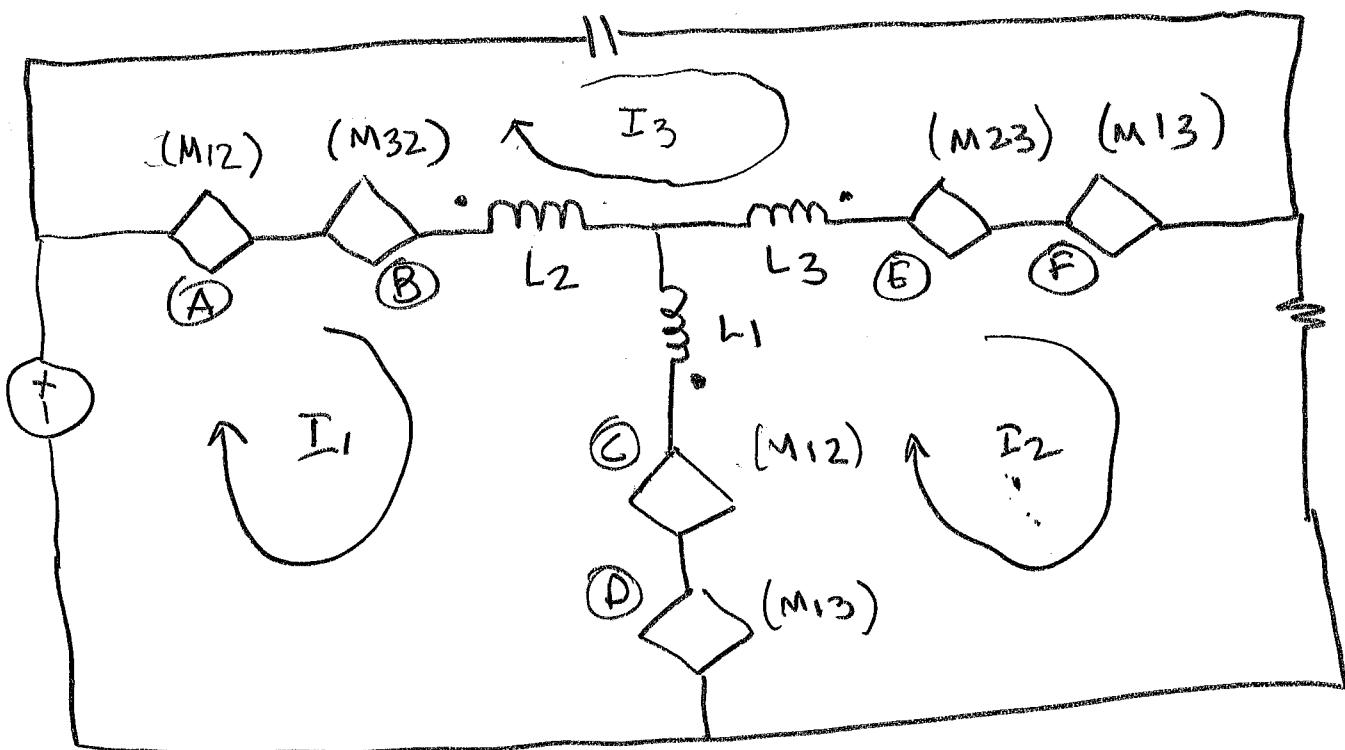

\checkmark I define current so it enters dot

(A) $\rightarrow I_{L1} = I_2 - I_1$, I_2 makes dot of L_2 more pos

$$\begin{array}{c} + \\ - \end{array} \quad S M_{12}(I_2 - I_1)$$

(B) $\rightarrow I_{L3} = I_3 - I_2$, I_3 makes dot of L_2 more positive

$$\begin{array}{c} + \\ - \end{array} \quad S M_{32}(I_3 - I_2)$$

(C) $\rightarrow I_{L2} = I_1 - I_3$, I_1 makes dot of L_1 more pos

$$\begin{array}{c} - \\ + \end{array} \quad S M_{12}(I_1 - I_3)$$

Professor Dorr's secret notes

LB

(D) $I_{L3} = I_3 - I_2$ I_3 makes dot of L_1 more pos

so

$$\begin{array}{c} - \\ + \end{array} \rightarrow SM_{13}(I_3 - I_2)$$

(E) $I_{L2} = I_1 - I_3$, I_1 makes dot of L_3 more pos


$$\begin{array}{c} - \\ + \end{array} \rightarrow SM_{23}(I_1 - I_3)$$

(F) $I_{L1} = I_2 - I_1$, I_2 makes dot of L_1 more pos

$$\begin{array}{c} - \\ + \end{array} \rightarrow SM_{13}(I_2 - I_1)$$

Professor Dorr's Secret Notes

10

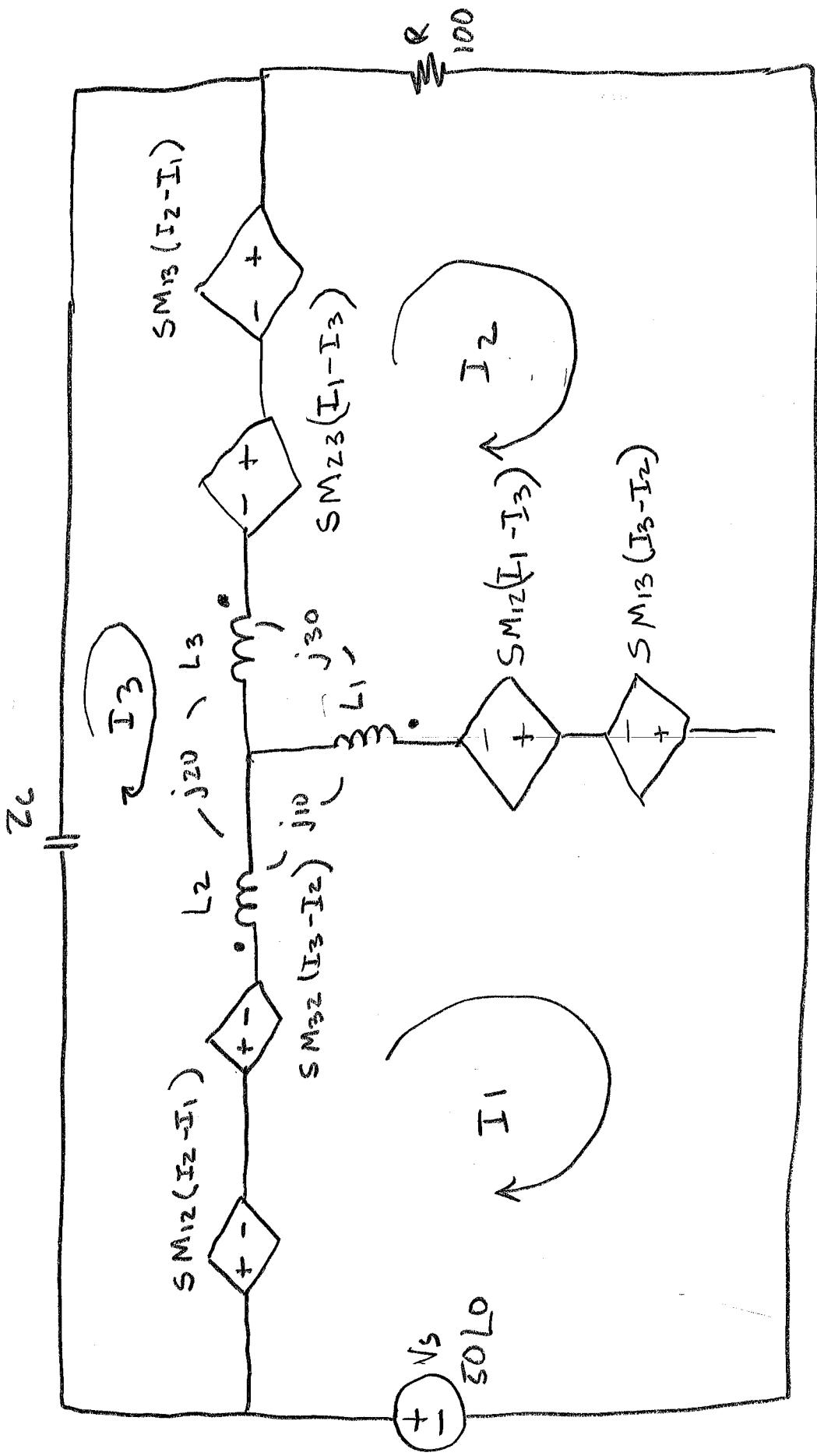

Professor Dorri's Secret notes

LD

(1)

$$-V_s + Z_{12}(I_2 - I_1) + Z_{32}(I_3 - I_2) + Z_{12}(I_1 + Z_{L1}(I_1 - I_2) - Z_{12}I_1 - Z_{12}(I_3 - I_2)) - Z_{12}I_3 = 0$$

$$I_1(-Z_{12} + Z_{L2} + Z_{L1} - Z_{12}) + I_2(Z_{12} - Z_{32} - Z_{L1} + Z_{13}) + I_3(Z_{32} - Z_{12}) - Z_{12}I_3 = V_s$$

(2)

$$Z_{13}(I_3 - I_2) + Z_{12}I_1 + Z_{L1}(I_2 - I_1) + Z_{L3}(I_2 - I_3) - Z_{23}I_1 - Z_{13}(I_2 - I_1) + I_2R + Z_{23}I_3 = 0$$

$$I_1(Z_{12} - Z_{L1} - Z_{23} + Z_{13}) + I_2(-Z_{13} + Z_{L1} + Z_{L3} - Z_{13} + R) + I_3(Z_{13} - Z_{L3}) - Z_{12} + Z_{23} = 0$$

(3)

$$(I_3 - I_1)Z_{12} - Z_{32}(I_3 - I_2) - Z_{12}(I_2 - I_1) + I_3Z_C + Z_{13}(I_2 - I_1) + Z_{23}I_1 - Z_{23}I_3 + (I_3 - I_2)Z_{L3} = 0$$

$$I_1(-Z_{L2} + Z_{12} - Z_{13} + Z_{23}) + I_2(Z_{52} - Z_{12} + Z_{13} - Z_{L3}) + I_3(Z_{L2} - Z_{32} + Z_C + Z_{L3}) - Z_{23} = 0$$

SOLVING GIVES

$$I_1 = 0.1885 + j0.143$$

$$I_2 = -0.0808 + j0.2962$$

$$I_3 = 0.5923 + j1.1615 = I_0 = 1.30 \quad \underline{62.980}$$