
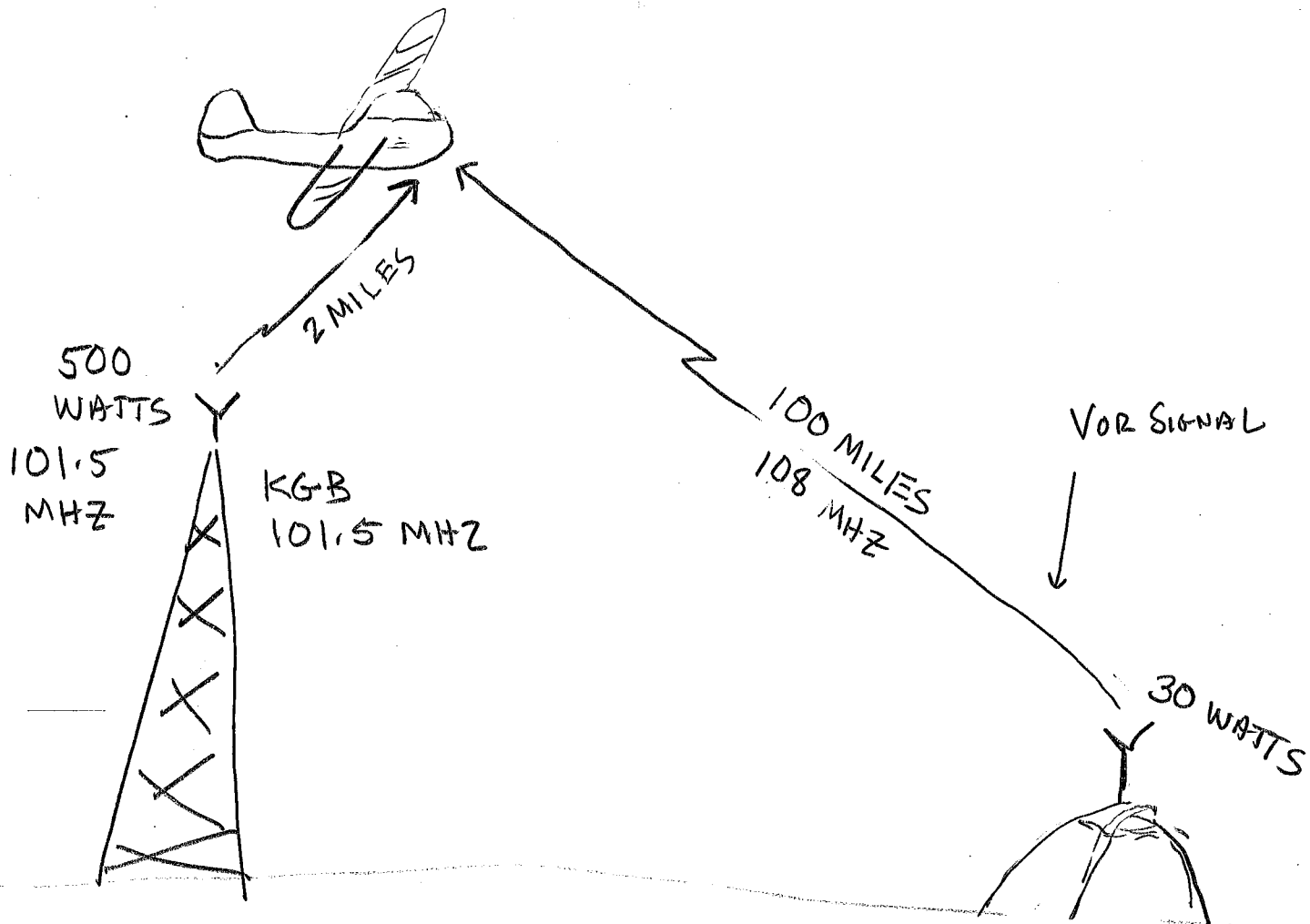


LECTURE 16 - INTRODUCTION TO FREQUENCY RESPONSE


L1

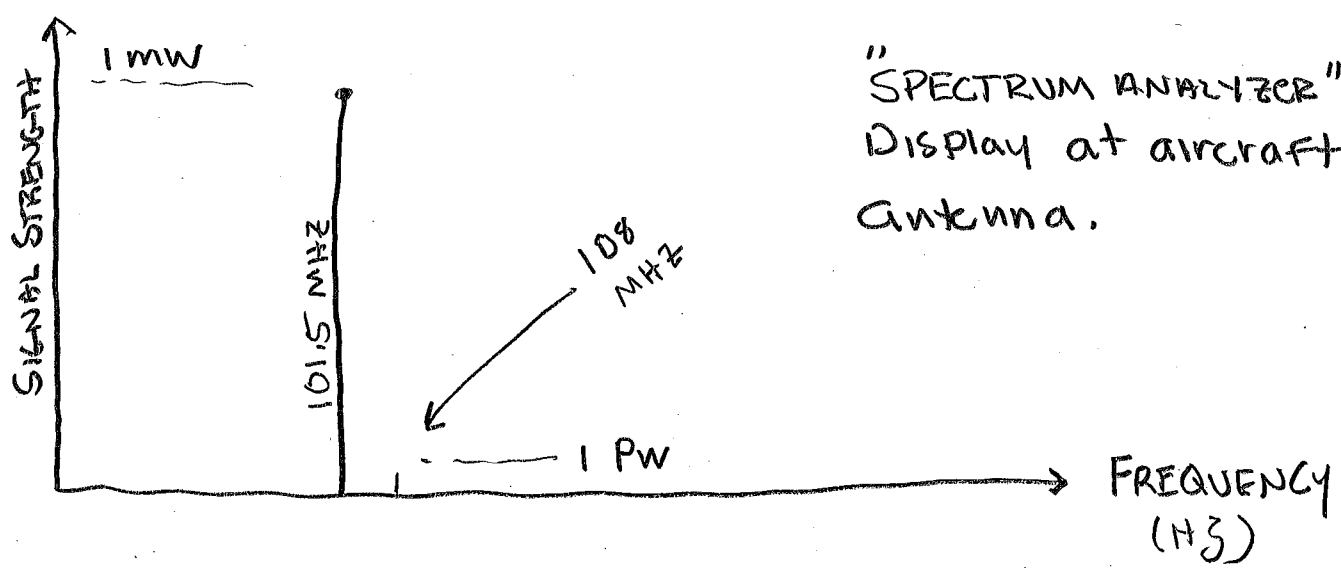



Why does KGB Get to OUTPUT 500 W and Air traffic Control only get to OUTPUT 30 W ??



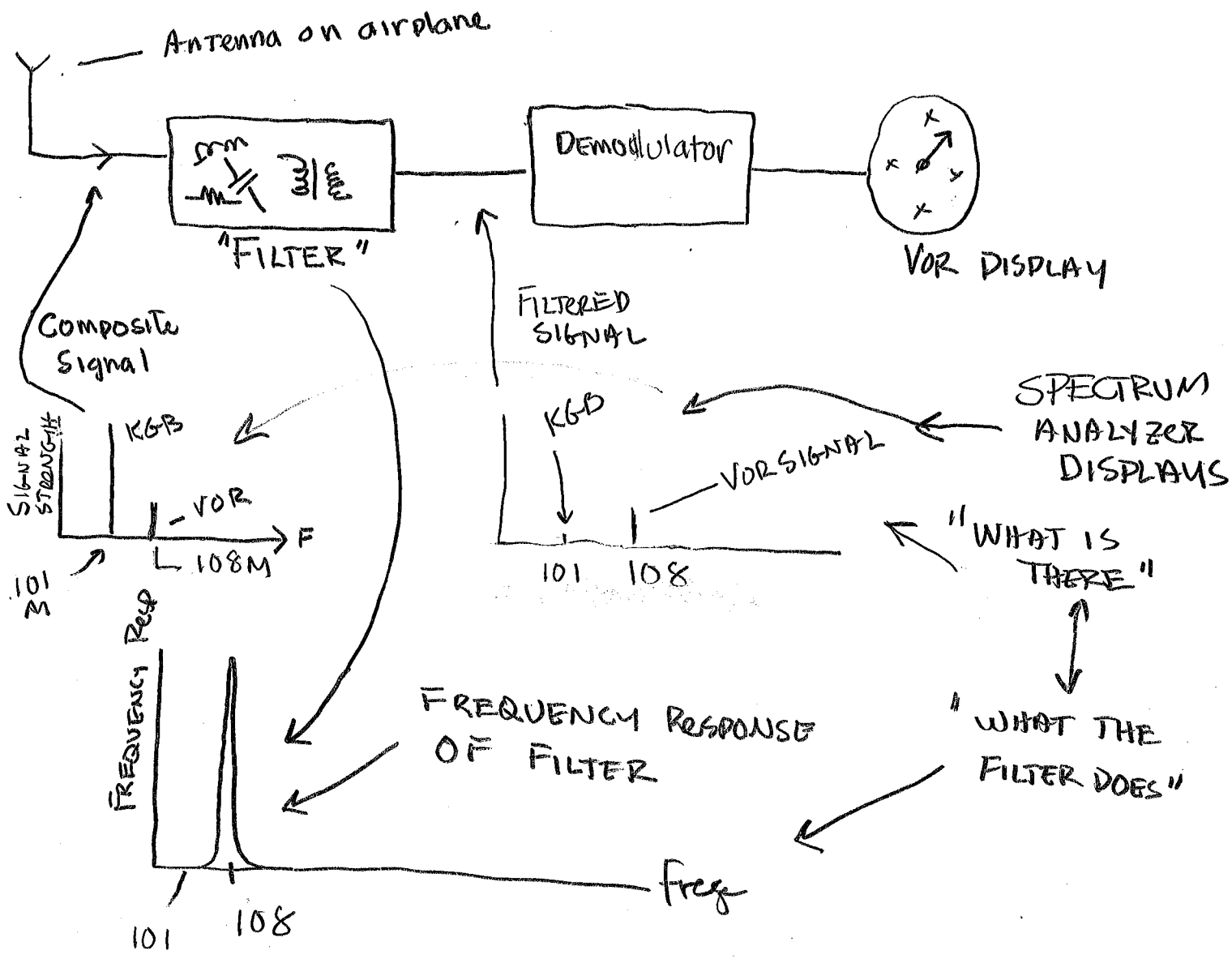$\frac{1 \text{ mw}}{1 \text{ pw}} = 10^9$ — That's a billion times more power!



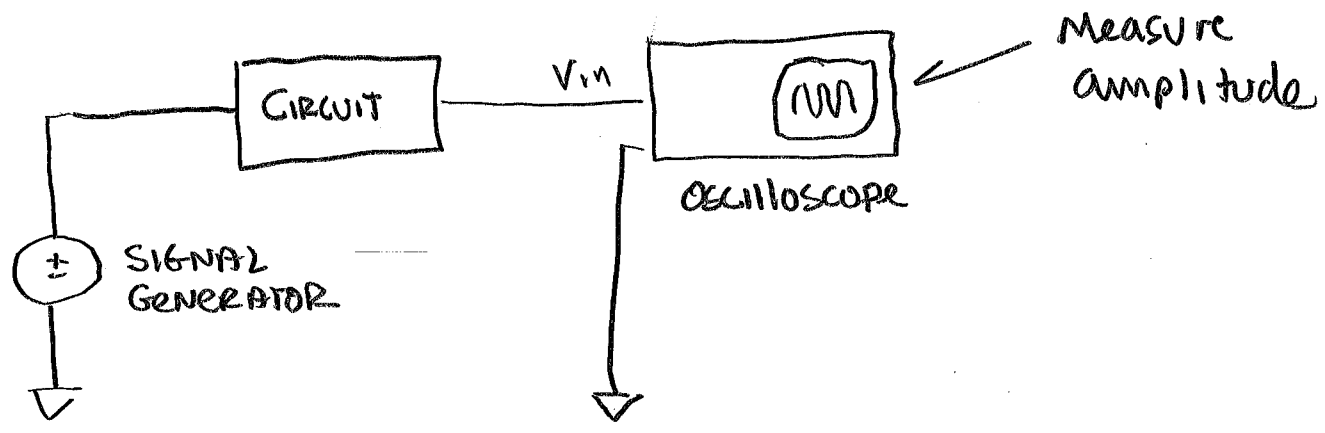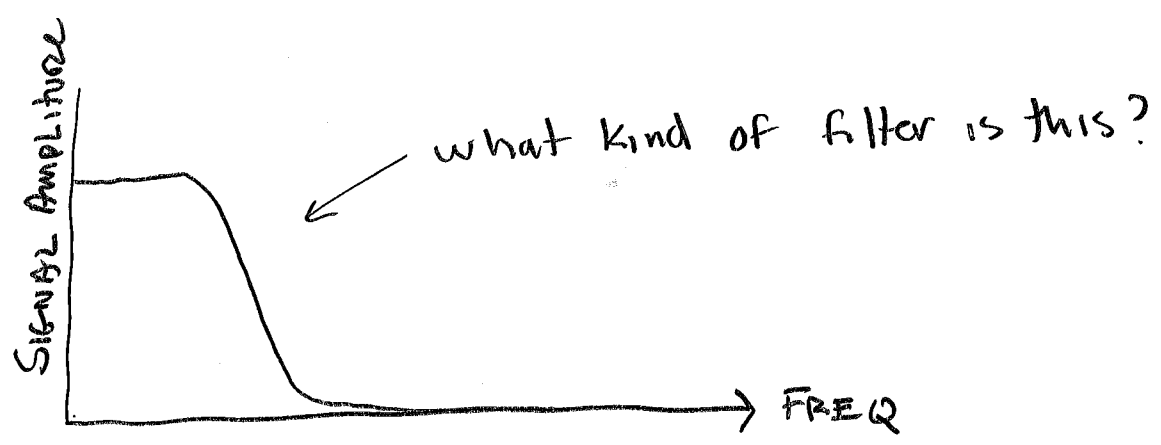
The filter eliminates the interferer. The filter is described by its "Frequency Response"



- Keep input level constant, Vary Frequency
- Measure amplitude with oscilloscope.
- Impedance of inductors and capacitors changes with frequency, what would you expect?

From pg 614

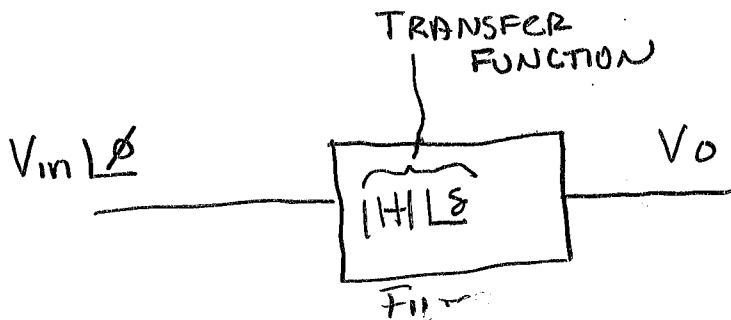" The Transfer Function $H(\omega)$ of a circuit is the frequency-dependent ratio of a phasor output, $Y(\omega)$ (an element voltage or current) to a phasor input $X(\omega)$ (source voltage or current)."



$$V_o = V_{in} \angle \phi \times |H| \angle \delta = V_{in} \cdot H \angle \phi + \delta$$

Connect to tnu's and boings

$$r(t) = A e^{(-\alpha + j\omega)t} = A e^{-\alpha t} e^{j\omega t}$$


For sinusoidal steady state, $\alpha = 0$ so

$$r(t) = A e^{j\omega t} = A e^{st} \quad \text{where } s = j\omega$$


Goodbye $j\omega$... It's s now!

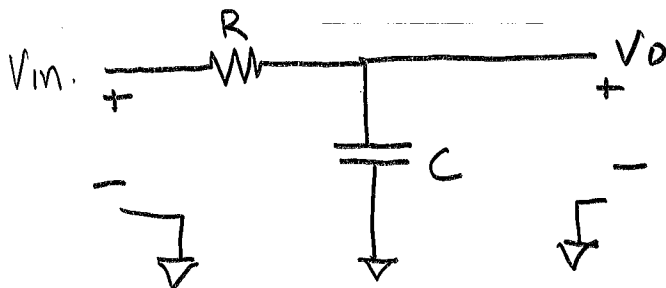Example 14.1 Pg 615


Find transfer function and frequency response of the RC circuit.



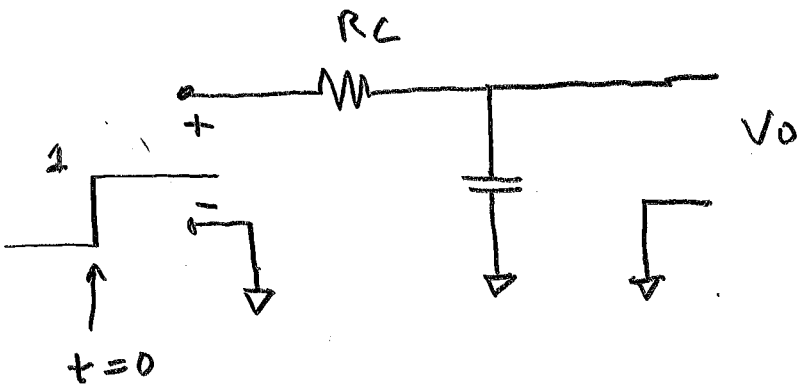
Before solving the right problem, let's solve the different one.



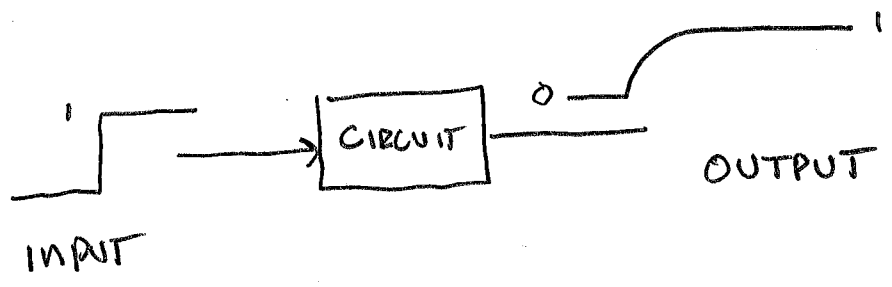Input is $u(t)$, output is $V_o(t) = 1 - e^{-t/RC}$



Now solve the right problem

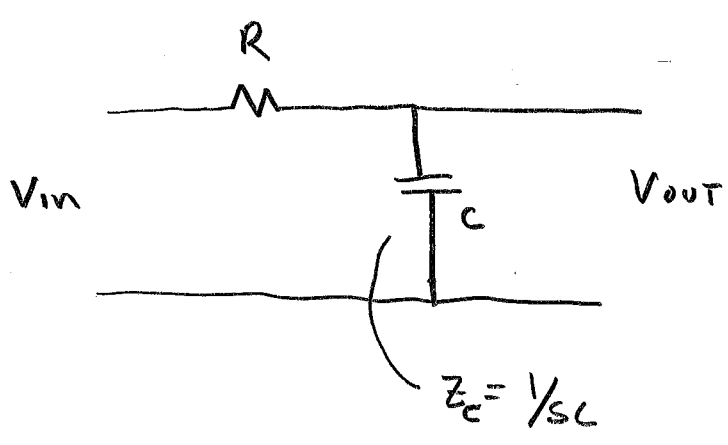


$$\frac{V_o}{V_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sCR}$$

Introduce tool: "Asymptotic Analysis"

RC circuit
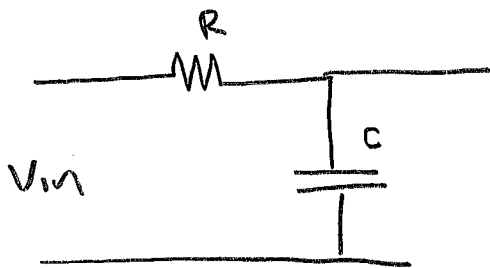
$$H(s) = H(j\omega) = \frac{1}{1 + sCR}$$




$V_o \left\{ \begin{array}{l} \text{Response at DC?} \\ \text{Response at freq} = \infty? \end{array} \right.$

$$\frac{1}{1 + sCR}$$

$\left\{ \begin{array}{l} \text{Response at DC?} \\ \text{Response at freq} = \infty \end{array} \right.$

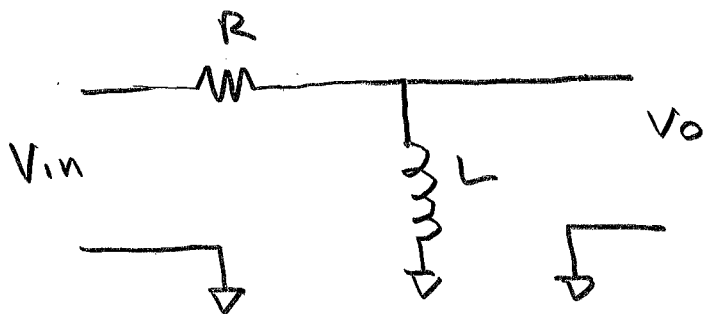This is an excellent way to see circuits intuitively and to check your work.



$$\frac{V_o}{V_{in}} = \frac{sL}{R + sL}$$

Circuit - Response at DC
Response at ∞

Equation - Response at DC
Response at ∞

Decibels

decibel-


$$G = \text{Number of } \hat{\text{bels}} = 10 \log \left[\frac{P_2}{P_1} \right] \leftarrow \text{Power gain}$$

$$G = \text{decibel} = 10 \log \left[\frac{V_2^2/R}{V_1^2/R} \right] = 20 \log \left(\frac{V_2}{V_1} \right)$$


Why do we need another term ?? !

Who has the money?

Raise
 \$ 1,00 / hr Lin
 or 10070 Log

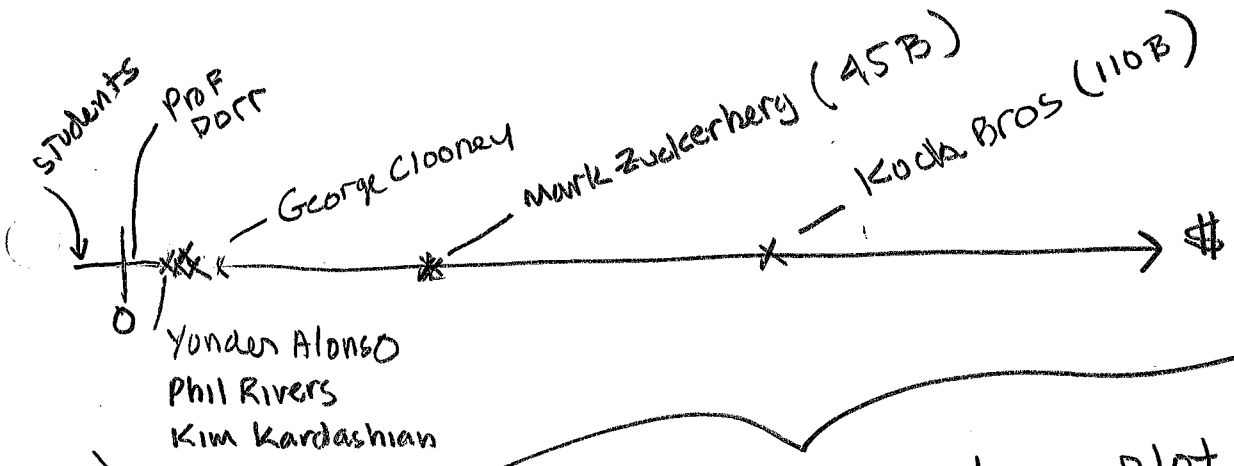

NOW PLOT THE LOG

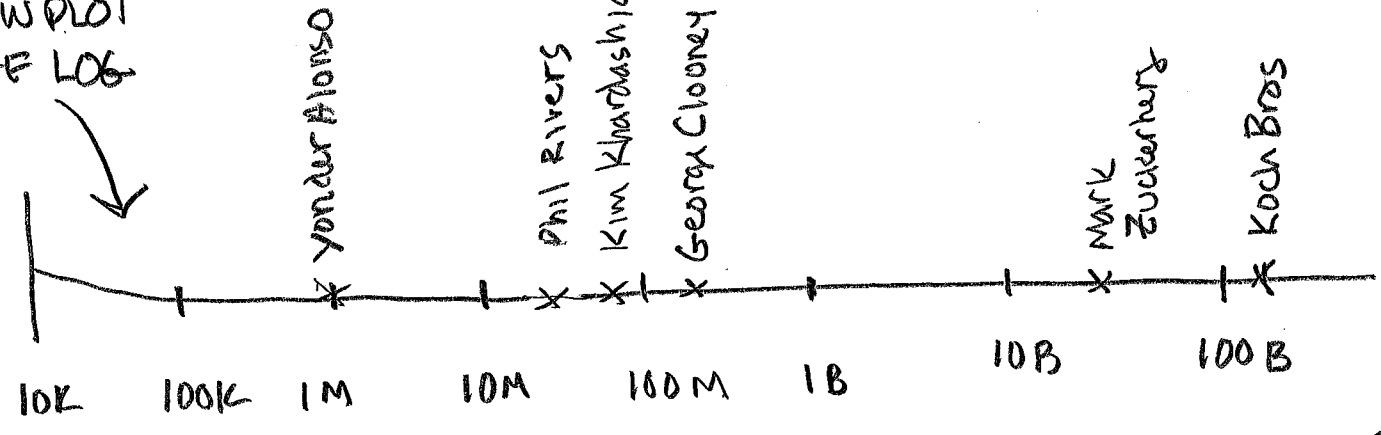


Great Plot


Remember power ratio of 10⁹ at beginning of lecture?

Plots for frequency response

$$\#dB(\omega) = 20 \log_{10}(|H(j\omega)|)$$

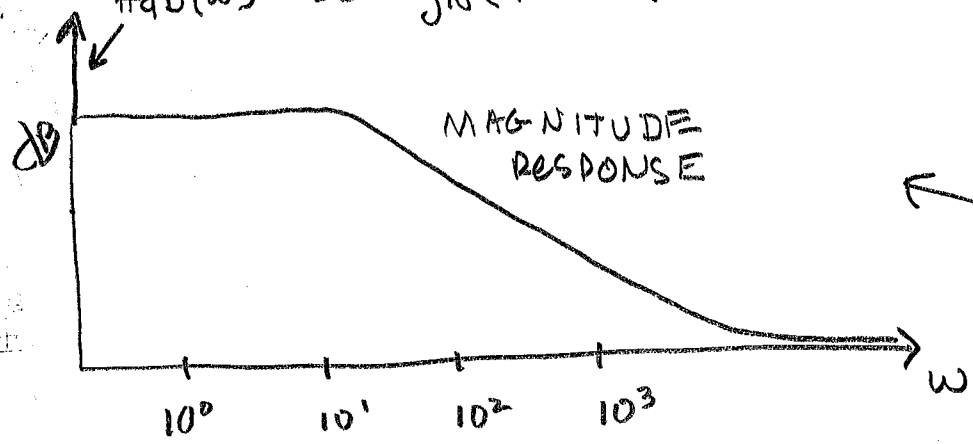


$$H(\omega) = |H(\omega)| \angle \phi(\omega)$$

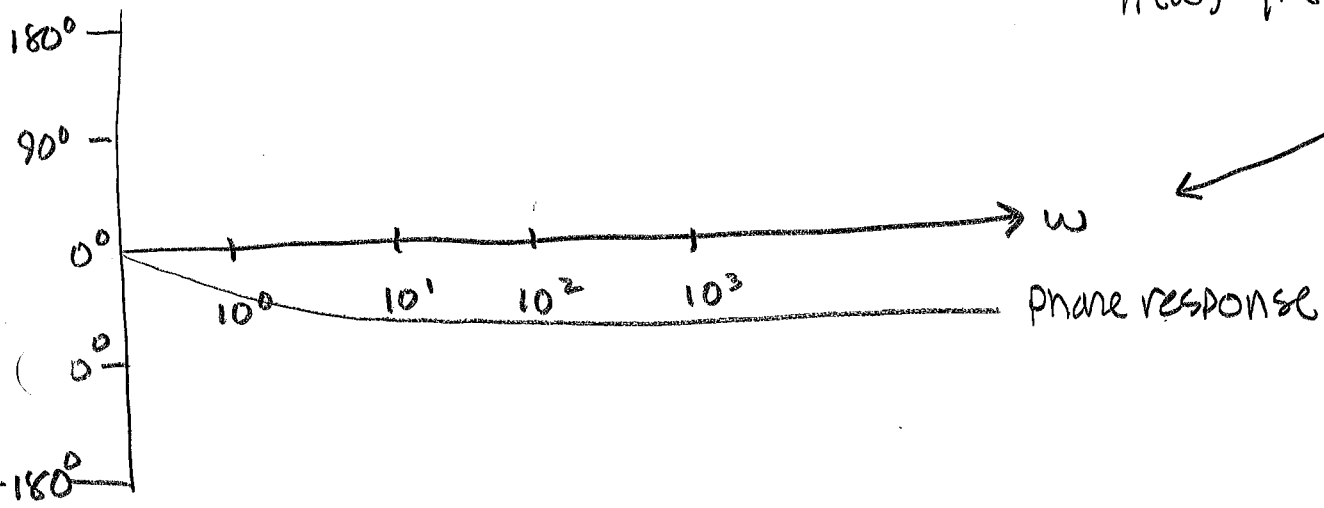

FOR RC CIRCUIT,


$$H(s) = \frac{1}{1+SCR} = \frac{1}{1+j\omega RC} = \underbrace{\frac{1}{\sqrt{1+\omega^2 R^2 C^2}}}_{\text{MAG}} \underbrace{\angle \tan^{-1}(\omega RC)}_{\text{Phase}}$$

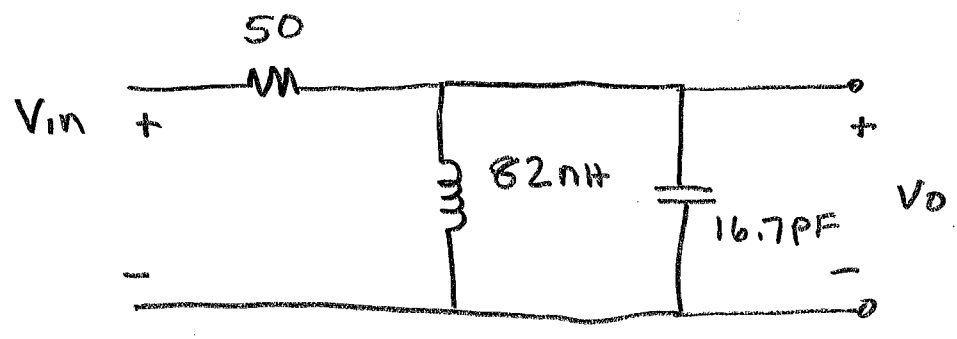Example - Find and plot Frequency Response



TRIAGE WITH Asymptotic analysis

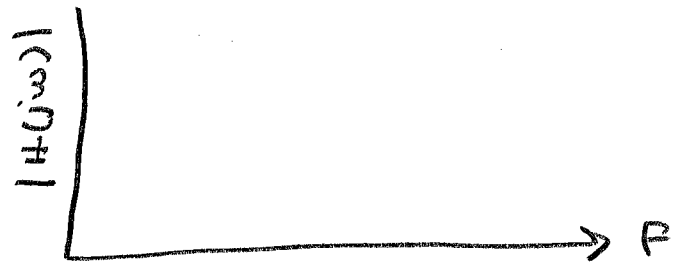- Response at DC ?
- Response at ∞ ?
- Response in the middle ?



$$\frac{V_o}{V_{in}} = \frac{Z_L || Z_C}{Z_L || Z_C + R} = \text{WAIT, STOP, MAKE IT EASIER!}$$

$$Z_L || Z_C = \frac{SL \times \frac{1}{SC}}{SL + \frac{1}{SC}} = \frac{SL}{S^2LC + 1} = \frac{N}{D}$$

$$\text{SO } \frac{V_o}{V_{in}} = \frac{\frac{N}{D}}{\frac{N}{D} + R} = \frac{N}{N + DR} = \frac{SL}{SL + (S^2LC + 1)R}$$

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{SL}{s^2RLC + R + SL} = \frac{\frac{SL}{RLC}}{s^2 \frac{RLC}{RLC} + \frac{R}{RLC} + \frac{SL}{RLC}}$$

$$H(s) = \frac{1}{RL} \times \frac{s}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$


Hey, note the similarity to parallel RLC characteristic Equation

Check it ...

DC $\rightarrow s=0 \rightarrow H(s) = \frac{1}{RL} \cdot \frac{0}{1/LC} = 0 \quad \checkmark$

freq = ω , $s=j\omega \rightarrow H(s) = \frac{\infty}{\infty^2} = 0 \quad \checkmark$

mid range \rightarrow something

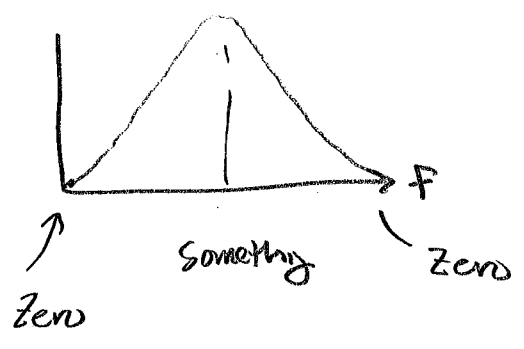

LOGARITHMIC COUNTING

10.1/2


PROBLEM: Create a set of frequency values that are uniformly spaced on a log plot.

- Start at frequency F_s
- Plot covers d decades
- Plot ppd points per decade

Then the plot contains $d \times ppd$ points and the frequencies are:

$$F_k = F_s \times 10^{\frac{k}{ppd}}, \quad k = 0, 1, \dots, (d \times ppd - 1)$$

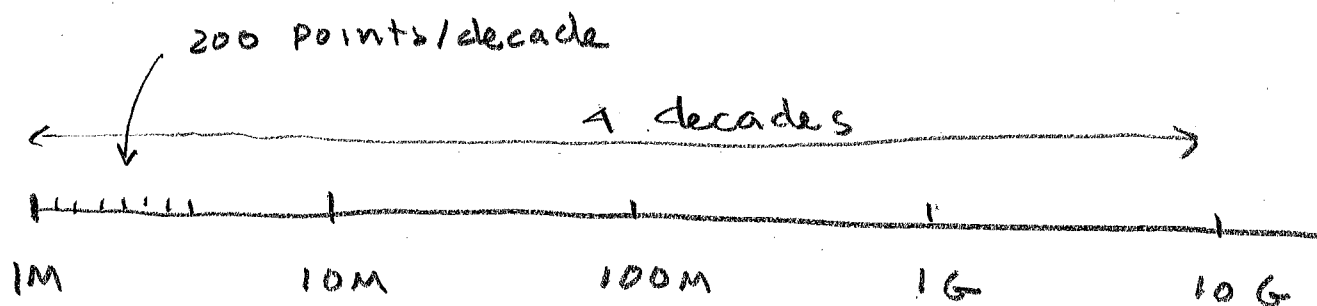Say $F_s = 1 \text{ MHz}$, $d = 4$ decades, $ppd = 200$ points/dec





Note: when $k > ppd$,


$$\begin{aligned} F_k &= F_s \times 10^{\frac{ppd + k'}{ppd}} = F_s \times 10^{\frac{ppd}{ppd}} \times 10^{\frac{k'}{ppd}} \\ &= 10 F_s \times 10^{k'/ppd} \end{aligned}$$

... and so on ...

Bandpass centered at 108 MHz

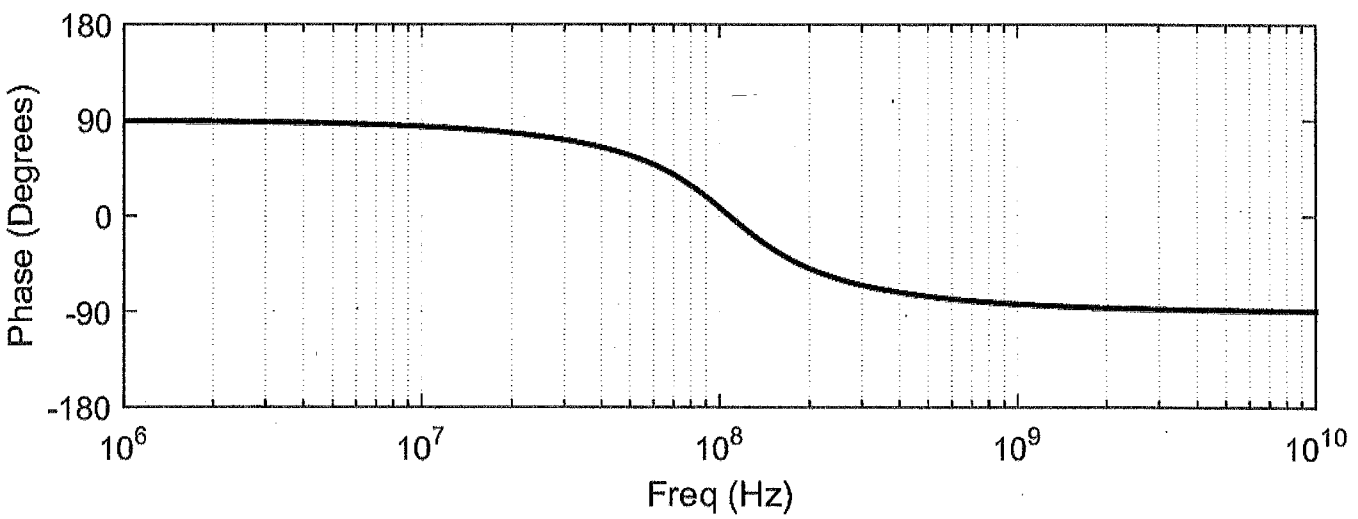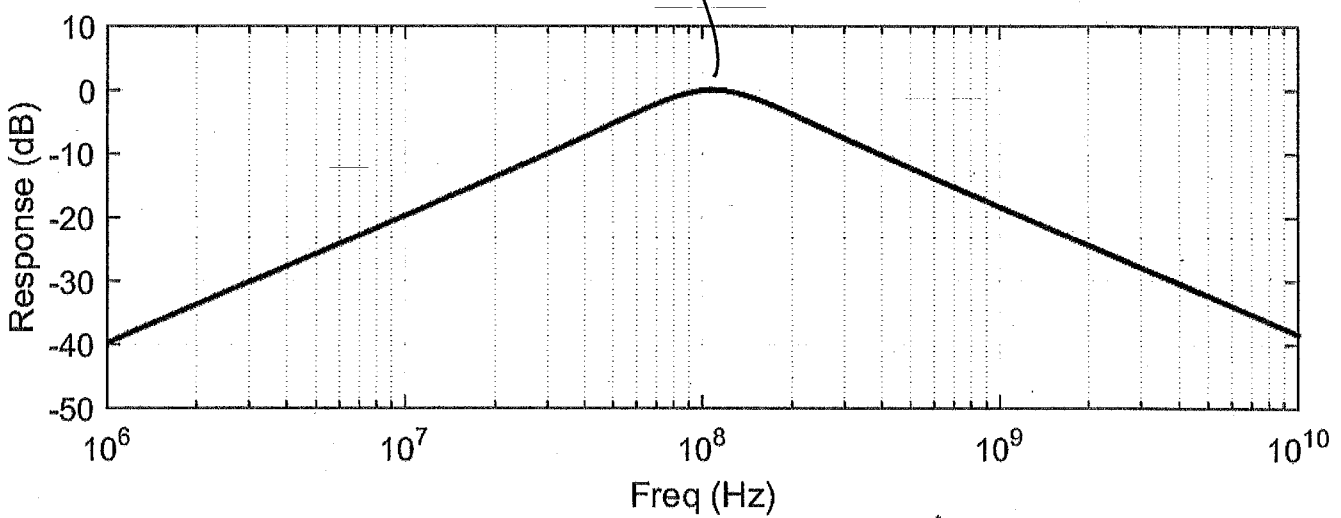

FLASHBACK TO CH 8

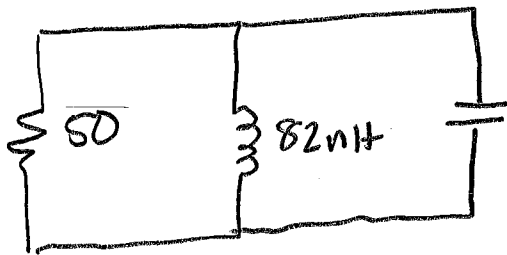

$\alpha = 3.77 \text{e}8, \omega_0 = 6.78 \text{e}8$

$\omega_0 > \alpha$ so underdamped

$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow 6.78 \text{e}8 \text{ rad/sec}$

That's 108 MHz

Remember corner pipe!

```
% Filename:      ComputeFreqResp.m
% Author:       Barry Dorr
% Last Modified: 10-23-2012

% This script computes the frequency response for a s-domain transfer function.

clear all;
close all;

StartFreq = 1000000;    % Lowest frequency to plot.
NumDec = 4;            % Number of decades to plot.
PtsPerDec = 200;      % Number of frequency points plotted per decade.

% Pre-allocate results matrices.
MagResp = zeros(NumDec*PtsPerDec,1);    % Matrix containing magnitude response.
PhaseResp = zeros(NumDec*PtsPerDec,1);  % Matrix containing phase response.
Freq = zeros(NumDec*PtsPerDec,1);       % Matrix containing plot frequencies.

% Values for example
R = 50;
L = 82e-9;
C = 26.48e-12;

% Compute frequency response at frequency points uniformly-spaced on a log plot.
for i=1 : NumDec*PtsPerDec
    Freq(i) = StartFreq*10^(i/PtsPerDec);    % Evaluate at this frequency.
    s = 1j * 2*pi*Freq(i);                  % Determine complex frequency.

    H = 1/(R*C) * s/(s^2 + s/(R*C) + 1/(L*C)); % Compute response at this frequency.

    MagResp(i) = abs(H);                    % Place magnitude response in result matrix.
    PhaseResp(i) = angle(H)*360/(2*pi);    % Place phase response in result matrix.
end

% Plot magnitude and phase.
subplot(2,1,1);
HMag=semilogx(Freq,20*log10(MagResp), 'color','k', 'linewidth', 2); % Plot magnitude
set(gca,'FontSize',12);
xlabel('Freq (Hz)');
ylabel('Response (dB)');
ylim([-50 10]);
grid on;

subplot(2,1,2);
HPhs = semilogx(Freq,PhaseResp, 'color','k', 'linewidth', 2); % Plot phase
set(gca,'FontSize',12);
xlabel('Freq (Hz)');
ylabel('Phase (Degrees)');
ylim([-180 180]);
set(gca,'YTick',[-180, -90, 0, 90, 180]);
grid on;
```