

L1


LECTURE 17 BODE PLOTS I

LAST LECTURE — Computed frequency response
OF a simple circuit.


- Computed separate plots for magnitude and phase.
- Plotted in Matlab.
- Asymptotic Analysis

Today's lecture: Bode plots - a quick way to approximate the frequency response OF a circuit.

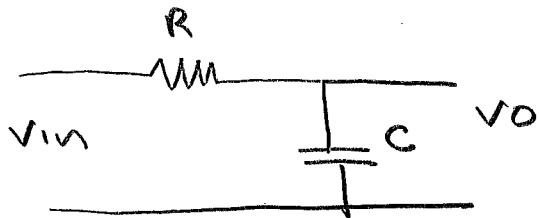Bode plot - helps you get an intuitive feel for circuits


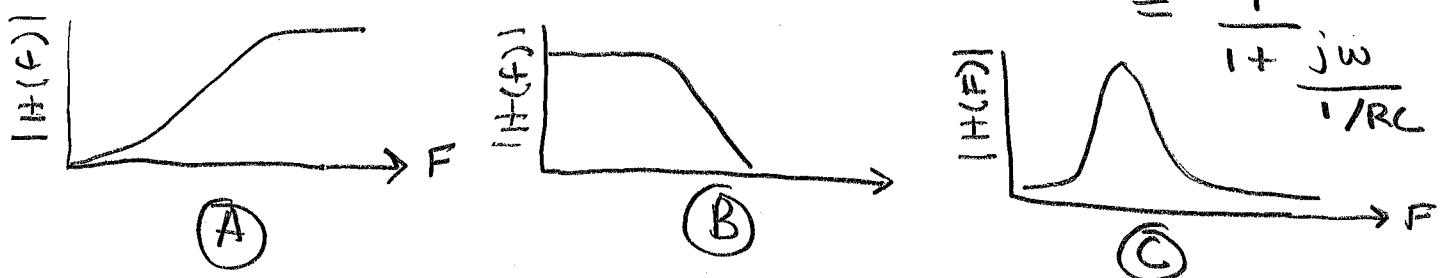
$$\frac{V_o(s)}{V_{in}(s)} = H(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sRC}$$



[2]

$$\frac{V_o(s)}{V_{in}(s)} = H(s) = H(j\omega) = \frac{1}{1 + j\omega \frac{1}{RC}} = \frac{1}{1 + j\omega \frac{1}{\omega_p}} \quad \text{where } \frac{1}{RC} = \omega_p$$

Exact frequency response

$$H_{dB}(w) = 20 \log_{10} \left| \frac{1}{1 + j\omega \frac{1}{\omega_p}} \right| = 20 \log_{10} \left(\frac{1}{\sqrt{1 + \frac{w^2}{\omega_p^2}}} \right)$$


Approximate frequency response

At low frequencies



$$H_{dB} \approx 20 \log_{10} \left(\frac{1}{\sqrt{1+0}} \right) = 0 \text{ dB}$$

At high frequencies
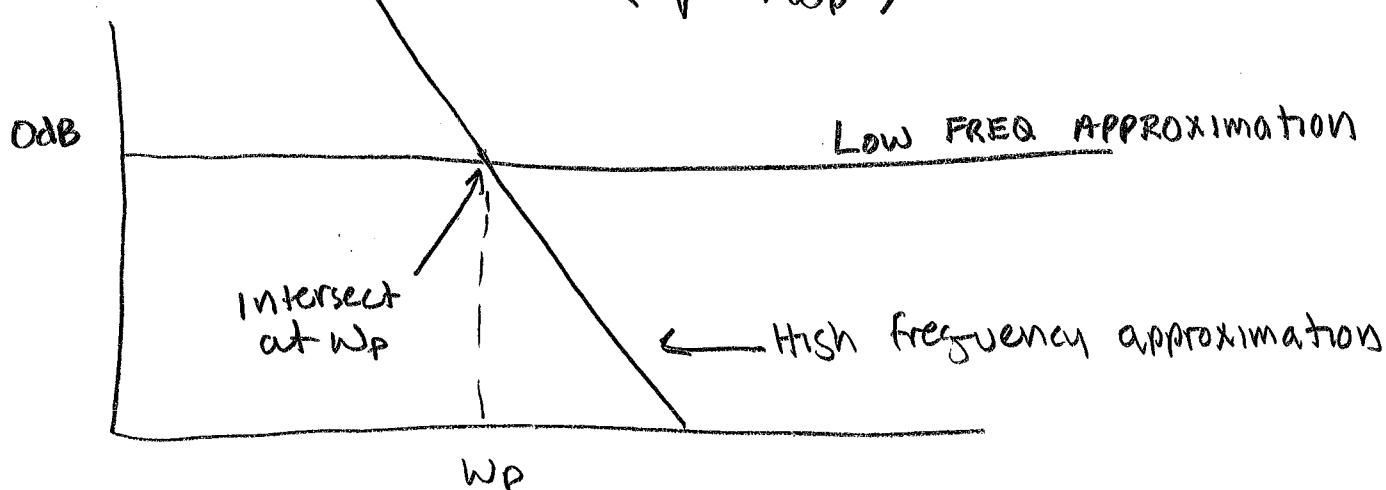
$$H_{dB}(w) \approx 20 \log \left(\frac{1}{\sqrt{w^2/\omega_p^2}} \right) = 20 \log \left(\frac{\omega_p}{w} \right)$$



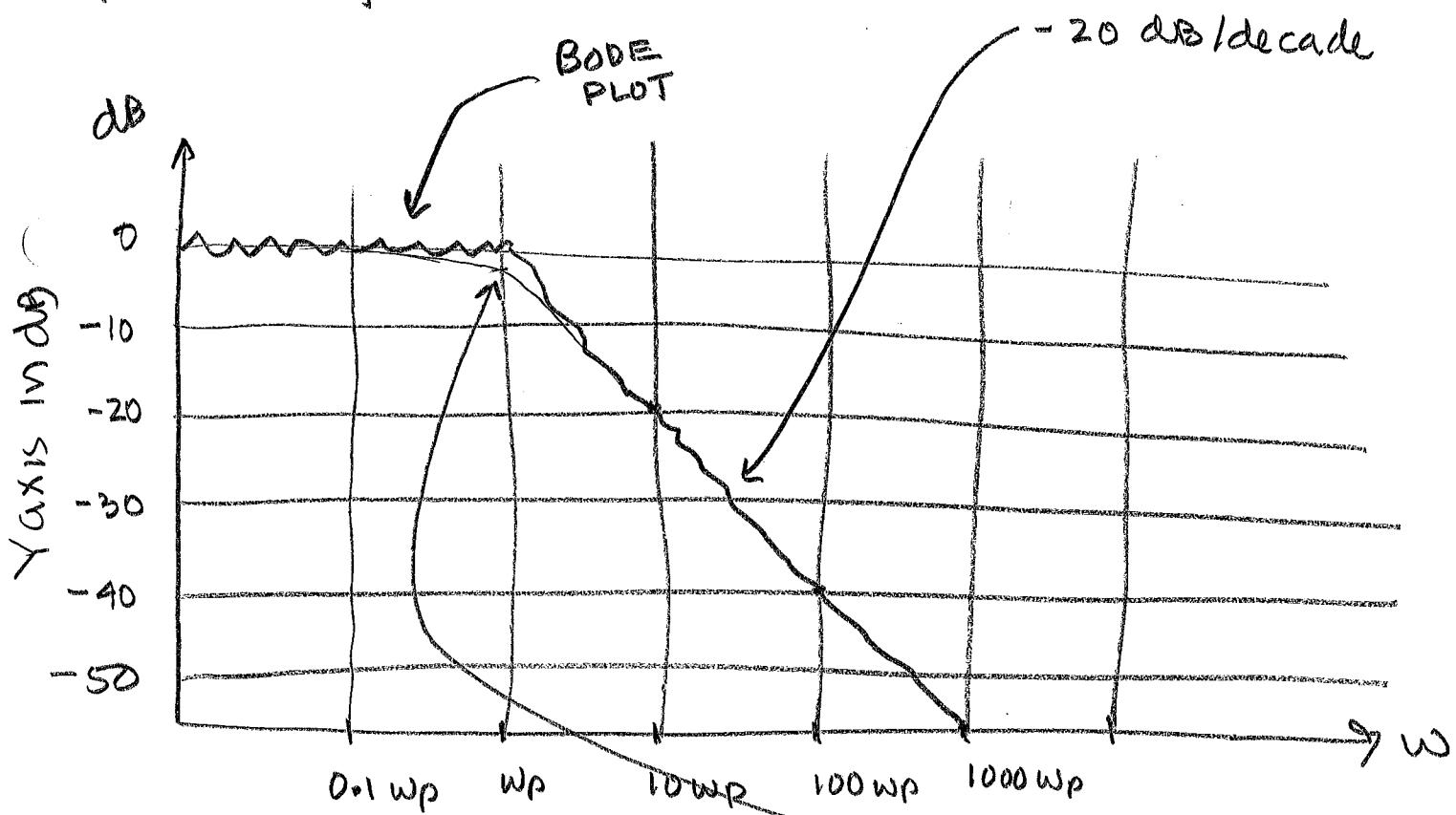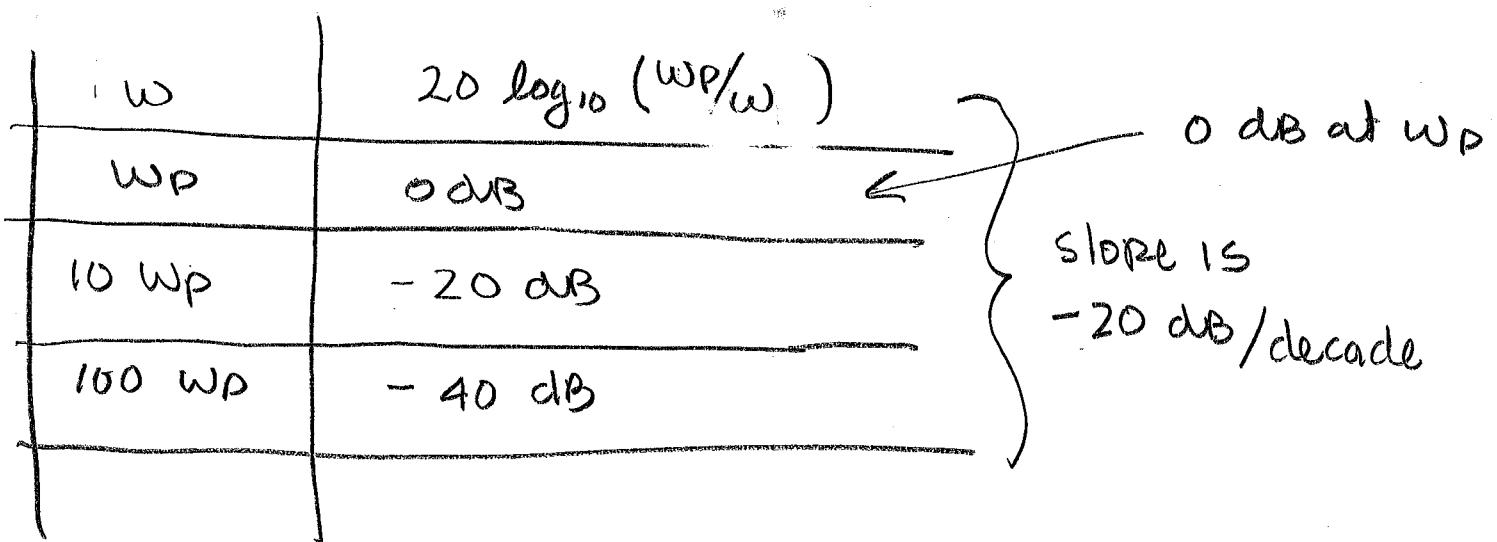Look Further at high frequency approximation



$$20 \log_{10} \left(\frac{1}{\sqrt{1 + \frac{w^2}{w_p^2}}} \right) = 20 \log \left(\frac{1}{\sqrt{2}} \right) = -3 \text{ dB}$$

Say

$$H(j\omega) = \frac{K(j\omega) \underbrace{(1 + \frac{j\omega}{\omega_{Z_1}})(1 + j\omega/\omega_{Z_2})}_{\text{zeros}}}{\underbrace{(1 + \frac{j\omega}{\omega_{P_1}})(1 + j\omega/\omega_{P_2})}_{\text{poles}}}$$

4


Frequency response

$$H_{dB}(j\omega) = 20 \log_{10} \left[\frac{|T_1(j\omega)| \cdot |T_2(j\omega)| \cdots}{|T_3(j\omega)| \cdot |T_4(j\omega)| \cdots} \right]$$

$$H_{dB}(j\omega) = 20 \log_{10} (|T_1(j\omega)|) + 20 \log (|T_2(j\omega)|) \\ - 20 \log_{10} (|T_3(j\omega)|) - 20 \log (|T_4(j\omega)|) \cdots$$

Shows we can handle terms independently and then add them.

We already saw pole behavior...

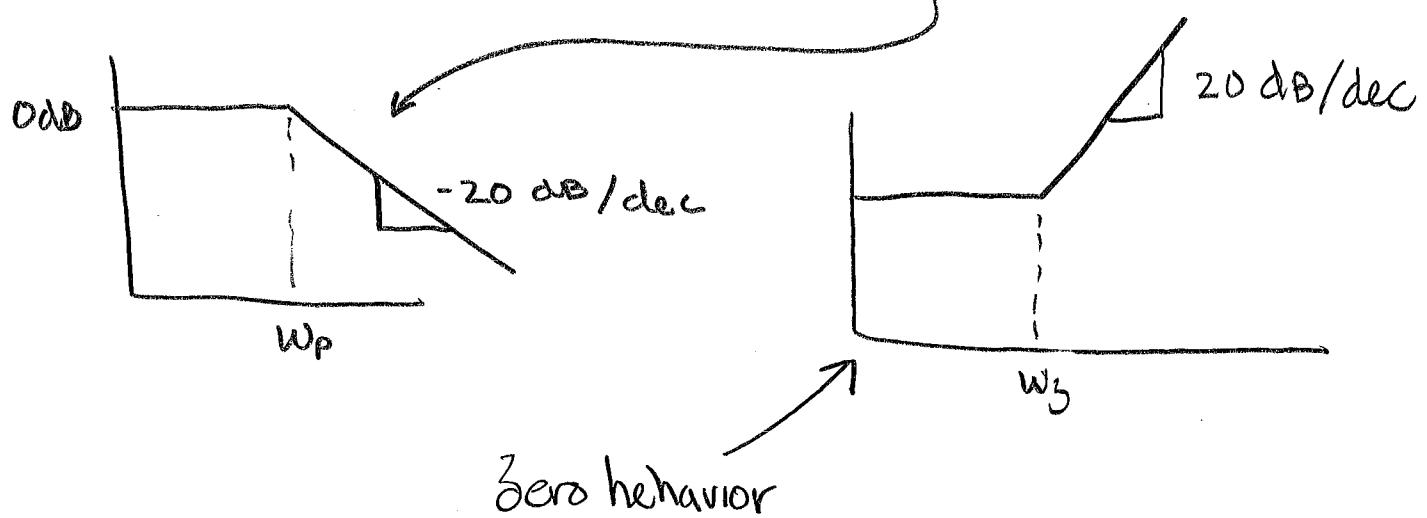


Transfer Function had constant, K


$$20 \log_{10}(K) = \text{flat line!}$$

Transfer function had zero at origin

$$20 \log_{10}(|j\omega|)$$

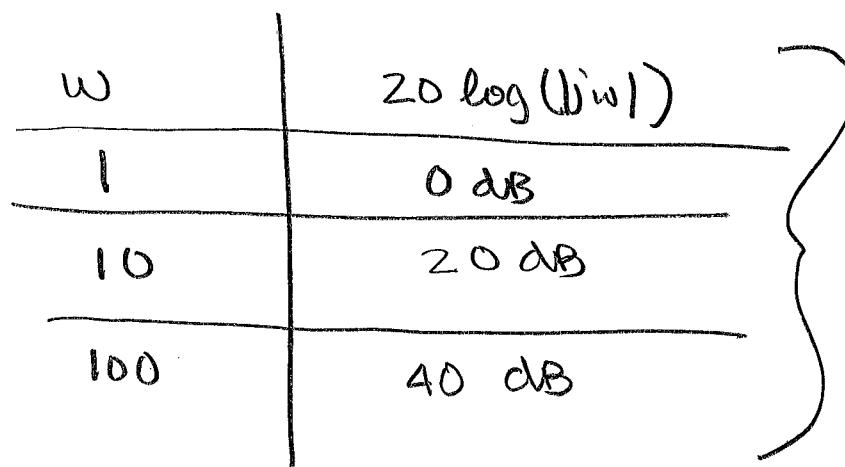

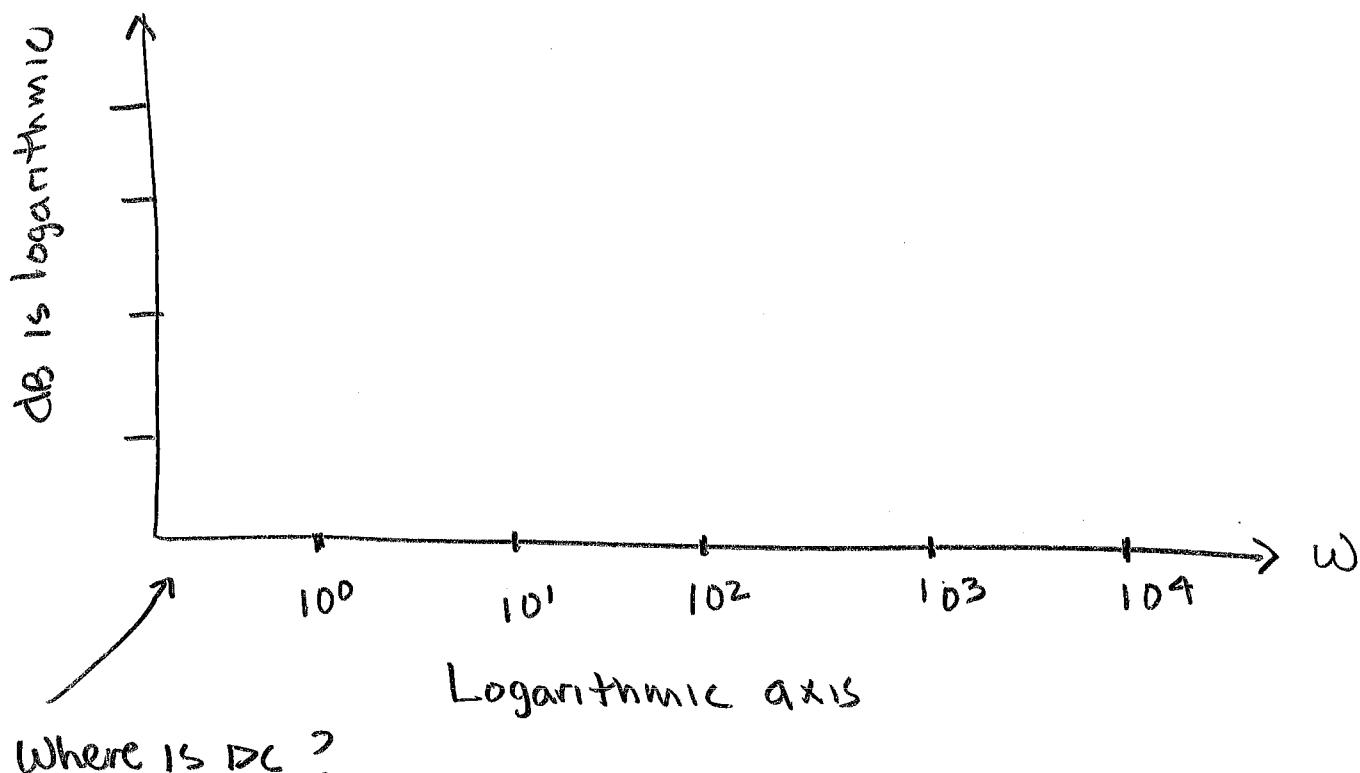
line segment has
slope of 20 dB/decade.
Goes through 0 dB at
 $w = 1 \text{ rad/s}$



Where is DC?

Example:

Sketch a Bode plot for the circuit below

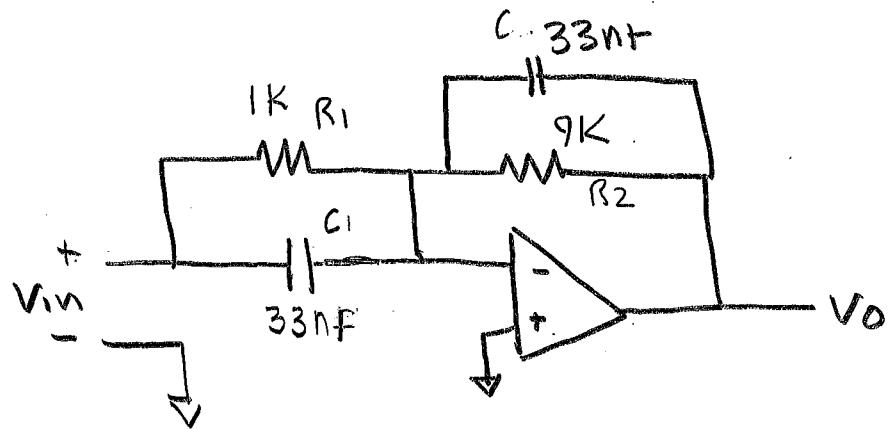

$$\frac{V_o}{V_{in}} = -\frac{R_2 // Z_C}{R_1 // Z_C} \quad R // C = \frac{R \times 1/sC}{R + 1/sC} = \frac{R}{1 + SCR}$$

$$H(s) = \frac{\frac{R_2}{1+SCR_2}}{\frac{R_1}{1+SCR_1}} = -\frac{R_2}{R_1} \left(1 + \frac{s}{1/R_{1C}} \right) \left(1 + \frac{s}{1/R_2C} \right)$$

Constant Term

Zero

Pole

$$\frac{R_2}{R_1} = 9, \quad \frac{1}{R_{1C}} = 30.3E3 \text{ r/s} = 10^{4.48} \quad \frac{1}{R_2C} = 3.37E3 \text{ r/s} = 10^{3.53}$$

$$H(j\omega) = -9 \times \frac{1 + s/30.3E3}{1 + s/3.37E3}$$



Constant term

$$20 \log_{10}(9) = 19.08 \text{ dB}$$

16


Zero - Flat line, 20 dB/decade above ω_3

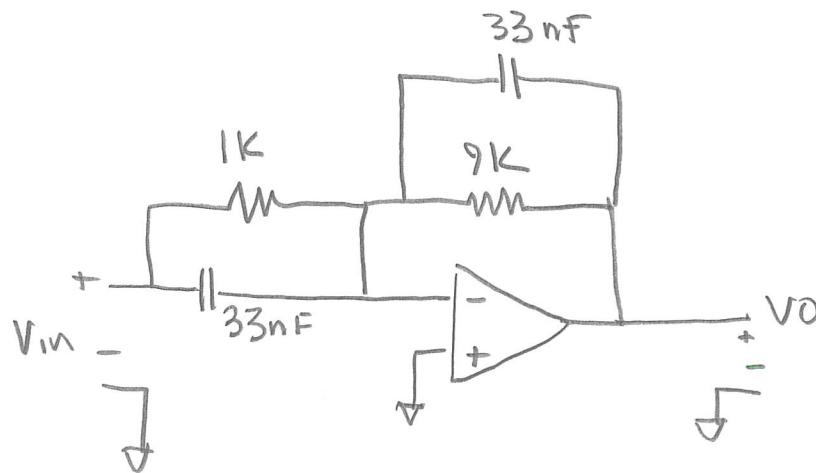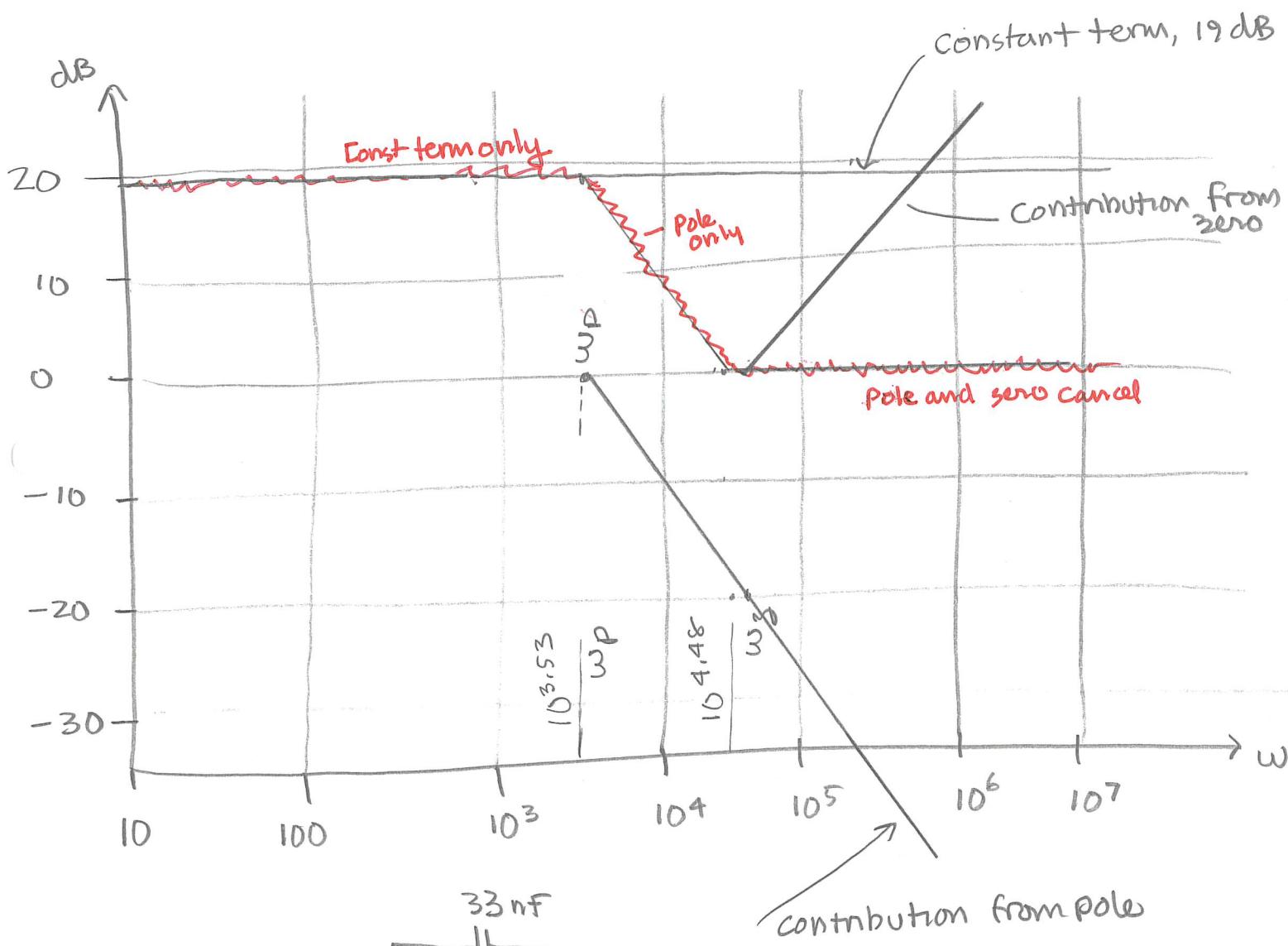Pole - Flat line, -20 dB/decade above ω_P



Check with Asymptotic analysis


Reality check.. Is this practical?

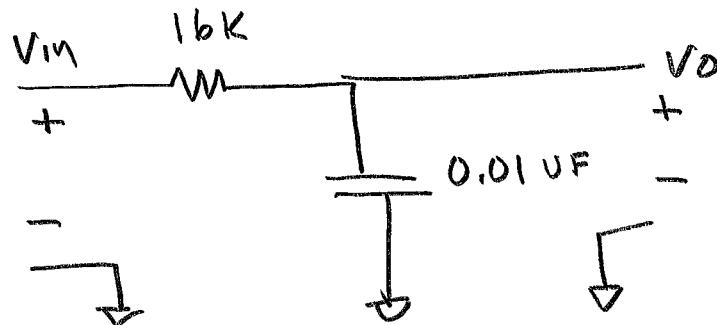

Find HdB(153 kHz)

$$H(s) = \frac{1/s_C}{R + 1/s_C} = \frac{1}{1 + sCR} = \frac{1}{1 + \frac{j\omega}{1/RC}} = \frac{1}{1 + \frac{j\omega}{\omega_p}}$$

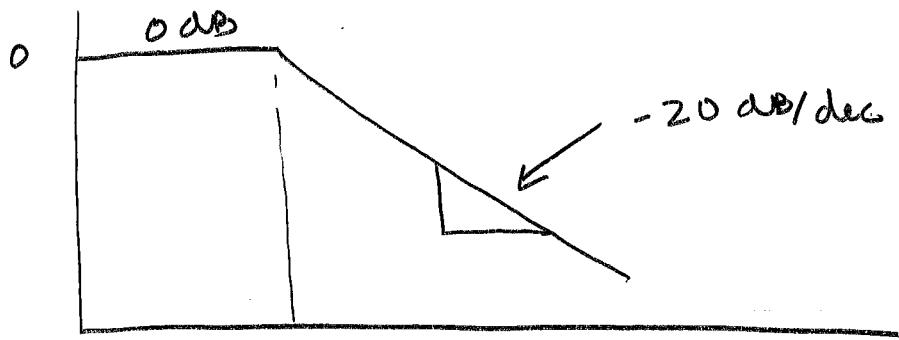so $\omega_p = \frac{1}{RC}$ or $f_{pole} = \frac{1}{2\pi RC} = \underline{994.7 \text{ Hz}}$



$$994.7 \text{ Hz} \\ = f_p$$

How many decades between 153 kHz and 995 Hz?

$$10^{\text{dec}} = \frac{153 \text{ K}}{995} \quad \text{or} \quad \text{dec} \times \log_{10}(10) = \log_{10}\left(\frac{153 \text{ K}}{995}\right)$$

$$\text{dec} = \log_{10}\left(\frac{153 \text{ K}}{995}\right) = 2.19 \text{ dec} \quad \text{so} \quad 0 - 20 \frac{\text{dB}}{\text{dec}} \times 2.19 \text{ dec}$$

$$= -43.8 \text{ dB}$$

PRACTICE PROBLEM 14.1, Pg 626


(Sketch Bode plot for

$$H(j\omega) = \frac{50j\omega}{(j\omega+4)(j\omega+10)^2}$$

Put in form used on sheet 4

$$H(j\omega) = \frac{50}{4 \times 10^2} \times \frac{j\omega}{\left(1 + \frac{j\omega}{4}\right) \left(1 + \frac{j\omega}{10}\right)^2}$$

↗ zero at origin
 ↘ Constant term
 ↗ single pole at $\omega=4$
 ↗ double pole at $\omega=10$

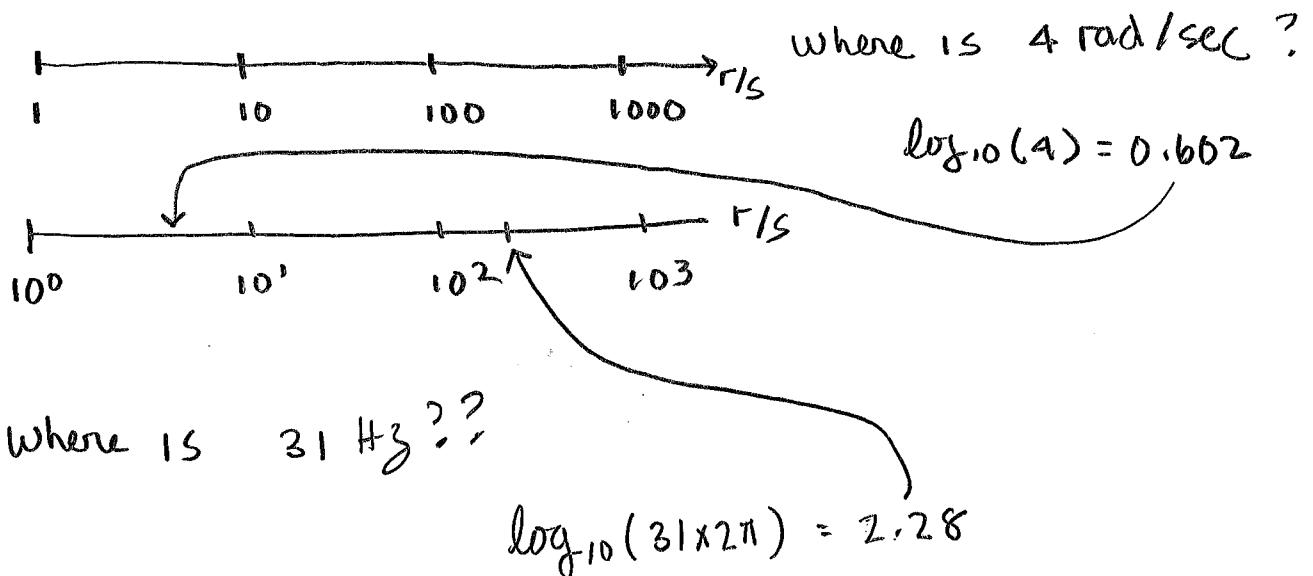

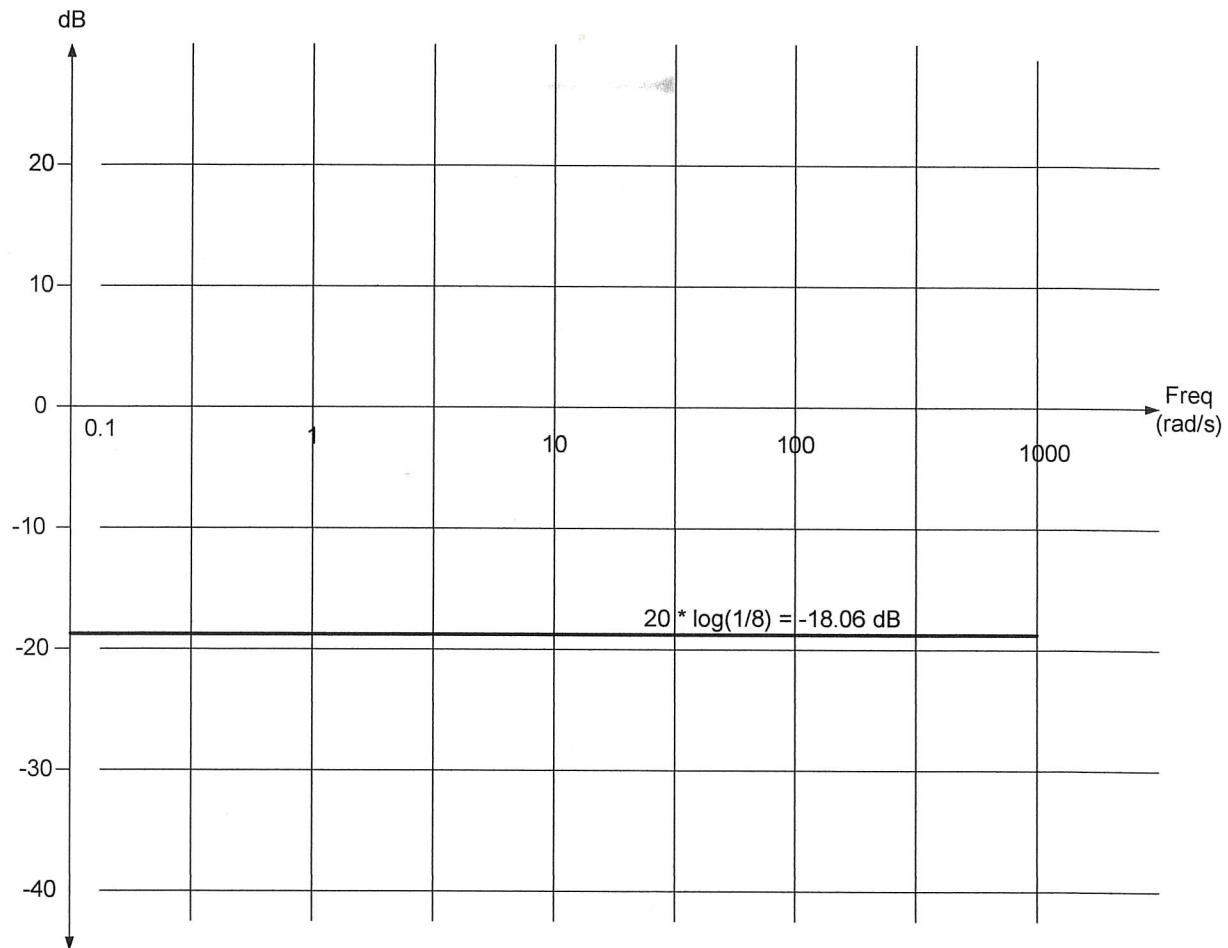


Figure 1 - Plot the constant Term

$$H(s) = \frac{1}{8} \cdot \frac{j \cdot \omega}{\left(1 + \frac{j \cdot \omega}{4}\right) \cdot \left(1 + \frac{j \cdot \omega}{10}\right)^2}$$

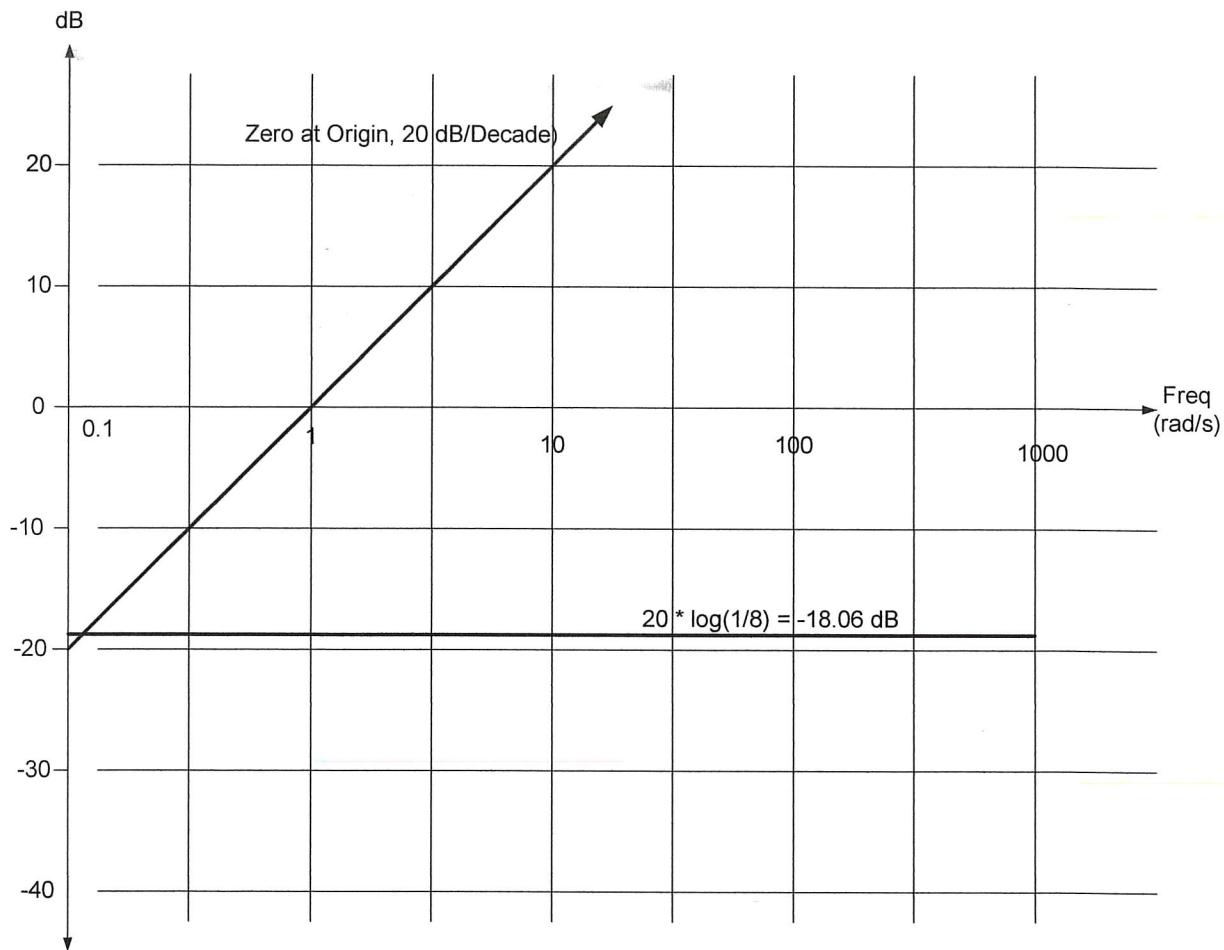


Figure 2 - Add Zero at origin

$$H(s) = \frac{1}{8} \cdot \frac{j \cdot \omega}{\left(1 + \frac{j \cdot \omega}{4}\right) \cdot \left(1 + \frac{j \cdot \omega}{10}\right)^2}$$

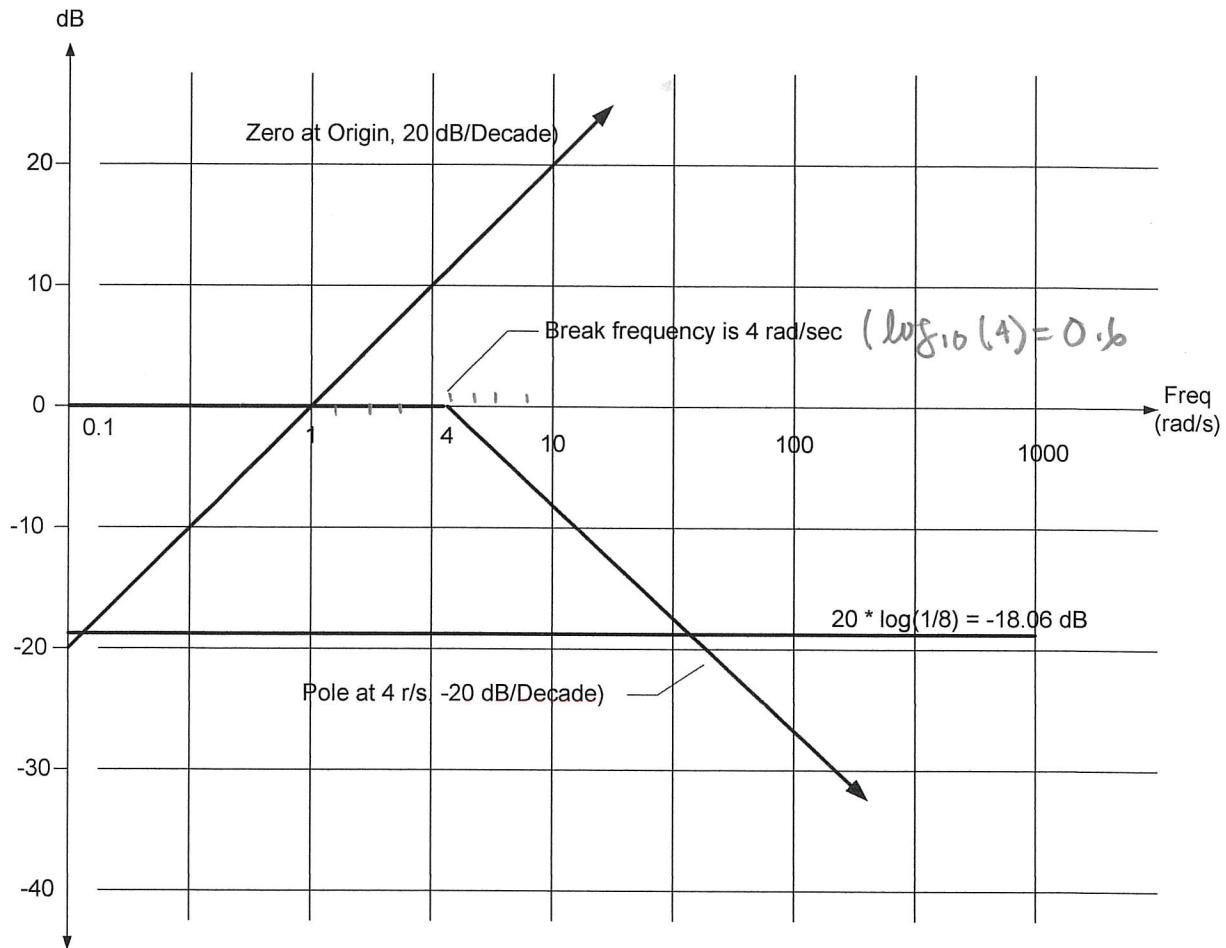


Figure 3 - Add the pole at 4 rad/s

$$H(s) = \frac{1}{8} \cdot \frac{j \cdot \omega}{\left(1 + \frac{j \cdot \omega}{4}\right) \cdot \left(1 + \frac{j \cdot \omega}{10}\right)^2}$$

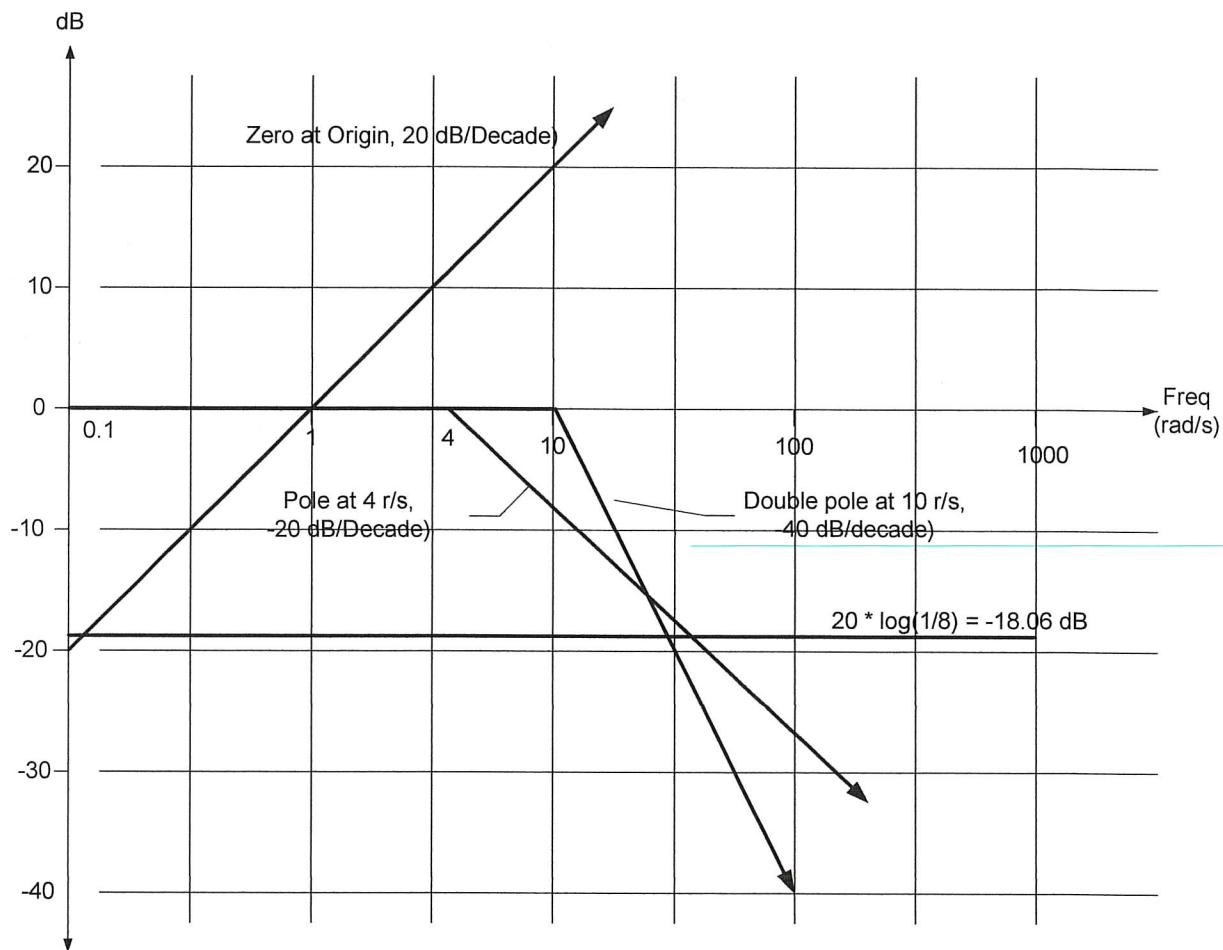


Figure 4 - Add the double pole at 10 r/s

$$H(s) = \frac{1}{8} \cdot \frac{j \cdot \omega}{\left(1 + \frac{j \cdot \omega}{4}\right) \cdot \left(1 + \frac{j \cdot \omega}{10}\right)^2}$$

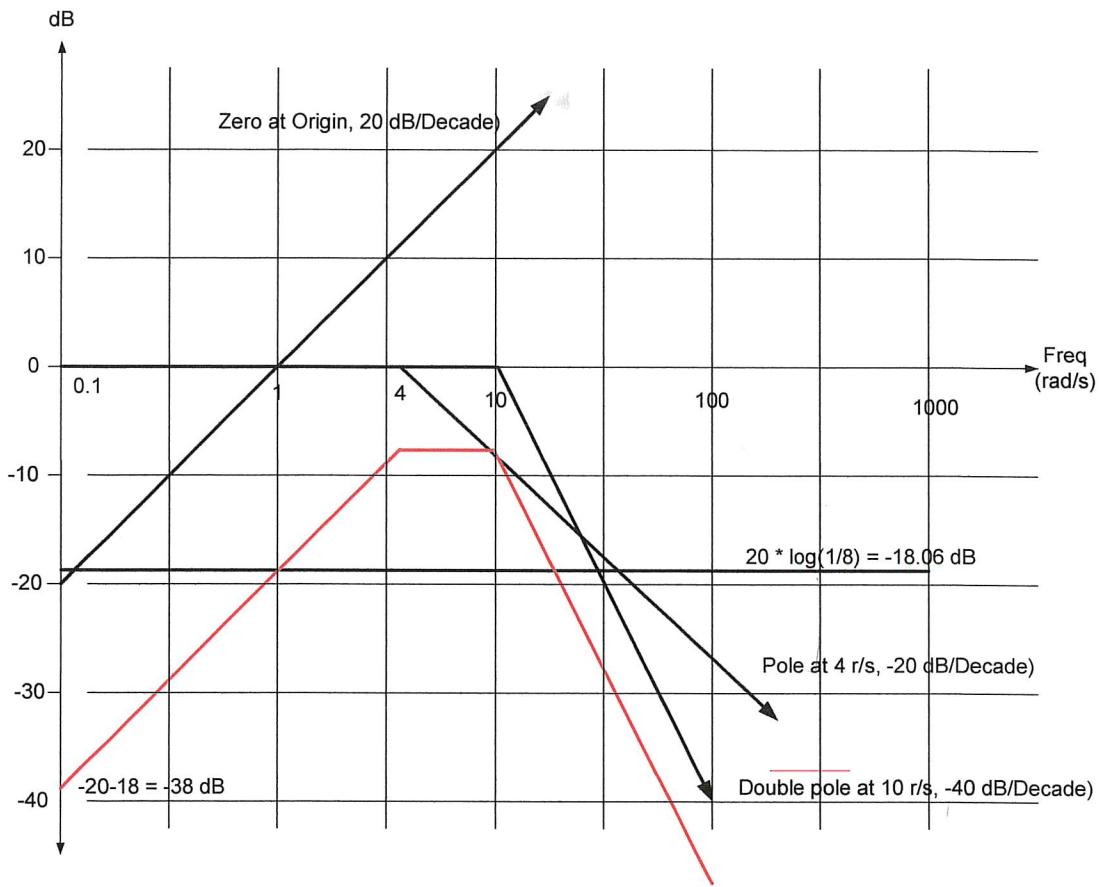


Figure 5 - Sum all the parts to Get magnitude

$$H(s) = \frac{1}{8} \cdot \frac{j \cdot \omega}{\left(1 + \frac{j \cdot \omega}{4}\right) \cdot \left(1 + \frac{j \cdot \omega}{10}\right)^2}$$

Quadratic Terms (Poles or zeros)

$as^2 + bs + c \leftarrow \dots \text{in an expression}$

$s^2 + 2\zeta\omega_n s + \omega_n^2 \leftarrow \dots \text{control systems and circuits. Most common way you'll see it.}$

$$\omega_n^2 \left[\frac{s^2}{\omega_n^2} + \frac{2s}{\omega_n} + 1 \right] \leftarrow \text{Manipulate a bit...}$$

$$\omega_n^2 \left[1 + \frac{2\zeta j\omega}{\omega_n} + \frac{(j\omega)^2}{\omega_n^2} \right] \leftarrow \begin{array}{l} \text{Standard Form} \\ \text{see Eq 14.15} \end{array}$$

(If $\omega \ll \omega_n$, Magnitude = 1 $\rightarrow (20 \log_{10}(1) = 0 \text{ dB})$)

If $\omega \gg \omega_n$, Magnitude = $\frac{\omega^2}{\omega_n^2}$

and

$$20 \log_{10} \left(\frac{\omega^2}{\omega_n^2} \right) = 40 \log_{10} \left(\frac{\omega}{\omega_n} \right) \text{ dB}$$

and we see that slope is 40 dB/decade.

At ω_n , see Figure 14.2 Pg 622 for frequency peaking.

... the "boingier" it is, the more frequency peaking we see!



We started with $s^2 + 2\zeta\omega_n s + \omega_n^2$

and equated it to


$$\omega_n^2 \left[1 + 2\zeta \frac{jw}{\omega_n} + \frac{(jw)^2}{\omega_n^2} \right]$$

↑ constant term

EXAMPLE

$$L = 2 \text{ H}$$

$$R = 1 \text{ }\Omega$$

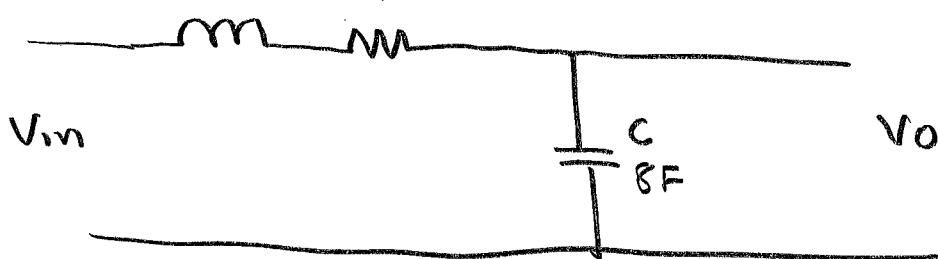

$$\frac{V_o}{V_{in}}(s) = H(s) = \frac{1/sC}{1/sC + R + sL}$$

$$= \frac{1}{LC} \times \frac{1}{s^2 + s \cdot \frac{R}{L} + \frac{1}{LC}}$$

← asymptotic analysis

DIGRESS TO CH 8

1) This is EQ 8.8 pg 320 for series RLC characteristic EQ

2) $\alpha = \frac{R}{2L} = \frac{1}{4}$, $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{4} \rightarrow$ Critical damping



L1b

Now put into standard form for plotting

... that's just algebra

$$\frac{1}{LC} \cdot \frac{1}{s^2 + \frac{SR}{L} + \frac{1}{LC}} = K \times \frac{1}{1 + 2\zeta \frac{jw}{\omega_n} + \frac{(jw)^2}{\omega_n^2}}$$

EQ 14.15

Multiply

$$\frac{1}{1 + SRC + S^2 LC} = K \times \frac{1}{1 + 2\zeta \frac{jw}{\omega_n} + \frac{(jw)^2}{\omega_n^2}}$$

$K = 1$

$$\frac{1}{1 + jwRC + \frac{(jw)^2}{1/LC}} = \frac{1}{1 + 2\zeta \frac{jw}{\omega_n} + \frac{(jw)^2}{\omega_n^2}}$$

$\omega_n^2 = \frac{1}{LC}$ or $\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4}} = \frac{1}{2}$

$$WRL = 2\zeta \frac{\omega}{\omega_n}, \quad \zeta = \frac{WRL \cdot \omega_n}{2\omega} = \frac{\omega_n R C}{2}$$

$$\zeta = \frac{1 \cdot 8}{4 \times 2} = 1.0$$

Critical damping, $\zeta = 1.0 \dots$

Summarize

$$K = 1.0$$

$$\zeta = 1.0$$

$$\omega_n = \frac{1}{4} \text{ rad/s}$$

$$s^2 + s \cdot \frac{R}{L} + \frac{1}{LC} \leftarrow \begin{array}{l} \text{Char Eq} \\ \text{for series RLC} \end{array}$$

$$\alpha = \frac{R}{2L} = \frac{1}{4}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \omega_n$$

$\alpha = \omega_0 \rightarrow \text{critical damping}$

Freq Response

CH 14

CHAPTER 8

$|H_{dB}|$

0dB

-40 dB/dec

Freq
rad/sec

$$\omega_n = \frac{1}{4} \text{ rad/s}$$