

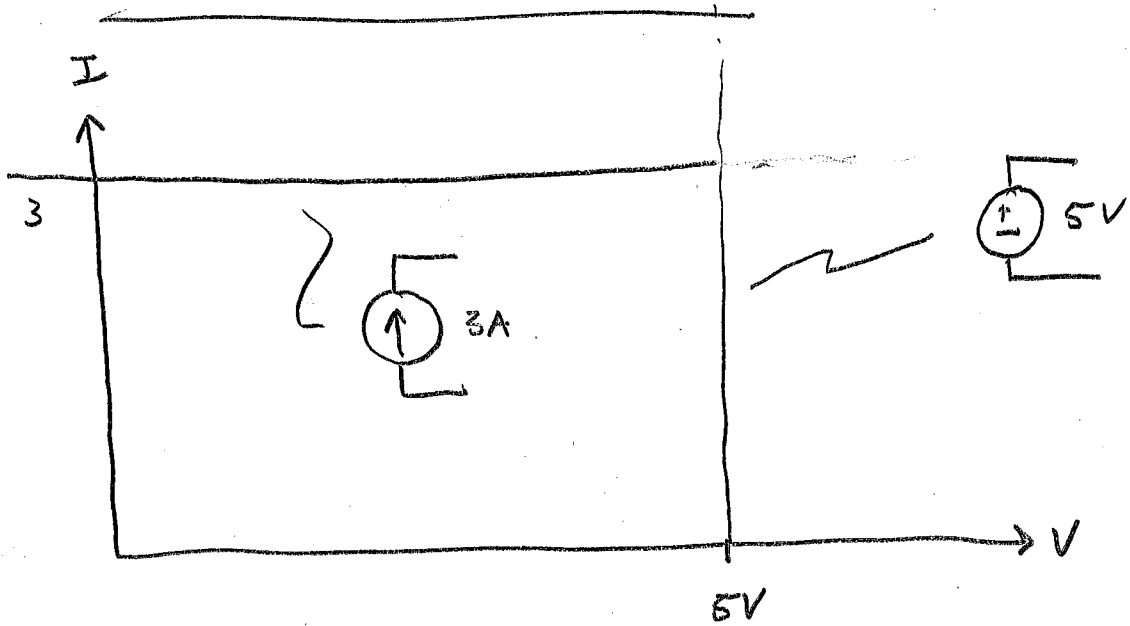
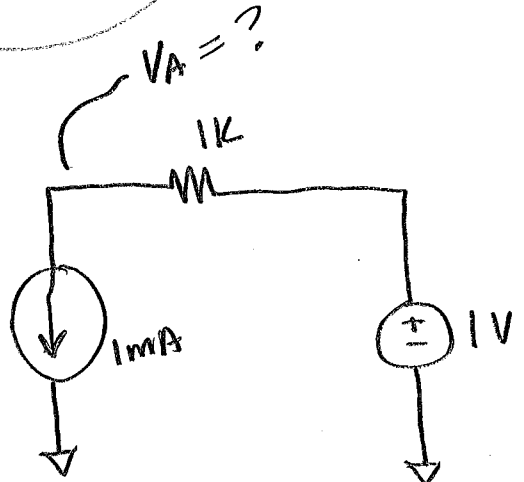


LECTURE #2

INITIAL CONDITIONS & OHM'S LAW

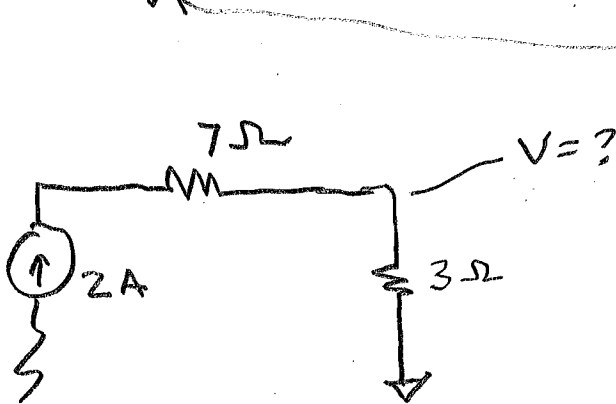

Voltage and Current sources

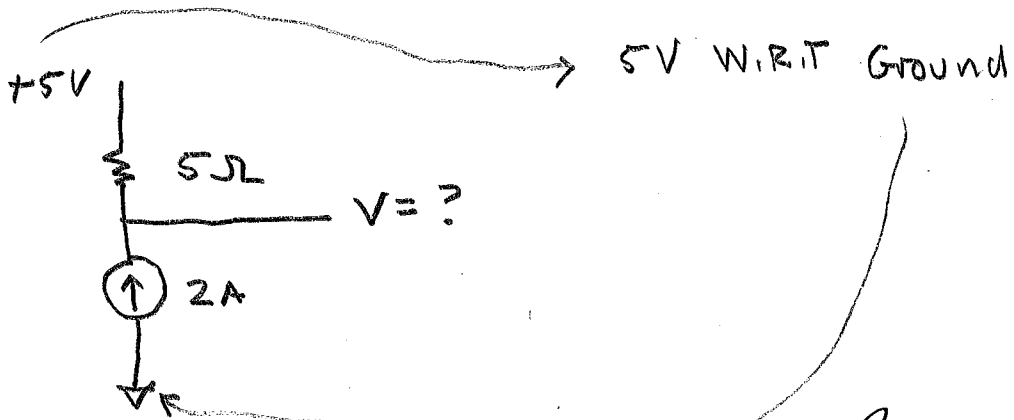

The Rules

"Verbal"

Equation

Inductor current cannot change instantaneously"

$$i_L(0^+) = i_L(0^-) \quad (1)$$

Capacitor voltage cannot change instantaneously

$$V_C(0^+) = V_C(0^-) \quad (2)$$

Inductor voltage can change instantaneously

$$V_L = L \frac{di}{dt} \quad (3)$$

Capacitor current can change instantaneously

$$i_C = C \frac{dV}{dt} \quad (4)$$


† steady state  $\frac{di}{dt} = 0$  so  
inductor voltage is zero

$$V_L(\infty) = 0 \quad (5)$$

† steady state  $\frac{dV}{dt} = 0$  so

$$I_C(\infty) = 0 \quad (6)$$

$$i_C = 0$$

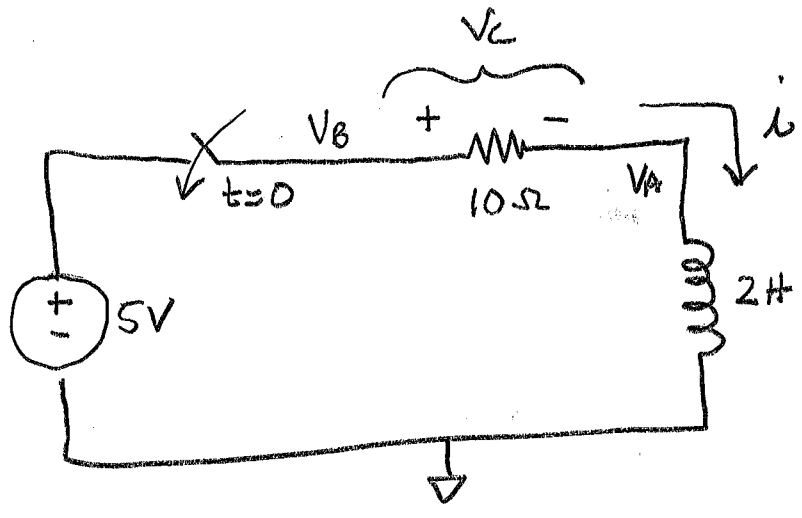


$i(0^-) = ?$ ,  $i(0^+) = ?$ ,  $i(\infty) = ?$ ,  $V_A(0^-) = ?$ ,  $V_A(\infty) = ?$

$V_B(0^-) = ?$ ,  $V_B(0^+) = ?$ ,  $V_B(\infty) = ?$ ,  $V_L(0^-) = ?$ ,  $V_L(0^+) = ?$

$V_L(\infty) = ?$

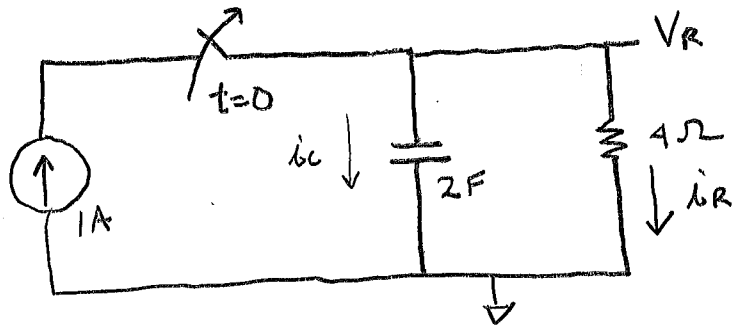$\frac{di}{dt}(0^+)$ ,  $V_A(0^+) = L \frac{di}{dt}(0^+)$  so  $\frac{di}{dt}(0^+) = \frac{V_A(0^+)}{L}$



$V_R(0^-) =$

$V_R(0^+) =$

$V_R(\infty) =$

$i_C(0^-) =$


$i_C(0^+) =$

$i_C(\infty) =$


$\frac{dV_R}{dt}(0^-) =$

$\frac{dV_R}{dt}(0^+) = \rightarrow i_C(t=0^+) = C \frac{dV_C(0^+)}{dt}$  so  $\frac{dV_C(0^+)}{dt} = \frac{i_C(0^+)}{C}$

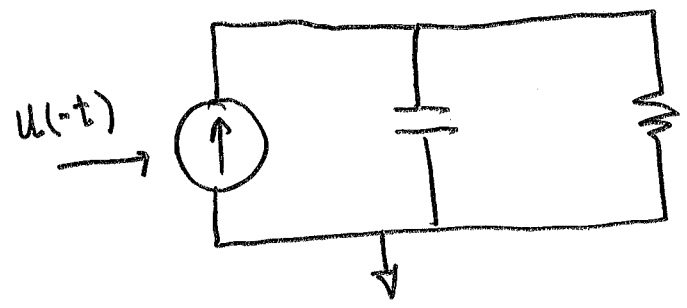$\frac{di_R}{dt} = \frac{dV_R(0^+)}{dt} \times \frac{1}{R}$



Better way to draw circuit

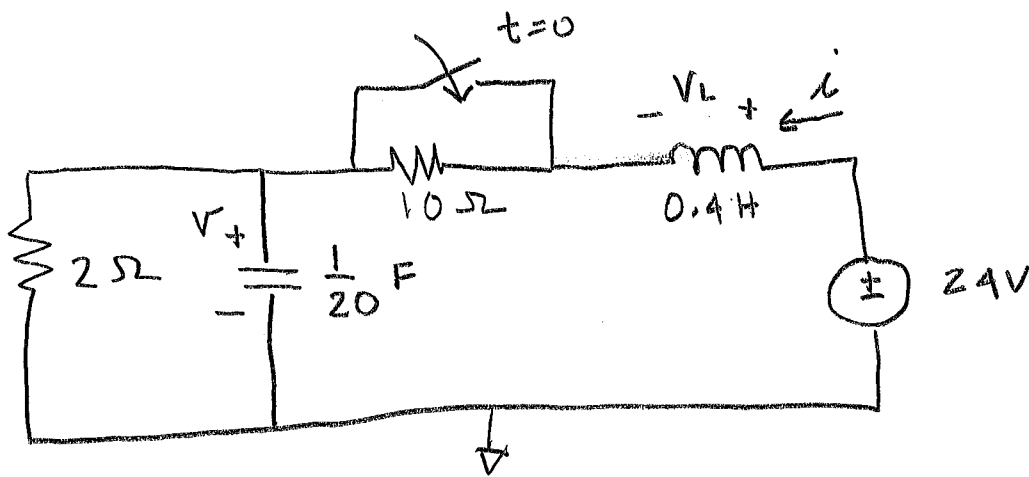

$$\underline{i(0^-)} = \frac{24}{10+2} = 2\text{A}, \quad \underline{i(0^+)} = i(0^-) = 2\text{A}$$

$$\underline{V(0^-)} = \frac{2}{10+2} \times 24 = 4\text{V}, \quad \underline{V(0^+)} = V(0^-) = 4\text{V}$$


$$\underline{\frac{di(0^+)}{dt}} \quad V_L = L \frac{di}{dt} \quad \text{so} \quad \underline{\frac{di}{dt}(0^+)} = \frac{V_L(0^+)}{L}$$

Since  $V_C(0^+) = V_C(0^-) = 4\text{V}$  and switch is closed,

$$V_L(0^+) = 24 - 4 = 20\text{V}$$

$$\text{so} \quad \underline{\frac{di}{dt}(0^+)} = \frac{V_L(0^+)}{L} = \frac{20}{0.4} = 50\text{A/s}$$

Does the sign make sense?

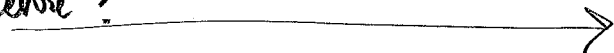


# Practice problem 8.1 CONT

LECTURE #2

6


$\frac{dv}{dt}(0^+)$

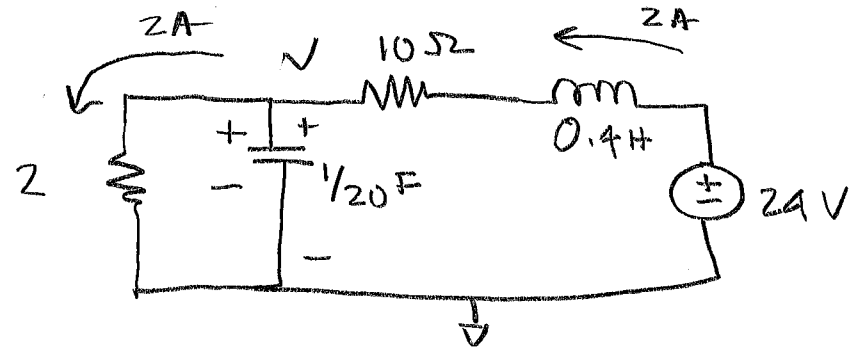$i = C \frac{dv}{dt}$  so  $\frac{dv}{dt} = \frac{i}{C}$



At  $t = 0^-$  There is no current in capacitor


at  $t = (0^+)$

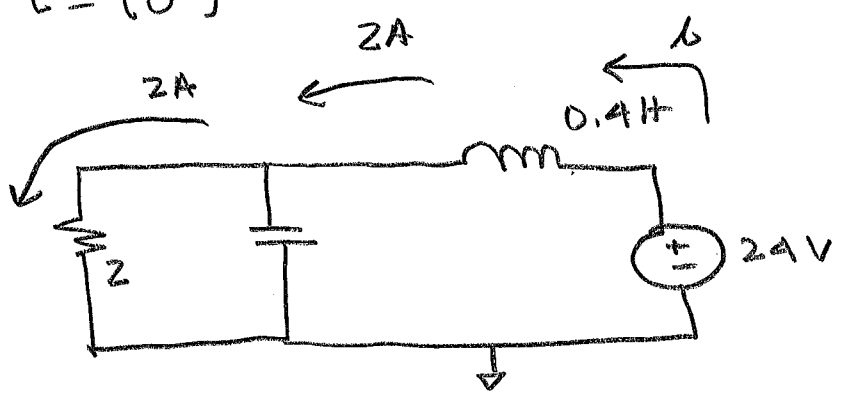

At  $t = 0^+$ , Capacitor current is zero!

so  $\frac{dv}{dt}(0^+) = \frac{i}{C} = \frac{0}{C} = 0 \text{ V/sec}$

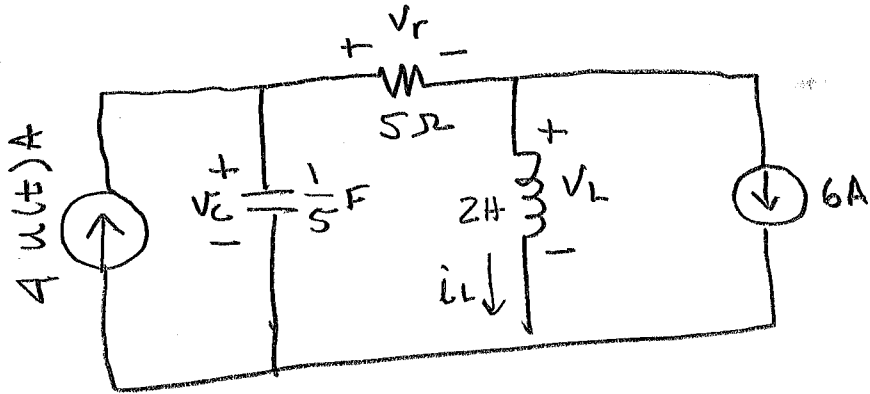$i_{\infty} = \frac{24 \text{ V}}{2 \Omega} = 12 \text{ A}$  ,  $V_{\infty} = 24 \text{ V}$



$$\underline{i_L(0^+)} = i_L(0^-) = -6A, \quad V_C(0^-) = V_C(0^+) = 0V$$

$$\underline{V_R(0^+)} = 5\Omega \times i_R(0^+) = 5 \times 0 = 0 \quad (\text{step current goes into cap.})$$

$$\underline{\frac{d i_L}{dt}(0^+)} = \frac{V_L(0^+)}{L} = 0 \frac{A}{s} \quad (\text{all step current goes in cap.})$$


$$\underline{\frac{d V_C}{dt}(0^+)} = \frac{i_C(0^+)}{C} = \frac{4}{1/5} = 20 \frac{V}{s}$$

$$\underline{\frac{d V_R}{dt}(0^+)} = 20 \text{ V/s} \quad \text{answer in book is wrong!}$$

$$i_L(\infty) = 4A - 6A = -2A$$

$$V_C(\infty) = 4A \times 5\Omega = 20V$$
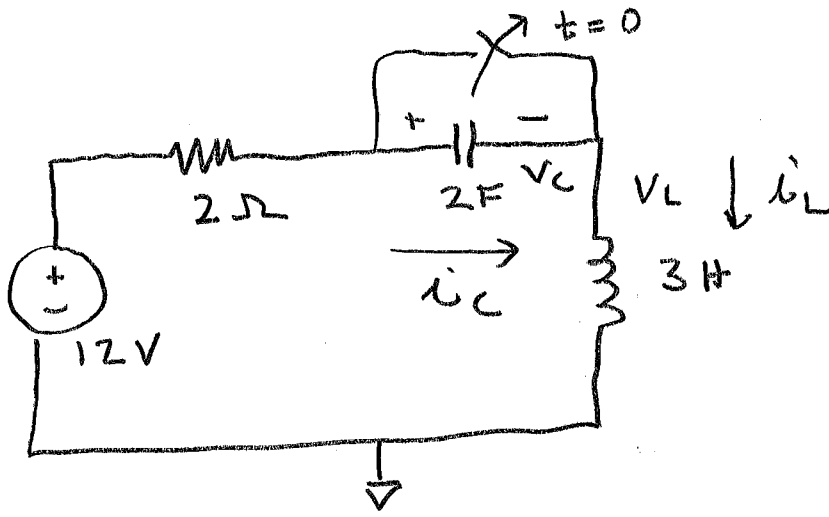
$$V_R(\infty) = 4A \times 5\Omega = 20V$$



$$V_L(0^-) =$$

$$i_L(0^-) =$$

$$i_L(0^+) =$$

$$i_C(0^-) =$$

$$i_C(0^+) =$$

$$V_C(0^-) =$$

$$V_C(0^+) =$$

$$V_L(0^+) =$$

$$\frac{dV_C}{dt}(0^+) =$$



$$\xrightarrow{V_L(\infty)} \frac{di_L}{dt} =$$

$$V_C(\infty)$$




( PR 8.4

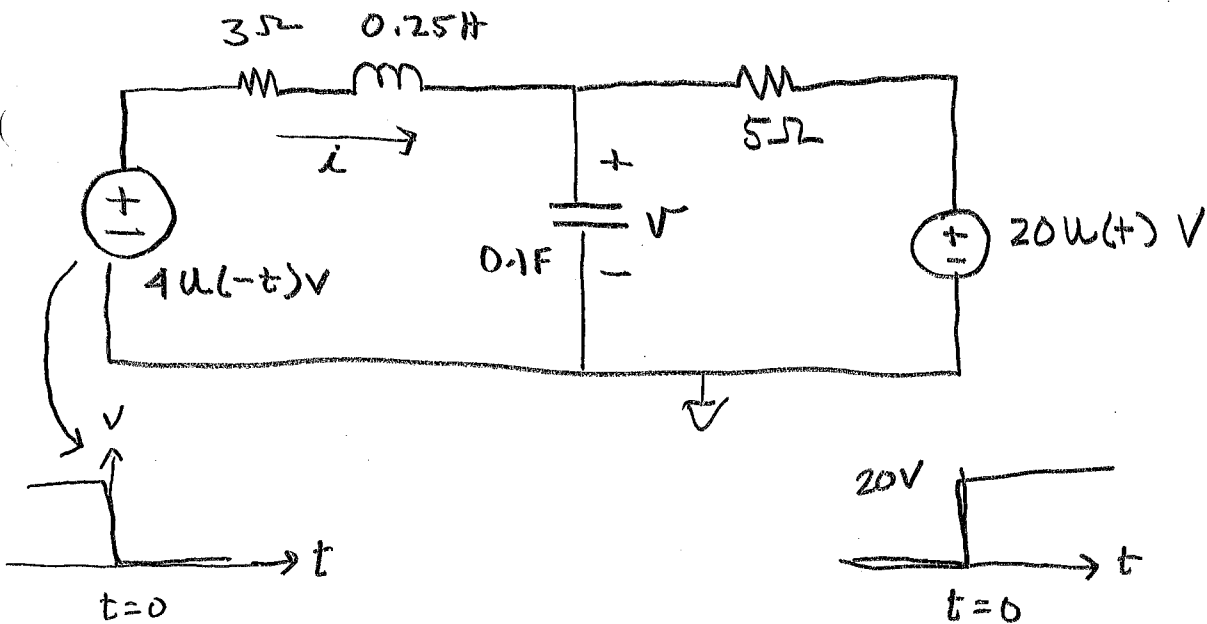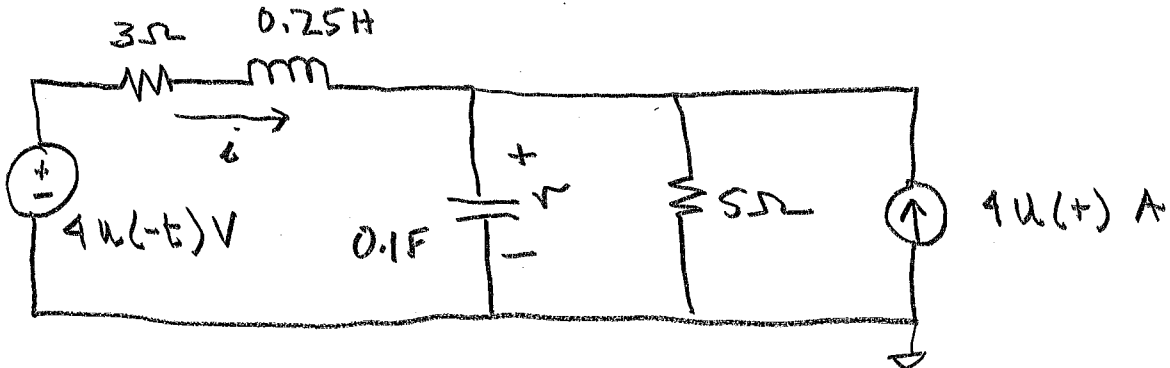
Find  $v(0^+)$ ,  $i(0^+)$ ,  $\frac{dv(0^+)}{dt}$ ,  $\frac{di(0^+)}{dt}$ ,  $v_{\infty}$ ,  $i_{\infty}$



At  $t=0^-$  we have

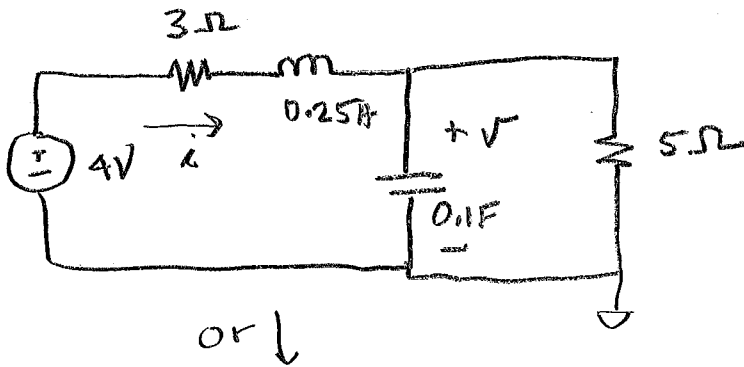

or ↓

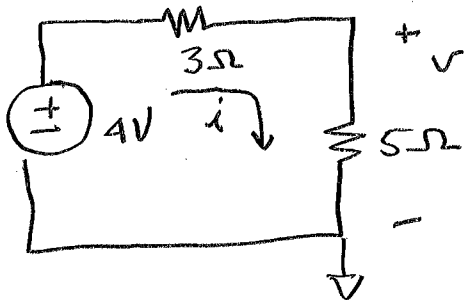


$$V = \frac{5}{5+3} \times 4 = 2.5V$$

$$i = \frac{4}{3+5} = \frac{1}{2}A$$

Note  $V(0^+) = V(0^-)$  and  $i(0^+) = i(0^-)$

At  $t=0^+$  we have

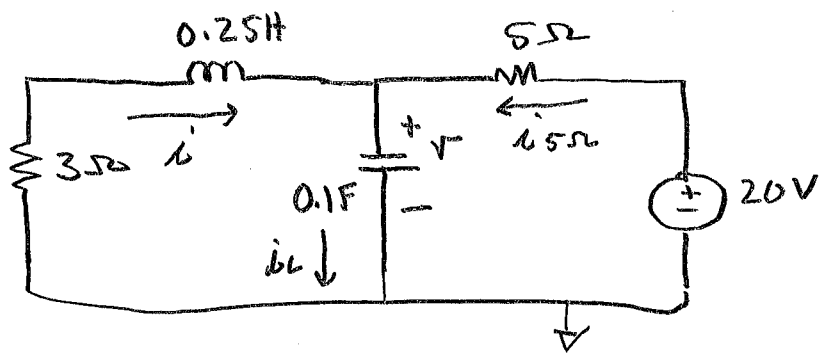


$$i(0^+) = i(0^-) = 0.5 \text{ A}, \quad v(0^+) = v(0^-) = 2.5 \text{ V}$$

$$i(5\Omega) = \frac{20 - 2.5}{5} = 3.5 \text{ A}$$

$$\text{so } i_C = 0.5 + 3.5 = 4 \text{ A}$$

$$i_C(0^+) = C \frac{dv_C(0^+)}{dt} \quad \text{so} \quad \frac{dv_C}{dt} = \frac{i_C}{C} = \frac{4}{0.1} = \underline{40 \text{ V/s}}$$

find  $\frac{di}{dt}(0^+)$

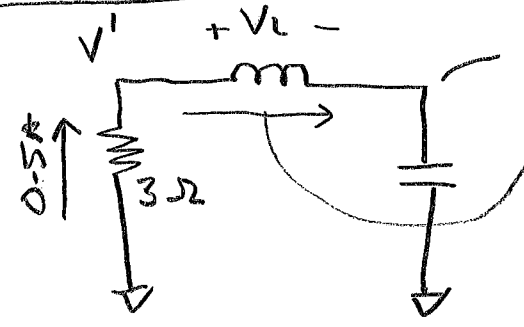

at  $t=0^+$ ,  $v_C = 2.5 \text{ V}$


at  $t=0^+$ ,  $i = 0.5 \text{ A}$

$$\text{so } V' = -1.5 \text{ V}$$

$$\begin{aligned} \text{and } V_L &= V' - v \\ &= -1.5 - 2.5 = -4 \text{ V} \end{aligned}$$

$$V_L = L \frac{di}{dt}, \quad \frac{di}{dt} = \frac{V}{L} = \frac{-4}{0.25} = \underline{-16 \text{ A/s}}$$

At  $t = \infty$

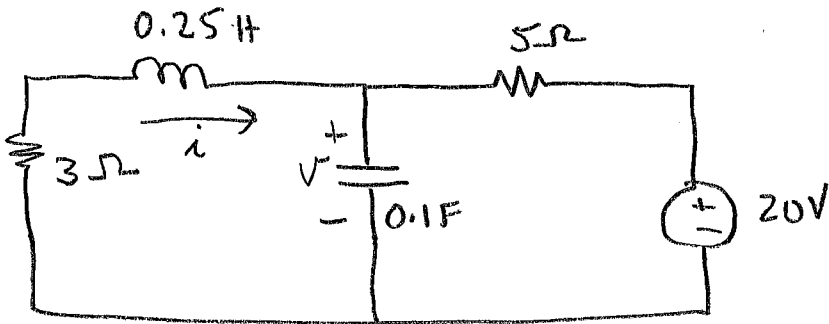

$$V_o = \frac{3}{3+5} \times 20 = \underline{7.5V}$$

$$i_o = \frac{-20}{5+3} = \underline{-2.5A}$$