



# LECTURE 25

## Circuit Element Models Sec 16.2

These models work for steady state AND transient analysis.

Resistor   $v(t) = R \cdot i(t)$ ,  $V(s) = R \cdot I(s)$

Inductor   $v(t) = L \frac{di}{dt}$


Use time differentiation property

$$V(s) = L [s I(s) - i(0^-)]$$

Solving for  $I(s)$  gives

$$I(s) = \frac{1}{sL} V(s) + \frac{i(0^-)}{s}$$


so Equivalent circuit models are

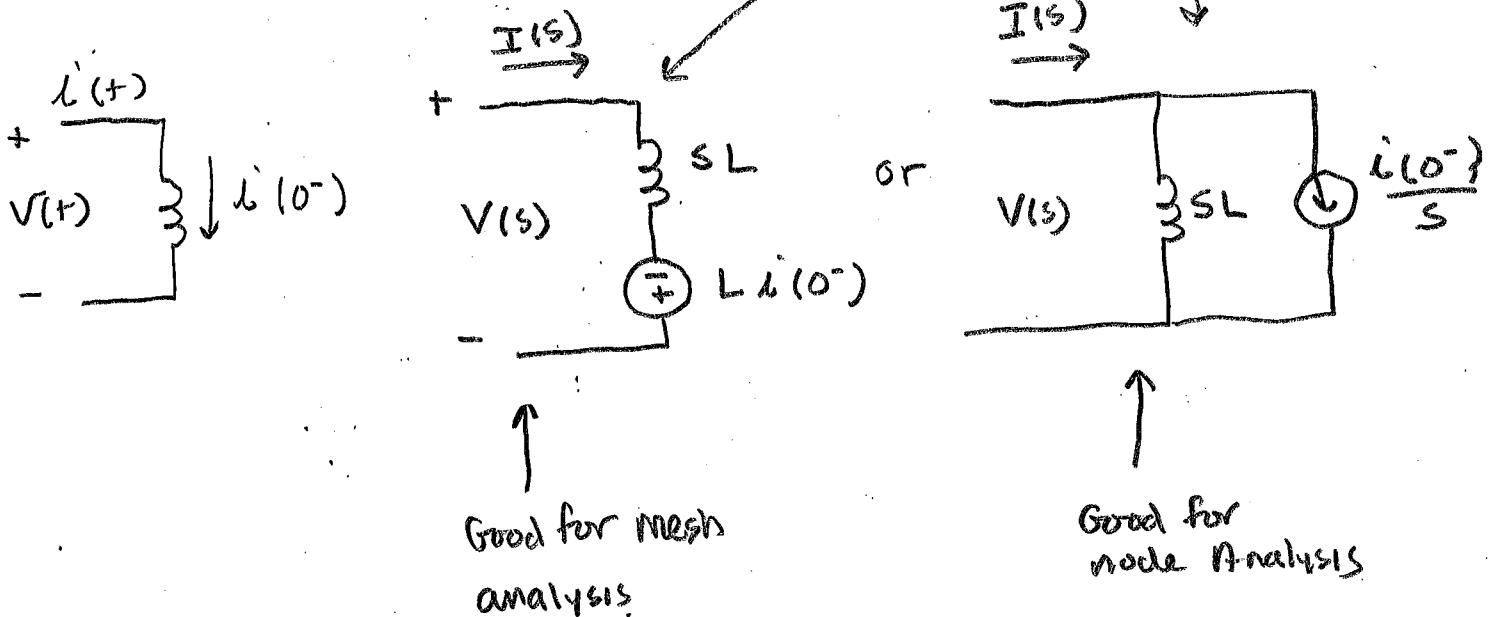

Capacitor   $i(t) = C \frac{dv}{dt}$

so  $I(s) = C [s V(s) - V(0^-)]$

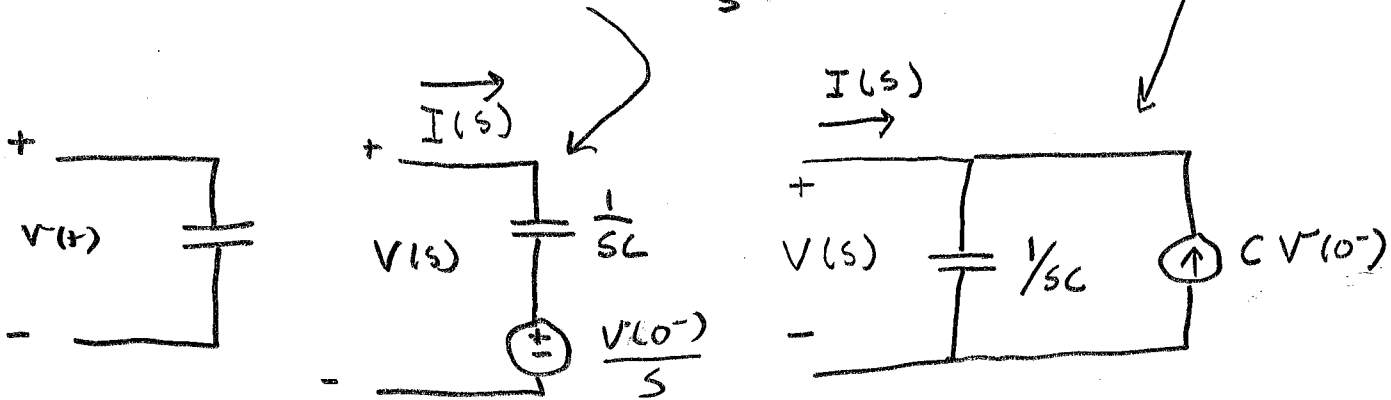or  $V(s) = \frac{1}{sC} I(s) + \frac{V(0^-)}{s}$



(if initial conditions are zero then .

Resistor  $V(s) = R \cdot I(s)$

Inductor  $V(s) = sL I(s)$

Capacitor  $V(s) = \frac{1}{sC} I(s)$

} Look familiar?


so "Impedance in the s-domain is the ratio of the voltage transform to the current transform under zero initial conditions"

} pg 718

"Bridge" between steady state and transient.

# Practice Problem 16.1

L3

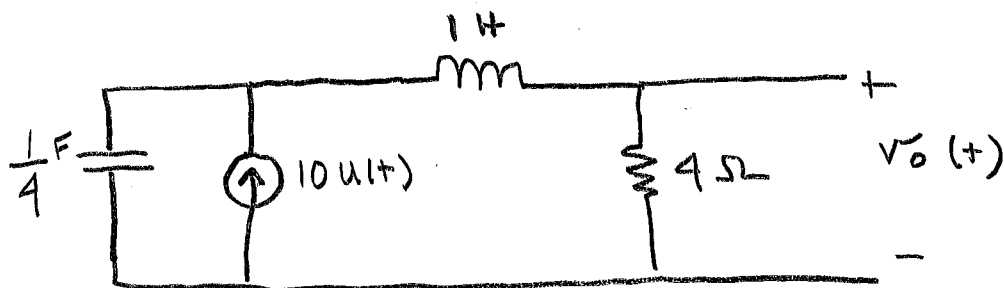


Find  $v_o(t)$

All initial conditions are zero

## Strategy

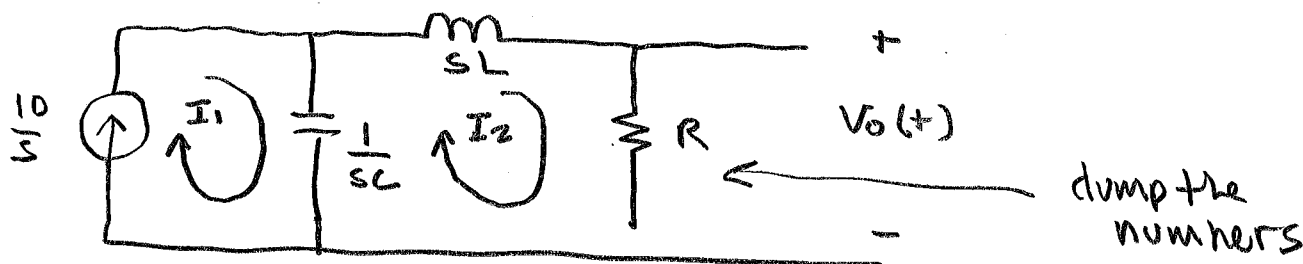- 1) Transform circuit from time domain to s-domain
- 2) Determine transfer function  $\frac{V_o(s)}{I(s)}$
- 3) Compute  $\int^{-1} \{ I(s) \cdot H(s) \} = v_o(t)$



s-domain equivalent

①  $I_1 = \frac{10}{s}$       ③  $V_o = I_2 R$  or  $I_2 = \frac{V_o}{R}$

②  $\frac{1}{sC} (I_2 - I_1) + sL I_2 + I_2 R = 0$

② using ①  $\frac{1}{sC} (I_2 - \frac{10}{s}) + sL I_2 + I_2 R = 0$

② using ③  $\frac{1}{sC} (\frac{V_o}{R} - \frac{10}{s}) + sL \frac{V_o}{R} + \frac{V_o}{R} \times R = 0$

we will just solve for  $V_o(s)$

$$\textcircled{2} \quad \frac{V_0}{sCR} - \frac{10}{s^2C} + \frac{sLV_0}{R} + V_0 = 0$$

$$V_0 \left[ \frac{1}{sCR} + \frac{sL}{R} + 1 \right] = \frac{10}{s^2C}$$

$$V_0 = \frac{10}{s^2C} \times \frac{1}{\frac{1}{sCR} + \frac{sL}{R} + 1}$$

$$V_0 = 10 \times \frac{1}{\frac{s}{R} + \frac{s^3LC}{R} + s^2C}$$

$$V_0 = 10 \times \frac{1}{s \left( \frac{s^2LC}{R} + sC + \frac{1}{R} \right)}$$

$$V_0 = \frac{10}{LC/R} \times \frac{1}{s \left( s^2 + \frac{sR}{L} + \frac{1}{LC} \right)}$$

Why is "characteristic equation" the same as Eq 8.87?

Is this two simple poles or two complex poles "Thud or boing"?

$$s^2 + s \times \frac{4}{1} + \frac{1}{1 \times \frac{1}{4}}$$

$$= s^2 + 4s + 4 = (s+2)^2$$

It's a repeated pole

$$V_o(s) = 160 \times \frac{1}{s(s+2)^2}$$

→ Get inverse Laplace using Properties to study for final.

That was a lot of work. Let's check with initial and final value theorems

$$f(0) = \lim_{s \rightarrow \infty} \{s F(s)\} = \lim_{s \rightarrow \infty} \left\{ 160 \times \frac{1}{(s+2)^2} \right\} = 0 \text{ V}$$

$$f(\infty) = \lim_{s \rightarrow 0} \left\{ \frac{160}{(s+2)^2} \right\} = 40 \text{ V}$$

Does this agree with the circuit?

### Partial fractions

Strategy:

1) USE Eq 15.54 (Guarantee)

$$\frac{160}{s(s+2)^2} = \frac{K_1}{(s+2)^2} + \frac{K_2}{s+2} + \frac{K_3}{s}$$

2) Use method of Algebra to get  $K_1, K_2, K_3$

$$\frac{160}{s(s+2)^2} = \frac{K_1 s + K_2 s(s+2) + K_3 (s+2)^2}{s(s+2)^2}$$

Equate numerators

$$160 = K_1 s + K_2 s^2 + 2K_2 s + K_3 s^2 + 4K_3 s + 4K_3$$

$$160 = s^2(k_2 + k_3) + s(k_1 + 2k_2 + 4k_3) + 4k_3$$

So

$$\begin{bmatrix} 0 & 1 & 1 \\ 1 & 2 & 4 \\ 0 & 0 & 4 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \\ k_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 160 \end{bmatrix}$$

and  $k_1 = -80$   
 $k_2 = -40$   
 $k_3 = 40$

So  $H(s) = \frac{160}{s(s+2)^2} = \frac{-80}{(s+2)^2} - \frac{40}{s+2} + \frac{40}{s}$

$$h(t) = [-80te^{-2t} - 40e^{-2t} + 40]u(t)$$

$$= 40 [1 - e^{-2t} - 2te^{-2t}]u(t)$$

check it!


$$f(0) \stackrel{40}{=} (1 - 1 - 0) = 0 \quad \checkmark$$

$$f(\infty) = 40 [1 - 0 - 0] \quad \checkmark$$

Practice Problem 16.1

Find  $v_o(t)$

... The chapter 8 way

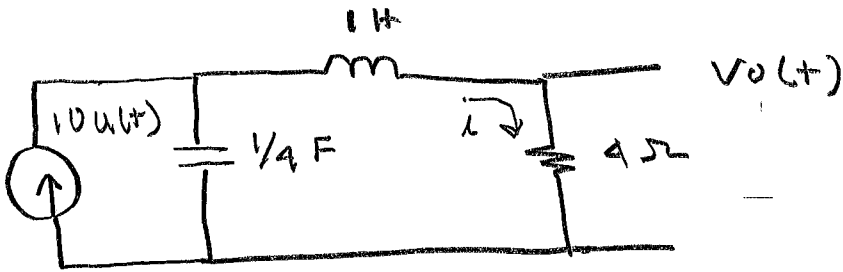

Series RLC

$$\alpha = \frac{R}{2L} = \frac{4}{2} = 2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$V_o(\infty) = V_s = ?$$

$$V_o(0^+) = ?$$

$$\frac{dv_o}{dt}(0^+) = ?$$

since  $\alpha = \omega_0$  it is critically damped

General form

$$r(t) = R_s + (A_1 + A_2 t) e^{-\alpha t}$$

or  $v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t}$

$$v(0^+) = 0 \quad \text{why?} \quad V_s = V_\infty = 40 \quad \text{why?}$$

$$A_1 = v(0^+) - V_s = 0 - 40 = -40$$

$$A_2 = \frac{dv}{dt}(0^+) + \alpha A_1$$

$$\hookrightarrow = R \frac{di}{dt} = 4 \times 0 = 0$$

so

$$A_2 = 0 + \alpha A_1 = 2 \times -40 = -80$$

$$v(t) = 40 + (-40 - 80t) e^{-2t}$$

See "chapter 8 - useful equations" under study materials

Same as we got with Laplace x form

Problem 16.2

$$\frac{d^2V}{dt^2} + 5 \frac{dV}{dt} + 4V = 0$$

Given  $V(0) = 0$ ,  $\frac{dV}{dt}(0) = 5 \text{ V/s}$ , find  $V(t)$

Convert to Laplace domain

$$\underbrace{\frac{d^2V}{dt^2}}_{\text{time differentiation}} + \underbrace{5 \frac{dV}{dt}}_{\text{time differentiation}} + 4V = 0$$

$$\left( s^2 V(s) - s \cdot V(0) - \underbrace{V'(0)}_{=5} \right) + 5 \left( s V(s) - \underbrace{V(0)}_{=0} \right) + 4V(s) = 0$$

$$s^2 V + 5sV + 4V - 5 = 0$$

$$V(s^2 + 5s + 4) = 5$$

$$\text{or } V = \frac{5}{s^2 + 5s + 4} = \frac{5}{(s+4)(s+1)}$$

Use method of algebra

$$\frac{5}{s^2 + 5s + 4} = \frac{A_1}{s+4} + \frac{A_2}{s+1} = \frac{A_1(s+1) + A_2(s+4)}{s^2 + 5s + 4}$$

$$\text{so } \frac{5}{s^2 + 5s + 4} = \frac{A_1 s + A_1 + A_2 s + 4A_2}{s^2 + 5s + 4}$$



$$5 = 5(A_1 + A_2) + A_1 + 4A_2$$

$$\begin{aligned} \text{so } A_1 + A_2 &= 0 & A_1 &= -5/3 \\ A_1 + 4A_2 &= 5 & A_2 &= 5/3 \end{aligned}$$

$$\text{so } v(t) = -\frac{5}{3}e^{-4t} + \frac{5}{3}e^{-t}$$

check using  $v(0^-)$  and  $\frac{dv}{dt}(0^-)$


$$v(0) = -\frac{5}{3} + \frac{5}{3} = 0 \quad \checkmark$$

$$\frac{dv}{dt} = \frac{4 \times 5}{3} e^{-4t} - \frac{5}{3} e^{-t}$$

$$\frac{dv}{dt}(0) = \frac{20 - 5}{3} = \frac{15}{3} = 5 \quad \checkmark$$

No need to check answer. I'm comfortable with this!

Problem 16.39

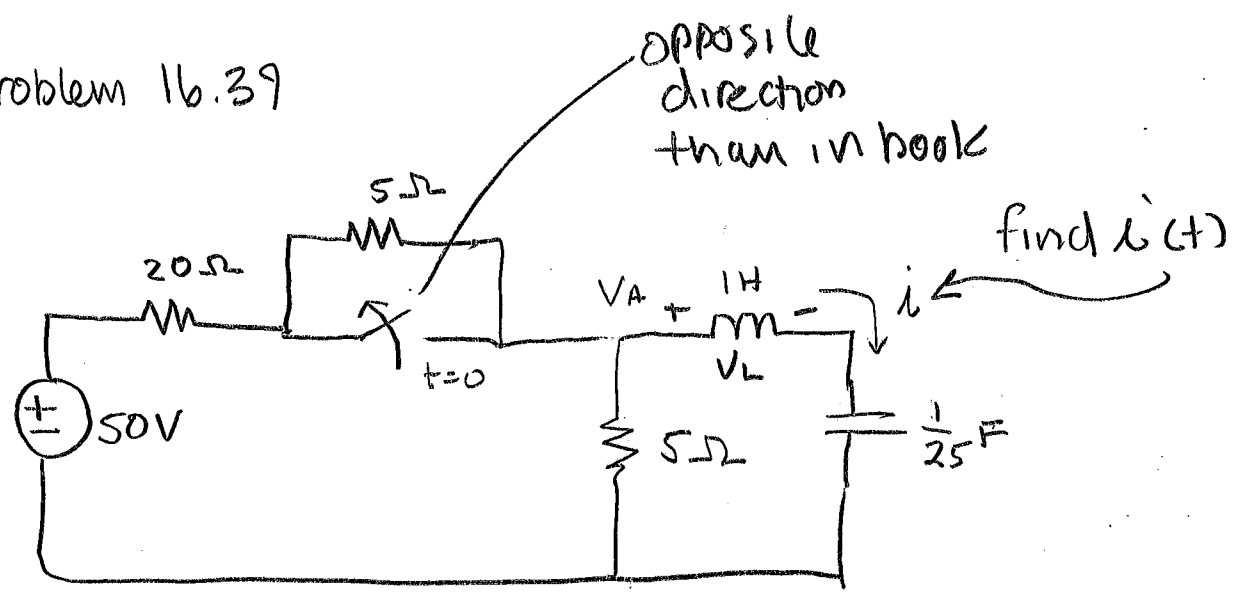

Triage

- What are  $V_A$  and  $i$  at  $t=0^-$ ?
- What is  $i$  at  $t=0^+$ ?
- What is  $V_A$  at  $t=0^+$ ?
- What is  $di/dt$  at  $t=0^+$ ?
- What kind of circuit is this?
- Are differential equations or Laplace the best method?


$$V_A(0^-) = \frac{5}{25} \times 50 = 10V$$

$$V_A(0^+) = \frac{5}{30} \times 50 = 8.33V$$

$$\text{so } V_L(0^+) = 8.33 - 10 = -1.67V$$

$$\frac{di_L}{dt} = \frac{-1.67}{1H} = -1.67A/s$$
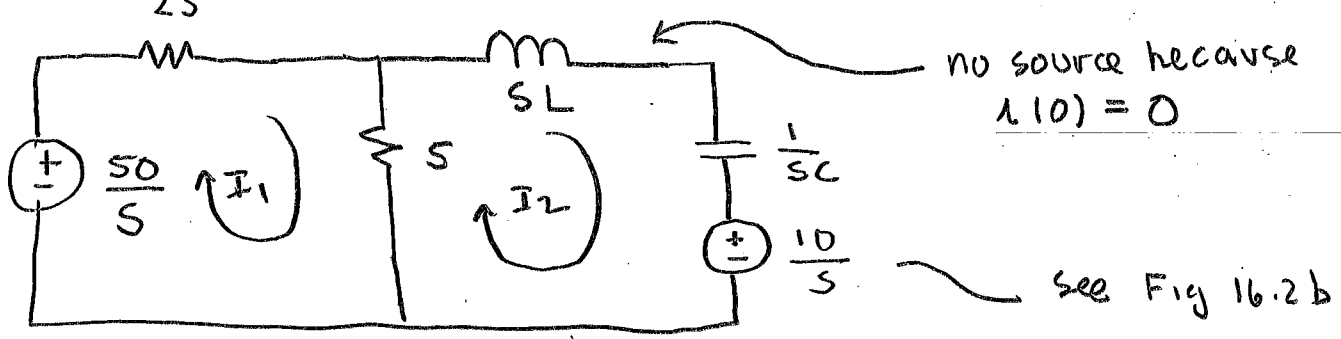
$$V_C(0^-) = V_C(0^+) = 50 \times \frac{5}{5+20} = 10V$$



Note that we don't need derivatives ( $\frac{dV_C(0^+)}{dt}, \dots$ ) with Laplace, just initial conditions

$$\textcircled{1} -\frac{50}{s} + 25I_1 + 5(I_1 - I_2) = 0$$

$$\textcircled{2} 5(I_2 - I_1) + sLI_2 + \frac{I_2}{sC} + \frac{10}{s} = 0$$

$$\textcircled{1} -\frac{50}{s} + 25I_1 + 5I_1 - 5I_2 = 0$$

$$\textcircled{1} 5I_2 = 25I_1 + 5I_1 - \frac{50}{s}$$

$$\textcircled{1} I_2 = 6I_1 - \frac{10}{s}$$

$$\textcircled{2} 5I_2 - 5I_1 + sLI_2 + \frac{I_2}{sC} + \frac{10}{s} = 0$$

$$I_2(5 + sL + \frac{1}{sC}) - 5I_1 = -\frac{10}{s}$$

$$\textcircled{2} (6I_1 - \frac{10}{s})(5 + sL + \frac{1}{sC}) - 5I_1 = -\frac{10}{s}$$

$$\textcircled{2} 30I_1 + 6I_1sL + \frac{6I_1}{sC} - \frac{50}{s} - 10L - \frac{10}{s^2C} - 5I_1 = -\frac{10}{s}$$





YUK - - -

Note Thevenin transformation easily converts this to a single loop . . . .


Re-start →

PR 16.39 CONT

12

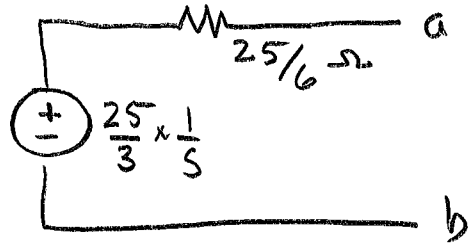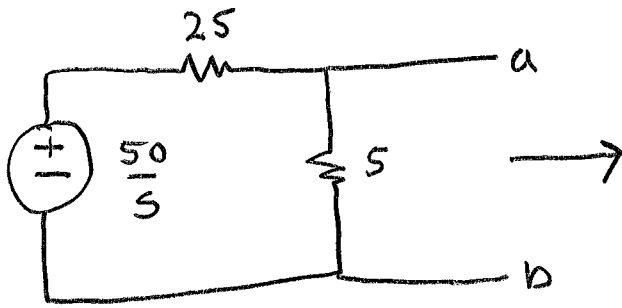
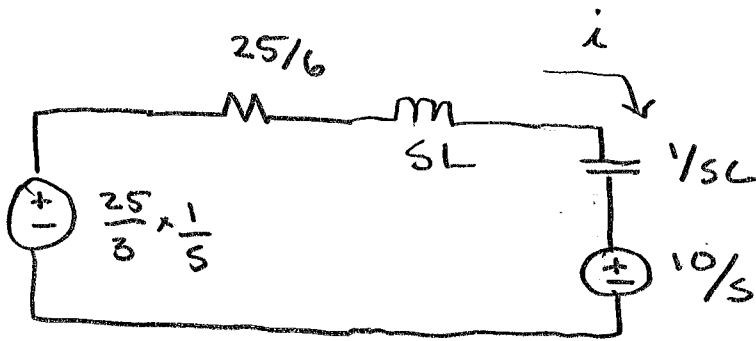
$$V_{Th} = \frac{50}{s} \times \frac{5}{25+5} = \frac{25}{3} \times \frac{1}{s}, \quad R_{Th} = \frac{5 \times 25}{5+25} = \frac{125}{30} = \frac{25}{6}$$



$$-\frac{25}{3} \times \frac{1}{s} + \frac{25}{6} I + SLI + \frac{I}{sC} + \frac{10}{s} = 0$$

$$I \left( \underset{\uparrow 4.17}{\frac{25}{6}} + SL + \frac{1}{sC} \right) = \left( \underset{\uparrow 8.33}{\frac{25}{3}} - 10 \right) \times \frac{1}{s}$$

$$I = \frac{-1.667}{s} \times \frac{1}{4.17 + SL + 1/sC}$$

$$I = \frac{-1.667}{s^2L + 4.17s + 1/c}$$

$$I = \frac{-1.667}{s^2 + 4.17s + 25} \quad \sqrt{b^2 - 4ac} \text{ is neg}$$

$$I(s) = \frac{-1.667}{s^2 + 4.17s + 25} = \frac{A_1 s + A_2}{s^2 + 4.17s + 25} \quad \leftarrow \text{GUARANTEE}$$

$\uparrow$  a                       $\uparrow$  b

Equate coeffs,  $A_1 = 0$ ,  $A_2 = -1.667$

Use formulas we derived in class

$$k = \frac{a}{2} = \frac{4.17}{2} = 2.08, \quad B = \sqrt{b - \frac{a^2}{4}} = \sqrt{25 - \frac{4.17^2}{4}}$$

$$= 4.54$$

and  $B_1 = \frac{A_2 - A_1 k}{B} = \frac{-1.667 - 0}{4.54} = -0.3672$

EQ 15.65

So  $i(t) = -0.3672 e^{-2t} \sin(4.54t) u(t) = i(t)$

disagrees with book because our switch opened at  $t=0$

Check against circuit.

$$i(0) = -0.3672 e^0 \sin(0) = 0$$


$$\frac{di}{dt} = -0.3672 \left[ -2e^{-2t} \sin(4.54t) + e^{-2t} \times 4.54 \times \cos(4.54t) \right]$$

$$= -0.3672 \times 4.54 = \underline{-1.667 \text{ A/s}}$$

Which agrees with result on pg 10

Find  $V_A/V_S$

We must assume initial cond are 0.

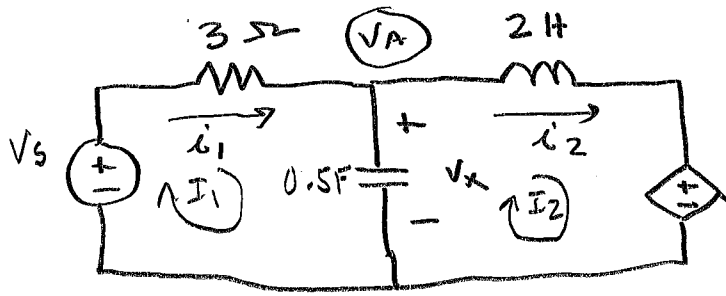

$4V_x \rightarrow V_x = (I_1 - I_2) \times \frac{1}{5C}$

①  $-V_S + 3I_1 + \frac{1}{5C} (I_1 - I_2) = 0$

②  $(I_2 - I_1) \frac{1}{5C} + 5L I_2 + 4(I_1 - I_2) \times \frac{1}{5C}$

mesh approach

Node will give me a single equation

$\frac{V_S - V_A}{3} - \frac{V_A}{1/5C} + \frac{4V_A - V_A}{5L} = 0$  (dep source)

$V_A \left( -\frac{1}{3} - 5C + \frac{3}{5L} \right) = -\frac{V_S}{3}$

$V_A = -\frac{V_S}{3} \times \frac{1}{\frac{3}{5L} - 5C - \frac{1}{3}}$

$\frac{V_A}{V_S} = \frac{1}{3 \left( \frac{1}{3} + 5C - \frac{3}{5L} \right)} = \frac{1}{1 + 35C - \frac{9}{5L}}$

$\frac{V_A}{V_S} = \frac{5}{35^2 C + 5 - 9/L} = \frac{1}{3C} \times \frac{5}{5^2 + \frac{5}{3C} - \frac{9}{3LC}}$

$$\text{so } \frac{V_A}{V_S} = \frac{2}{3} \left[ \frac{s}{s^2 + 2/3s - 3} \right]$$

Say we input a unit step. what would the circuit do?

Now let's look at the math

$$V_A = \frac{1}{s} \times \frac{2}{3} \times \frac{s}{s^2 + 2/3s - 3}$$

$$= \frac{2}{3} \times \frac{1}{(s - 1.4288)(s + 2.1)}$$

pole is in right half plane!

$$= \frac{k_1}{s - 1.43} + \frac{k_2}{s + 2.1}$$

$$\text{and } f(t) = k_1 e^{1.43t} + k_2 e^{-2.1t}$$

Does this justify what you observe from the circuit?

Say the dependent source was  $-4V_x$  instead of  $4V_x$ , then

16

$$\frac{V_s - V_A}{R} - \frac{V_A}{1/SC} + \frac{-4V_A - V_A}{SL} = 0$$

$$\text{or } \frac{V_A}{V_s} = \frac{1}{RC} \times \frac{S}{S^2 + \frac{1}{RC}S + \frac{5}{LC}}$$

$$\frac{V_A}{V_s} = \frac{2}{3} \times \frac{S}{S^2 + 0.667S + 5}$$

What would the circuit do if we input a unit step?

Now the math...

$$V_A(s) = \frac{1}{s} \times \frac{2}{3} \times \frac{S}{(S^2 + 0.667S + 5)}$$

$$\text{Poles are } p_1, p_2 = \frac{-0.67 \pm \sqrt{0.67^2 - 20}}{2}$$

Real part is negative so stable.

Final value

$$f(\omega) = \lim_{s \rightarrow 0} (sF(s)) = \lim_{s \rightarrow 0} \left\{ \frac{2}{3} \times \frac{S}{S^2 + 0.667S + 5} \right\}$$

$$= 0$$

See LT SPICE file posted on Blackboard