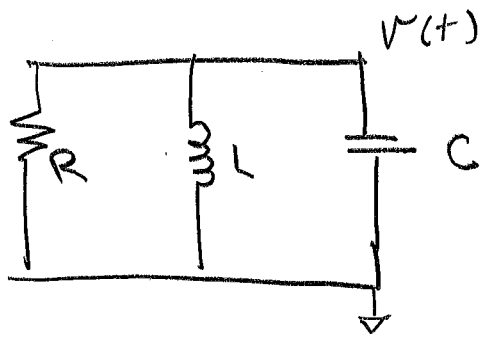


Source-Free Parallel RLC Circuit

Section 8.4

Lecture 4

110



KCL at top node

$$V_L = L \frac{di}{dt} \quad \text{so} \quad i_L(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

KCL gives

$$\underbrace{\frac{v}{R}}_{\text{Resistor}} + \underbrace{\frac{1}{L} \int_{-\infty}^t v(\tau) d\tau}_{\text{inductor}} + \underbrace{C \frac{dv}{dt}}_{\text{capacitor}} = 0$$

Take the derivative and divide by C

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

Assume solutions are $v = Ae^{st}$

$$\text{So } \frac{d^2v}{dt^2} = s^2 \cdot Ae^{st} \quad \text{and} \quad \frac{dv}{dt} = sAe^{st}$$

and our equation becomes

12

$$s^2 A e^{st} + \frac{1}{RC} s A e^{st} + \frac{1}{LC} A e^{st} = 0$$

factoring out $A e^{st}$ gives the characteristic equation

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \quad \text{EQ 8.30}$$

Compare to characteristic equation for series RLC

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Series RLC

EQ 8.7

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

Parallel RLC

EQ 8.30

We find the roots with quadratic formula


$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

α α^2 ω_0^2

Again compare series and parallel

	α	ω_0
Series	$R/2L$	$1/\sqrt{LC}$
Parallel	$1/2RC$	$1/\sqrt{LC}$

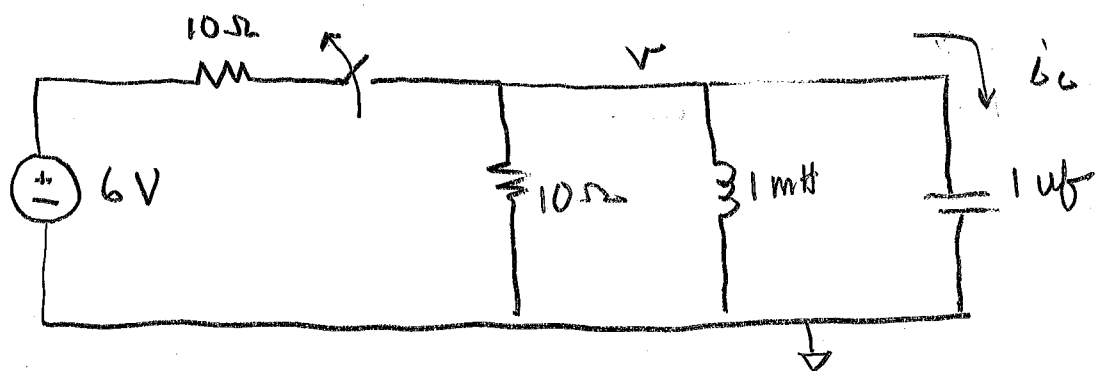Other than this, the analysis is the same



find $v(t)$ for $t > 0$
 Strategy \rightarrow find $v(t)$ \rightarrow not always the same!

Initial conditions

inductor is a short at DC, so $I_L(0^-) = I_L(0^+) = 6/10 = 600 \text{ mA}$
 Capacitor voltage = inductor voltage = 0 at $t=0^-$ and $t=0^+$

Now get dv/dt .

At $t=0^+$, current in inductor cannot change.

- $V = 0$, so NO current in 10Ω resistor.
- Therefore all current comes from capacitor. and $i_c(0^+) = -600 \text{ mA}$

Since $i = C \frac{dv}{dt}$, $\frac{dv}{dt} = \frac{i}{C} = \frac{-0.6}{1\mu\text{F}} = -600,000 \text{ V/S}$

So $v(0^+) = 0 \text{ V}$, $\frac{dv}{dt}(0^+) = -600,000 \text{ V/S}$

initial conditions

Determine the type of response

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 10^{-6}} = 50 \times 10^3$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 31.6 \times 10^3$$

Since $\alpha > \omega_0$, it is over damped and

$$r(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Use r because it works for voltage, current, pressure...



$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\frac{dv}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$v(0^+) = A_1 + A_2 = 0$$

$$\frac{dv(0^+)}{dt} = A_1 s_1 + A_2 s_2 = -600 \text{ K V/S}$$

So $A_1 + A_2 = 0$

$$A_1 s_1 + A_2 s_2 = -600 \text{ K}$$



$$\begin{bmatrix} 1 & 1 \\ s_1 & s_2 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -600K \end{bmatrix}$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left[\frac{1}{2RC}\right]^2 - \frac{1}{LC}}$$

$$\left. \begin{aligned} s_1 &= -11.27e3 \\ s_2 &= -88.73e3 \end{aligned} \right\}$$

doesn't matter which is s_1, s_2 provided you use them consistently in the equation

$$\begin{bmatrix} 1 & 1 \\ -11.27e3 & -88.73e3 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -600K \end{bmatrix}$$


$$A_1 = -7.746, A_2 = 7.746$$

So $V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$V(t) = -7.746 e^{-11.27e3 t} + 7.746 e^{-88.73e3 t}$$

See LTSpice and Excel implementations on Blackboard.


Example

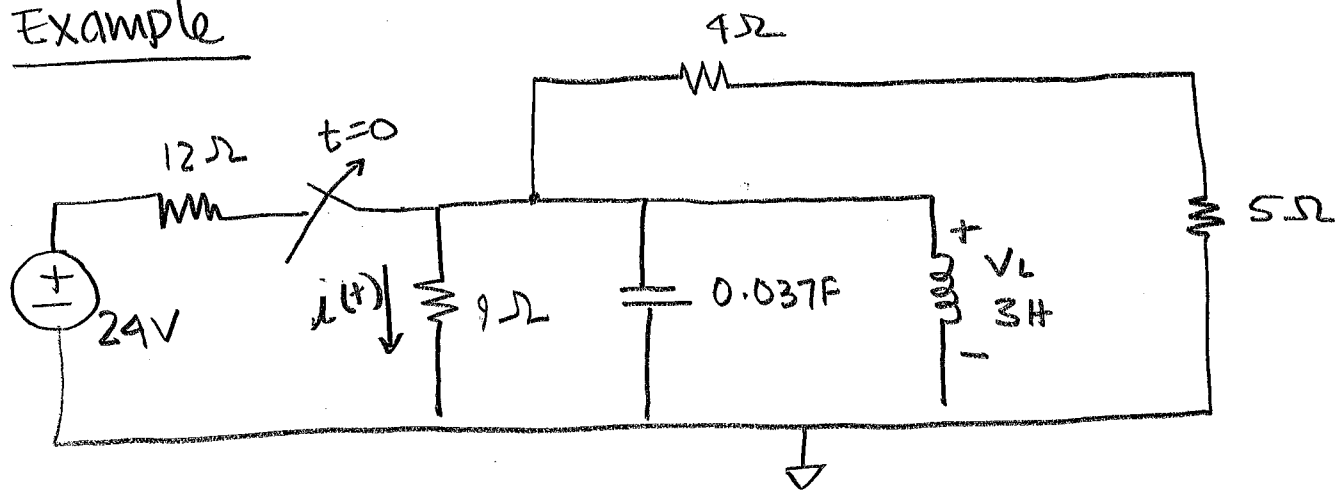

Find $i(t)$

Tricky?

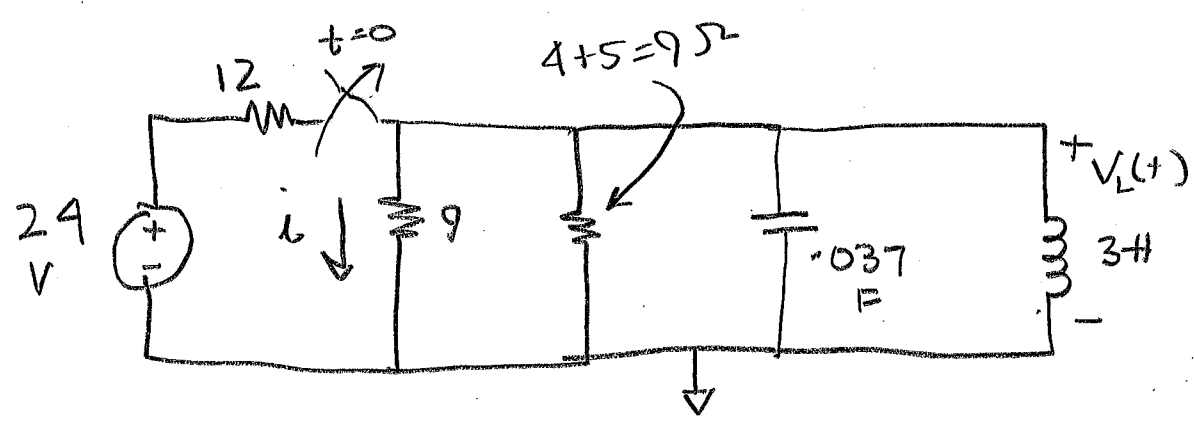- 1) The 4 and 5 Ω Resistors make weird topology.
- 2) Asking for i instead of V for Parallel RLC



Strategy

- 1) solve for $V_L(t)$
- 2) $i(t) = \frac{V_L(t)}{9}$

Since we are solving for $v_L(t)$, we need initial conditions $v_L(0^+)$ and $\frac{dv_L}{dt}(0^+)$

at $t = 0^-$, $v_L = 0$, $i_L = 0$

$$i_L(0^+) = i_L(0^-) = \frac{24V}{12\Omega} = 2A$$

When switch opens,

- 1) Capacitor voltage remains at 0. $\rightarrow v_C(0^+) = 0$
- 2) No current in resistors
- 3) Inductor current remains 2A
- 4) Capacitor current is -2A

for cap $i = C \frac{dv}{dt}$ so $\frac{dv}{dt} = \frac{i}{C} = \frac{-2}{0.037} = -54.05 \text{ V/s}$

Summarize initial conditions, $v_L(0^+) = 0$

$$\frac{dv_L}{dt}(0^+) = -54.05 \text{ V/s}$$



Next determine the response type

Topology is parallel RLC so

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 4.5 \times 0.037} = 3$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3 \times 0.037}} = 3$$

so it's critically damped.

Use equations from previous lecture

$$V_L(t) = (A_2 + A_1 t) e^{-\alpha t}$$

$$A_2 = V_L(0^+) = 0$$

$$A_1 = \frac{d(V_L)}{dt} + \alpha A_2 \overset{\rightarrow 0}{=} -54.05$$

$$\text{So } \underline{V_L(t) = -54.05 t e^{-3t}}$$

Check result before converting to i

$$\text{We know } V_L(0^+) = 0$$

$$-54.05 \times 0 \times e^{-3t} = 0V \checkmark$$



We know $\frac{dv}{dt}(0^+) = -54.05 \text{ V/s}$

19

$$\frac{d}{dt} [-54.05 t e^{-3t}]$$

$$= -54.05 e^{-3t} + 3 \times 54.05 t e^{-3t}$$

$$= -54.05 \text{ V/s}$$

We know $V_L(\infty) = 0 \rightarrow$ all energy lost

$$\lim_{t \rightarrow \infty} [-54.05 t e^{-3t}] = \infty \times 0 \quad \text{uh-oh}$$

$$\lim_{t \rightarrow \infty} \left[-54.05 \frac{t}{e^{+3t}} \right] = \frac{-\infty}{\infty}$$

use L'Hopital's Rule

$$-54.05 \times \frac{1}{3e^{3t}} = -54.05 \times \frac{1}{\infty} = 0 \quad \checkmark$$

Now get final answer by dividing $V(t)$ by 9Ω

$$i(t) = \frac{V(t)}{9} = -6 t e^{-3t} \text{ amp}$$

