

# LECTURE #6

## GENERALIZED SECOND ORDER CIRCUITS

### SEC 8.7


We have worked with series RLC and parallel RLC.

Now we will work with any circuit with two energy storage elements.

### STEPS (Pg 339)

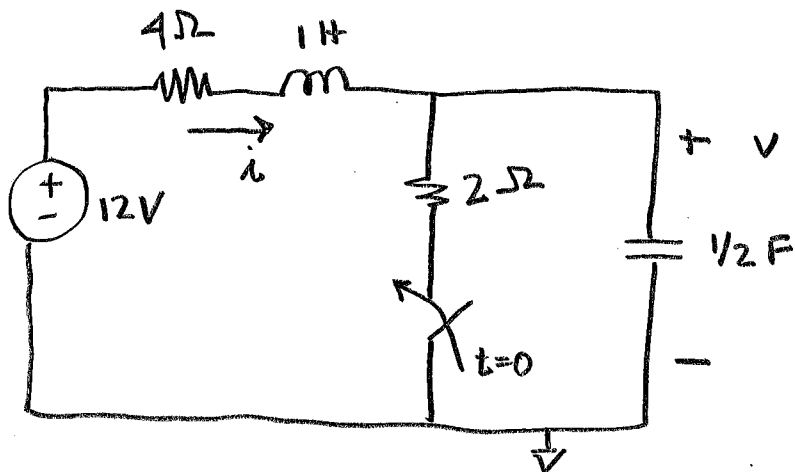- 1) find  $r(0^+)$ ,  $\frac{dr}{dt}(0^+)$ , and  $r(\infty)$   
    ↙ (these can be interchanged)  
    ↘
- 2) Turn off independent sources, use KVL/KCL to write a differential equation. Obtain the transient response
- 3) Add in the steady state response,  $r_{ss} = r(\infty)$
- 4) Final result  $r(t) = r_t(t) + r_{ss}$   
                        ↑                          ↓  
                        transient                 steady state


Find the complete response for  $v$  and then  $i$



← Neither series nor parallel RLC

Step 1 - Initial and final conditions


At  $t=0^-$

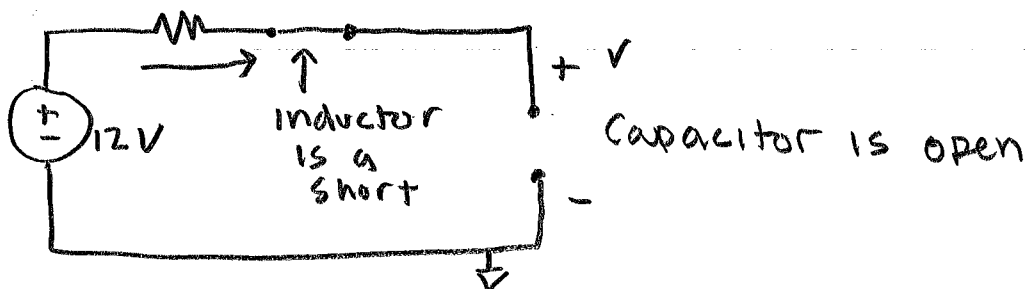

So  $v(0^+) = v(0^-) = 12V$

$i(0^+) = i(0^-) = 0A$

Get  $\frac{dv}{dt}$

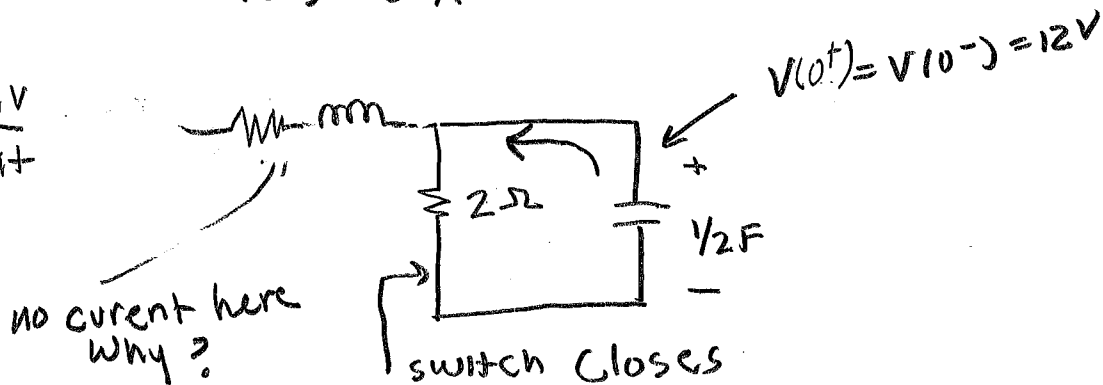


Capacitor current =  $-\frac{12}{2} = -6A$ ,  $\frac{dv}{dt} = \frac{i}{C} = \frac{-6}{1/2} = -12 \frac{V}{s}$

Get  $\frac{di}{dt}$        $\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L}$

Capacitor voltage does not change, 12 V source doesn't change  
 So inductor voltage does not change and  $\frac{di}{dt} = 0 \text{ A/s}$


Final conditions

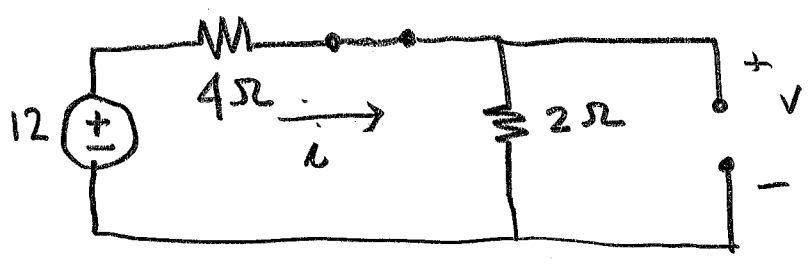

$$V(\infty) = \frac{2}{4+2} \times 12 = 4 \text{ V}$$

$$i(\infty) = \frac{12}{4+2} = 2 \text{ A}$$

STEP 2

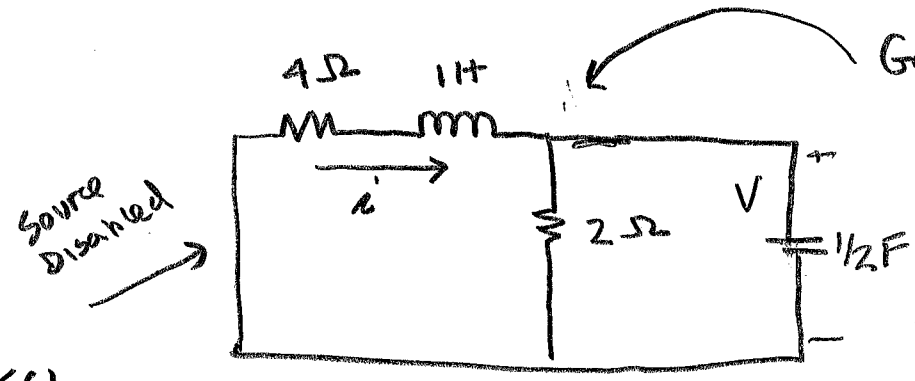

Get transient with KCL at this node

KCL

$$-i + \frac{V}{2} + C \frac{dV}{dt} = 0 \quad \leftarrow \text{sum currents leaving node to zero}$$

This is one equation in two unknowns.

write KVL in left mesh ( $i$  is mesh current)

$$4i + L \frac{di}{dt} + V = 0 \quad \text{so now we have 2 eqs in 2 unk.}$$

# EQUATIONS

①  $i = \frac{V}{2} + C \frac{dv}{dt}$  ← from KCL

②  $4i + L \frac{di}{dt} + V = 0$  ← from KVL

Let's substitute ① into ②

$4 \left[ \frac{V}{2} + C \frac{dv}{dt} \right] + L \left[ \frac{1}{2} \frac{dv}{dt} + C \frac{d^2v}{dt^2} \right] + V = 0$  ← UGLY, but 1 EQ IN 1 UNK

$\frac{d}{dt}$  OF ① IS  $di/dt$

$-C \frac{d^2v}{dt^2} + (4C + \frac{1}{2}L) \frac{dv}{dt} + 3V = 0$

$\frac{1}{2} \frac{d^2v}{dt^2} + 2.5 \frac{dv}{dt} + 3V = 0$

see eq 8.7 for this step

$\frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6 = 0 \implies s^2 + 5s + 6 = 0$   
roots are -2, -3

So  $V_n(t) = Ae^{-2t} + Be^{-3t}$   
natural response  
eq 8.9.6

Both roots are distinct and real so overdamped (Book doesn't say this)

Important note: I could have picked ANY voltage or current and I would get the same characteristic Eqn and same  $s_1, s_2$ , (book doesn't emphasise this)

Use the equation from page 2 of lecture #3 for overdamped circuit.

$$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ s_1 & s_2 \end{bmatrix}^{-1} \begin{bmatrix} r(0^+) - R_s \\ \frac{dr}{dt}(0^+) \end{bmatrix}$$

Solve for  $V(t)$  transient

$$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -2 & -3 \end{bmatrix}^{-1} \times \begin{bmatrix} 8 \\ -12 \end{bmatrix}$$

$V(0^+) - V_\infty$

$\frac{dV}{dt}(0^+)$

So  $A_1 = 12, A_2 = -4$

$$V(t) = 12e^{-2t} - 4e^{-3t}$$

transient voltage response

Now get transient current response

$$i_n(t) = A_1 e^{-2t} + A_2 e^{-3t}$$

Same procedure as above

$$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -2 & -3 \end{bmatrix}^{-1} \begin{bmatrix} -2 \\ 0 \end{bmatrix}$$

$i(0^+) - i_\infty$

$-\frac{di}{dt}(0^+)$

$A_1 = -6, A_2 = 4$

$$i_n(t) = -6e^{-2t} + 4e^{-3t}$$

transient current response

Step 3 add in steady state

$$v(t) = 4 + 12e^{-2t} - 4e^{-3t}$$

↑  
 $v_{\infty}$

$$i(t) = 2 - 6e^{-2t} + 4e^{-3t}$$

↑  
 $i_{\infty}$

Quick check:


We know  $v(0) = 12V$

$$v(0) = 4 + 12 \times e^0 - 4e^0 = 12 \quad \checkmark$$

We know  $i(0) = 0A$

$$i(0) = 2 - 6e^0 + 4e^0 = 0 \quad \checkmark$$

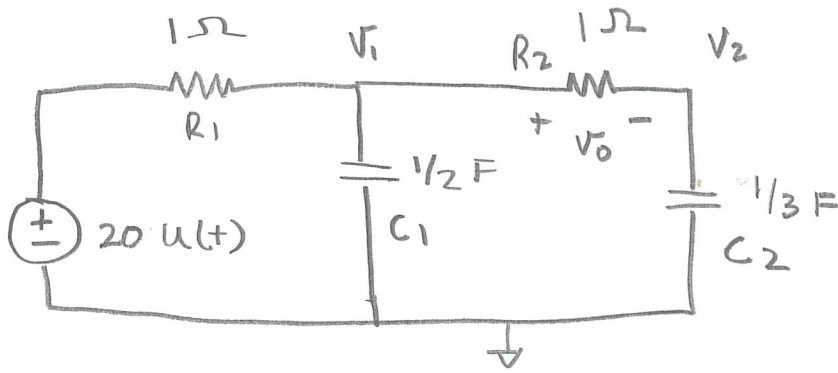We could check with  $\frac{d}{dt}$  of the equations also



Find  $V_0(t)$  Hint: (first find  $V_1$  and  $V_2$ )

①  $\frac{V_1}{1} + C_1 \frac{dV_1}{dt} + \frac{(V_1 - V_2)}{1} = 0$  } Where does this equation come from?

↑  
disable 20V

for  $V_2$ , I know  $i = C \frac{dv}{dt}$  in cap and resistor

So  $C_2 \frac{dV_2}{dt} \times R + V_2 = V_1$  } Where does this equation come from?

Voltage in resistor  $V_2$  is voltage across  $C_2$

Substitute ② into ①

①  $\left[ C_2 \frac{dV_2}{dt} R + V_2 \right] + C_1 \left[ C_2 \frac{d^2 V_2}{dt^2} + \frac{dV_2}{dt} \right] + \left[ C_2 \frac{dV_2}{dt} + V_2 \right] - V_2 = 0$

Subst for  $V_1$   $dV_1/dt$

UGLY BUT  
1 EQ IN 1 UNK

$$C_1 C_2 \frac{d^2 V_2}{dt^2} + (C_2 + C_1 + C_2) \frac{dV_2}{dt} + V_2 = 0$$

$$\frac{1}{6} \frac{d^2 V_2}{dt^2} + \left(\frac{2}{3} + \frac{1}{2}\right) \frac{dV_2}{dt} + V_2 = 0$$

$$\frac{d^2 V_2}{dt^2} + 7 \frac{dV_2}{dt} + 6V_2 = 0$$

$$s^2 + 7s + 6 = 0 \quad \leftarrow \text{Characteristic EQN}$$

roots are -1, -6

At this point we know the roots. Furthermore they are real and distinct, so circuit response is over damped

$$V_0 = V_{0ss} + A_1 e^{-t} + A_2 e^{-6t}$$

Get initial and final conditions

$$V_0(0^-) = 0, \text{ No current in cap}$$

$$V_0(\infty) = 0, \text{ No current in cap}$$

$$\frac{dV_0(0^+)}{dt} = \frac{40V}{s} \quad \text{why?} \quad V_{C_1}(0^+) = V_{C_1}(0^-) = 0$$

$$I_{C_1} = \frac{20V}{1 \Omega} = 20 A, \quad \frac{dV_{C_1}}{dt} = \frac{20}{1/2} = 40V/s$$

$$I_{C_2}(0^+) = 0, \quad \frac{dV_{C_2}}{dt} = 0 \quad \text{so} \quad \frac{dV_0}{dt} = 40V/s$$



Use our equation for overdamped.

8

$$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ s_1 & s_2 \end{bmatrix}^{-1} \begin{bmatrix} v(0^+) \\ dv/dt(0^+) \end{bmatrix} \quad \left. \begin{array}{l} -V_0 \\ \text{which is zero} \end{array} \right\}$$


$$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -1 & -6 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 40 \end{bmatrix} = \begin{bmatrix} 8 \\ -8 \end{bmatrix}$$

$$A_1 = 8, \quad A_2 = -8$$


and so

$$v_0 = 8e^{-t} - 8e^{-6t}$$

# INTRODUCTION TO OP-AMPS FOR EE-310

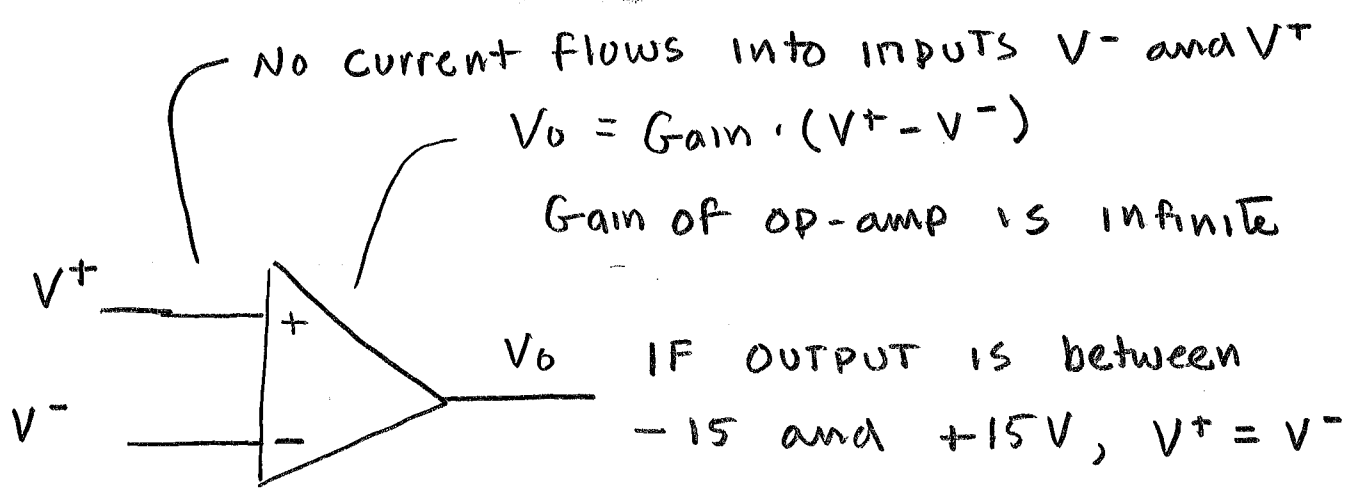

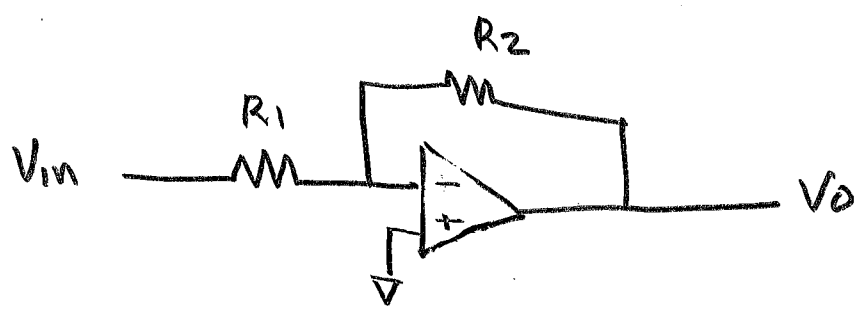Gain of op amp is infinite. What is the gain of this circuit?




KCL at inverting terminal: (No current into  $V^-$ )

Also, since  $V^+ = V^-$ ,  $V^- = 0$

$$\frac{V_{in}}{R_1} + \frac{V_o}{R_2} = 0, \quad \frac{V_{in}}{R_1} = -\frac{V_o}{R_2} \quad \text{or} \quad \text{Gain} = \frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$

"Inverting Configuration"

What is the gain of this circuit?

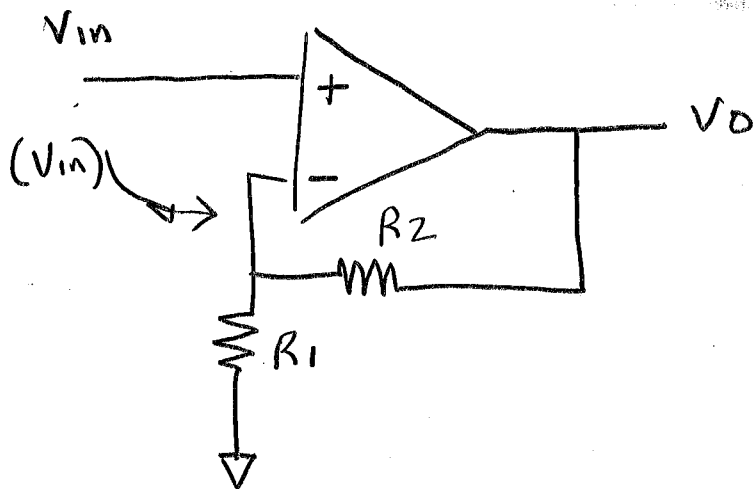

Use KCL again. Remember  $V^+ = V^- = V_{in}$

$$\frac{V_{in}}{R_1} = \frac{V_O - V_{in}}{R_2}$$

$$V_{in} R_2 = R_1 (V_O - V_{in}) = R_1 V_O - R_1 V_{in}$$

$$V_O R_1 = V_{in} R_2 + V_{in} R_1$$


$$V_O R_1 = V_{in} (R_2 + R_1)$$

$$\text{or } \frac{V_O}{V_{in}} = \text{Gain} = \frac{R_2 + R_1}{R_1}$$


"Non-inverting configuration"

PRACTICE PROBLEM 8.11, PG 346

find  $v_o(t)$

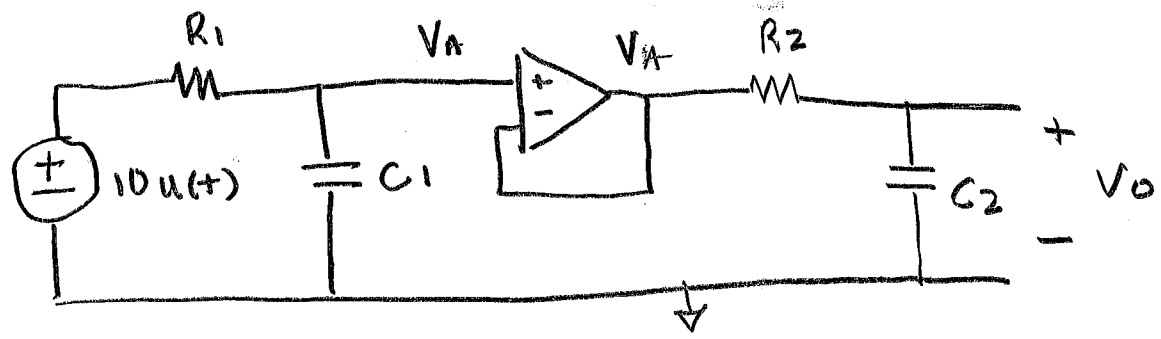

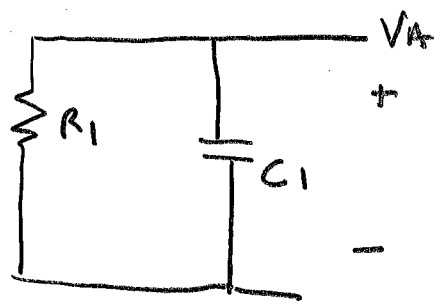STEP 1 - GET CHARACTERISTIC EQN AND SOLVE.



$$\textcircled{1} \quad \frac{v_A}{R_1} + C_1 \frac{dv_A}{dt} = 0$$

Capacitor Current

SINCE OP AMP GAIN IS 1,

$$\textcircled{2} \quad \frac{v_A - v_o}{R_2} = C_2 \frac{dv_o}{dt}$$

current in  $R_2$       current in  $C_2$

$$\textcircled{1} \quad \frac{v_A}{R_1} + C_1 \frac{dv_A}{dt} = 0 \quad \textcircled{2} \quad \frac{v_A - v_o}{R_2} = C_2 \frac{dv_o}{dt}$$

2 EQ IN 2 UNKNOWN

I can solve  $\textcircled{2}$  for  $v_A$

$$\textcircled{2} \quad v_A = R_2 C_2 \frac{dv_o}{dt} + v_o$$

Substitute (2) into 1

$$\frac{1}{R_1} \left[ \overbrace{R_2 C_2 \frac{dV_0}{dt} + V_0}^{V_A} + C_1 \left[ \overbrace{R_2 C_2 \frac{d^2 V_0}{dt^2} + \frac{dV_0}{dt}}^{dV_A/dt} \right] \right] = 0$$

Yeech!!!

$$R_2 C_1 C_2 \frac{d^2 V_0(t)}{dt^2} + \left( \frac{R_2 C_2}{R_1} + C_1 \right) \frac{dV_0(t)}{dt} + \frac{V_0(t)}{R_1} = 0$$

$$R_1 = R_2 = 10K, \quad C_1 = 20\mu F, \quad C_2 = 100\mu F$$

$$20E-6 \frac{d^2 V_0(t)}{dt^2} + 120E-6 \frac{dV_0(t)}{dt} + 100E-6 V_0(t)$$

$$\frac{d^2 V_0(t)}{dt^2} + 6 \frac{dV_0(t)}{dt} + 5 V_0(t) = 0$$

so  $s^2 + 6s + 5 = 0, \quad s_{1,2} = -1, -5$

STEP 2 Get initial and final conditions

$V_0(0^+) = 0$  why?

$\frac{d(V_0)}{dt}(0^+) = 0$  Voltage at  $C_1$  is 0 at  $t = 0^+$ .  
 ∴ no current into  $C_2$

$V_0(\infty) = 10V$  why?

roots are distinct and real, so over damped

STEP 3 Get  $A_1, A_2$


$$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -1 & -5 \end{bmatrix}^{-1} \begin{bmatrix} -10 \\ 0 \end{bmatrix}$$

$0 \quad -10$   
 $\leftarrow V_0(0^+) - V_{\infty}$   
 $\leftarrow -\frac{dV_0}{dt}(0^+)$

$A_1 = -12.5$   
 $A_2 = 2.5$

$$V_0(t) = 10 - 12.5e^{-t} + 2.5e^{-5t}$$

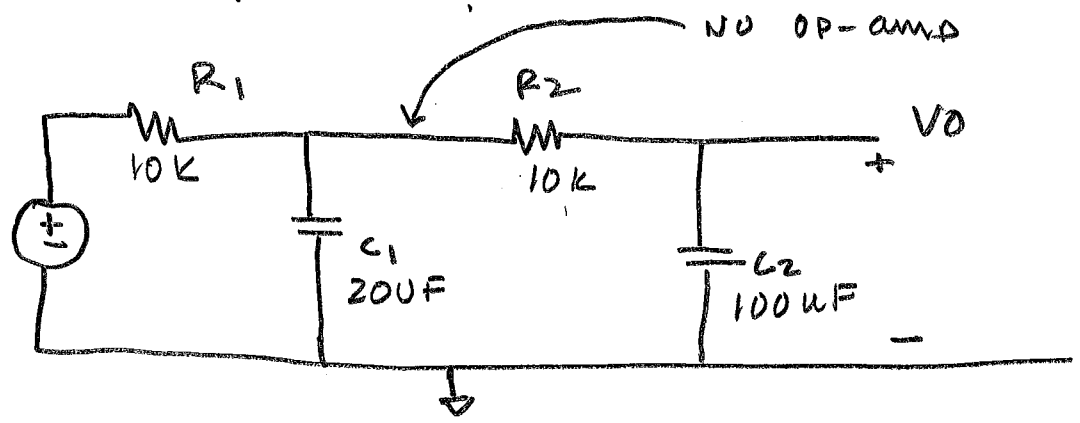What is the difference between the circuit we analyzed and the same circuit, but without the OP-amp?



# Generalized responses

1/2

## Overdamped

$$r(t) = R_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$r(0^+) = R_s + A_1 + A_2$$

$$dr/dt(0^+) = A_1 s_1 + A_2 s_2$$

so

$$\begin{bmatrix} 1 & 1 \\ s_1 & s_2 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} r(0^+) - R_s \\ dr/dt(0^+) \end{bmatrix}$$

or

$$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ s_1 & s_2 \end{bmatrix}^{-1} \begin{bmatrix} r(0^+) - R_s \\ dr/dt(0^+) \end{bmatrix}$$

## Critically damped

$$r(t) = R_s + (A_1 + A_2 t) e^{-\alpha t}$$

$$r(0^+) = R_s + A_1$$

$$\frac{dr}{dt}(0^+) = -\alpha A_1 + A_2$$

so  $A_1 = r(0^+) - R_s$

$$A_2 = \frac{dr}{dt}(0^+) + \alpha A_1$$

## Underdamped

12/2

$$r(t) = R_s + (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) e^{-\alpha t}$$

$$r(0^+) = R_s + A_1$$

$$\frac{dr}{dt} = \frac{d}{dt} \left[ R_s + A_1 \cos(\omega_d t) e^{-\alpha t} + A_2 \sin(\omega_d t) e^{-\alpha t} \right]$$

$$= -\alpha A_1 \cos(\omega_d t) e^{-\alpha t} - A_1 \omega_d \sin(\omega_d t) e^{-\alpha t} \\ + A_2 \omega_d \cos(\omega_d t) e^{-\alpha t} - \alpha A_2 \sin(\omega_d t) e^{-\alpha t}$$

$$\left. \frac{dr}{dt} \right|_{(0^+)} = -\alpha A_1 + A_2 \omega_d$$

$$\text{So } A_1 = r(0^+) - R_s$$

$$A_2 = \frac{\left. \frac{dr}{dt} \right|_{(0^+)} + \alpha A_1}{\omega_d}$$