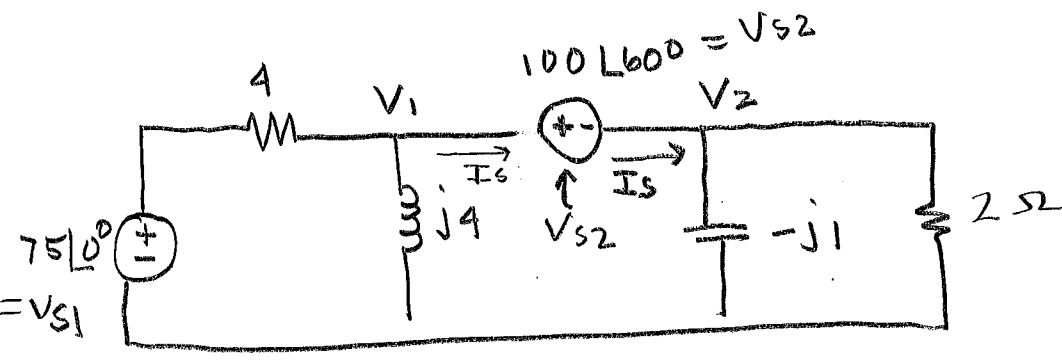


LECTURE 9 AC STEADY STATE

Practice Problem 10.2 Pg 417



Find V_1 and V_2

$$\begin{aligned} \textcircled{1} \quad & \frac{V_1 - V_{s1}}{4} + \frac{V_1}{j4} + I_s = 0 \\ \textcircled{2} \quad & -I_s + \frac{V_2}{-j1} + \frac{V_2}{2} = 0 \\ \textcircled{3} \quad & V_1 = V_2 + V_{s2} \end{aligned}$$

3 EQ, 3 UNK V_1, V_2, I_s
 Use "supernode" (Pg 417)
 if you wish

$$\begin{aligned} \textcircled{1} \quad & V_1 \left[\frac{1}{4} + \frac{1}{j4} \right] + 0 V_2 + I_s = \frac{V_{s1}}{4} \\ \textcircled{2} \quad & 0 V_1 + V_2 \left[\frac{1}{-j1} + \frac{1}{2} \right] - I_s = 0 \\ \textcircled{3} \quad & V_1 - V_2 + 0 I_s = V_{s2} \end{aligned}$$

$$V_{s1} = 75 \angle 0^\circ = 75 + j0$$


$$V_{s2} = 100 \angle 60^\circ = 50 + j86.6$$

$$\begin{bmatrix} \frac{1}{4} + \frac{1}{j4} & 0 & 1 \\ 0 & \frac{1}{-j1} + \frac{1}{2} & -1 \\ 1 & -1 & 0 \end{bmatrix}^{-1} \begin{bmatrix} V_{s1}/4 \\ 0 \\ V_{s2} \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ I_s \end{bmatrix}$$

$$V_1 = 33.63 + j90.77 \rightarrow 96.8 \angle 69.7^\circ \text{ V}$$

$$V_2 = -16.37 + j4.17 \rightarrow 16.89 \angle 165.7^\circ \text{ V}$$

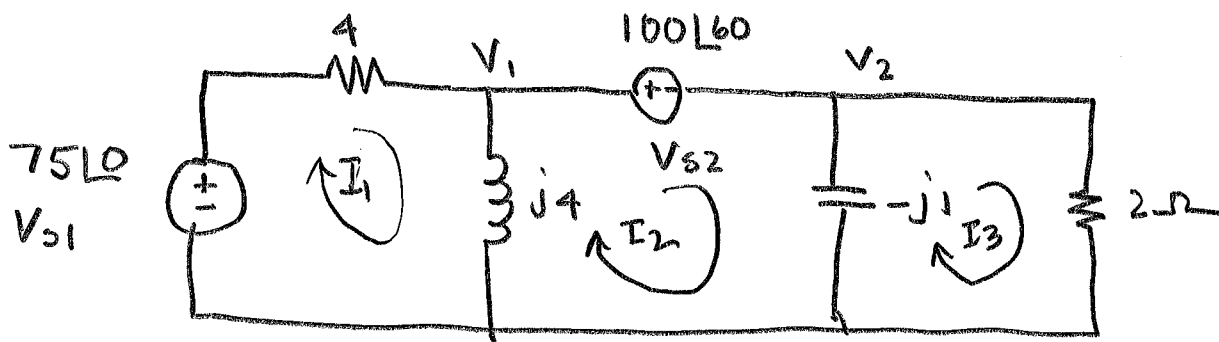Now we solve the same problem with mesh analysis



$$\textcircled{1} \quad -V_{s1} + 4I_1 + j4(I_1 - I_2) = 0$$

$$\textcircled{2} \quad j4(I_2 - I_1) + V_{s2} + -j1 \cdot (I_2 - I_3) = 0$$

$$\textcircled{3} \quad -j1(I_3 - I_2) + I_3 \times 2 = 0$$

$$\textcircled{1} [4+j4]I_1 - j4I_2 + 0I_3 = V_{s1}$$

$$\textcircled{2} -j4I_1 + [j4-j1]I_2 + j1I_3 = -V_{s2}$$

$$\textcircled{3} 0I_1 + j1I_2 + (2-j)I_3 = 0$$

$$\begin{bmatrix} 4+j4 & -j4 & 0 \\ -j4 & j4-j1 & j1 \\ 0 & j1 & 2-j \end{bmatrix}^{-1} \begin{bmatrix} V_{s1} \\ -V_{s2} \\ 0 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = 10.34 - j22.69$$

$$I_2 = -12.35 - j14.28$$

$$I_3 = -8.18 + j2.08$$

$$V_1 = \underbrace{(I_1 - I_2)}_{\text{see circuit}} \times j4 = 96.8 \angle 69.7^\circ \text{ V}$$


$$V_2 = [I_2 - I_3] \times -j1 = 16.9 \angle 165.7^\circ \text{ V}$$

Superposition in AC circuits


for any linear systems $f(a+b) = f(a) + f(b)$

This is really useful when circuit has sources with different frequencies.

Practice problem 10.6 Pg 424 (sort of)

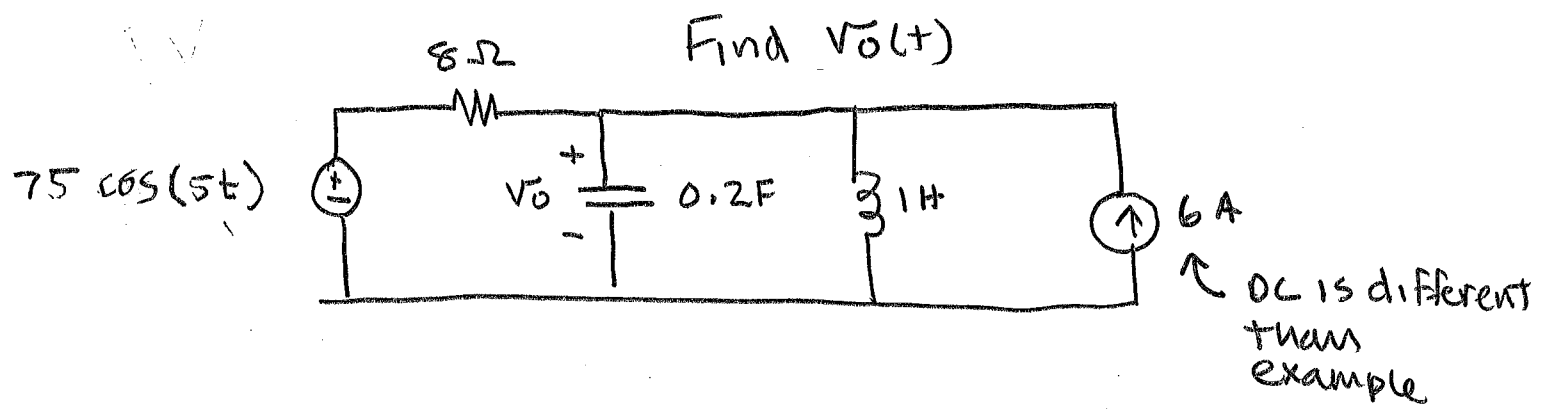

get response from AC source

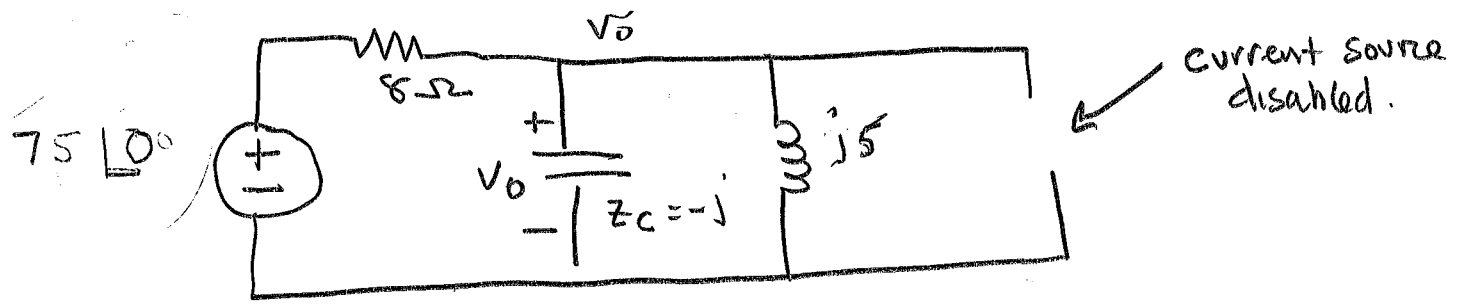

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j5 \times 0.2} = -j \quad Z_L = j\omega L = j5$$

$$V_o = \frac{Z_C // Z_L}{Z_C // Z_L + 8} \times 75 \angle 0 \quad \text{Voltage Division}$$

$$Z_C // Z_L = \frac{j5 \times -j}{j5 - j} = \frac{5}{4j} = -1.25j$$

$$\text{So } V_0 = \frac{-1.25j}{-1.25j + 8} \times 75 \angle 0 = 1.784 - j11.44 \text{ V}$$

$$= 11.58 \angle -81.12^\circ \text{ V}$$

5


Now use E_0 , 9.25

$$V(t) = V_m \cos(\omega t + \phi) \iff V = V_m \angle \phi$$

\nearrow \uparrow
 11.58 -81.12

So $V(t) = 11.58 \cos(5t - 81.12^\circ)$

Now solve for output due to DC response

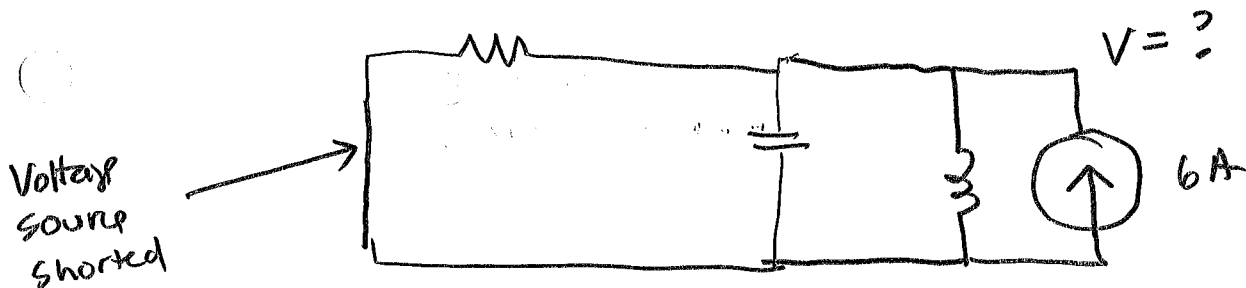


$$V(t) = 11.58 \cos(5t - 81.12^\circ)$$

Note that I set the source on the right to DC, If we used $6\cos(10t)$ as shown^{in the book}, we would have two sinewaves at different frequencies

Thevenin's theorem

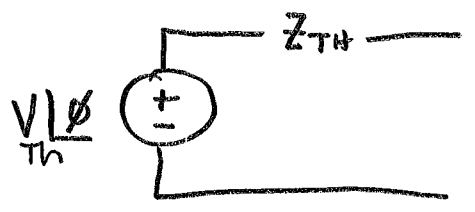Any linear source can be represented with this circuit:



We can measure V_{Th} by simply observing the open circuit voltage


We can measure Z_{Th} by shorting the voltage source and measuring the resistance.

We can also determine Z_{Th} by measuring the short circuit current. Then

$$Z_{Th} = \frac{V_{Th}}{I_{sc}}$$

Norton's Theorem


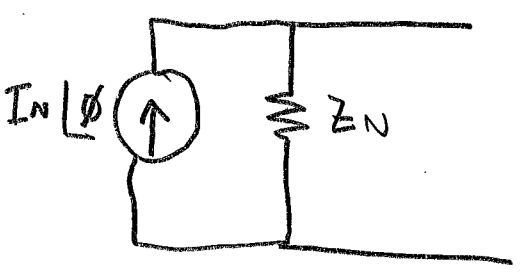
Any linear source can be represented with this circuit:



We can determine I_N by shorting the output and measuring the current.

We can determine Z_N by disabling the current source and measuring impedance.

Re-visit Problem 8.53

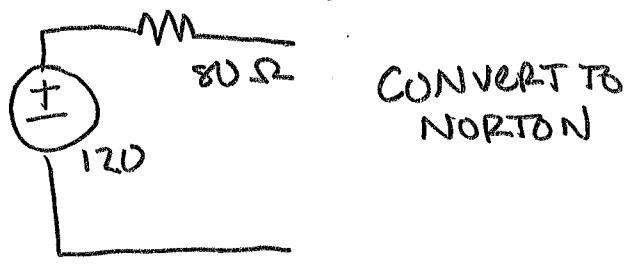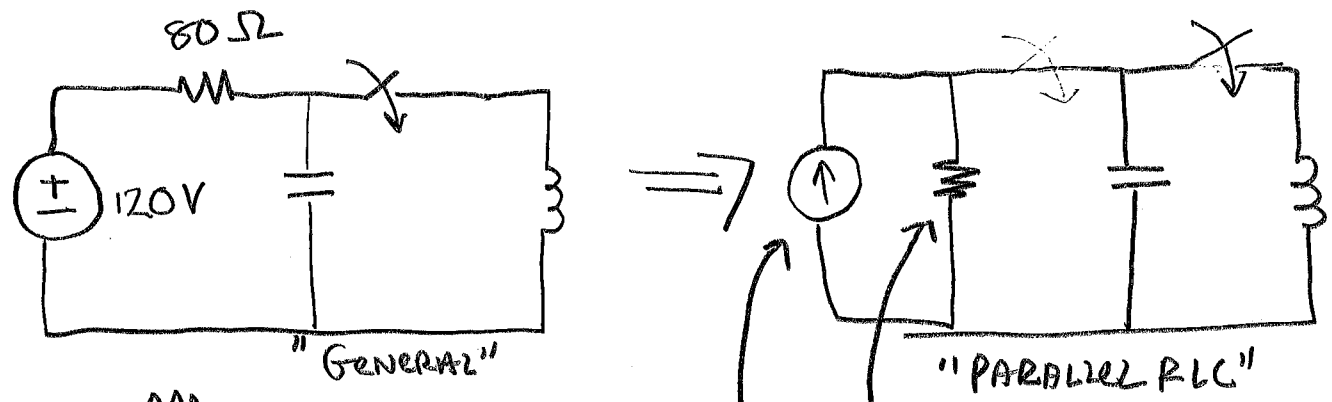

Short output, $\frac{120}{80} = 1.5A$


FOR NORTON, WE KNOW $I_N \times Z_N = V_{OC}$

SO $Z_N = \frac{V_{OC}}{I_N} = \frac{120}{1.5} = 80\Omega$

Simplified the problem.

Practice problem 10.8 Pg 428

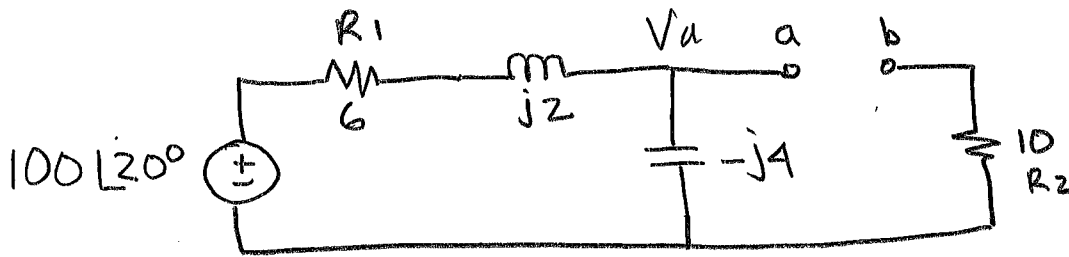Find Thevenin equivalent at terminals a-b - also NORTON




First get open circuit voltage.

No current in 10Ω resistor

so

$$V_{TH} = \frac{-j4}{6 + j2 - j4} \times 100 \angle 20^\circ = 63.24 \angle -51.56^\circ$$

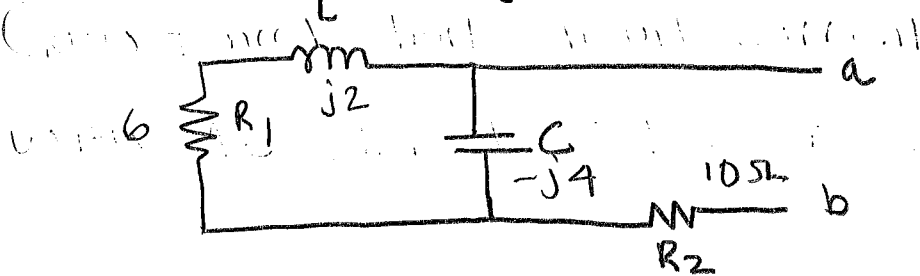
Get Z_{TH} by disabling voltage source and measuring




$$Z_{TH} = (R_1 + j2) \parallel (-j4) + R_2$$

$$= \frac{(6 + j2) \times (-j4)}{(6 + j2) - j4} + 10 = 12.4 - j3.2 \Omega$$

Thevenin EQUIV IS

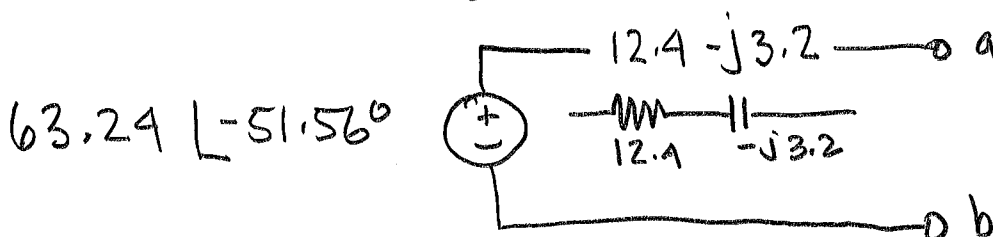

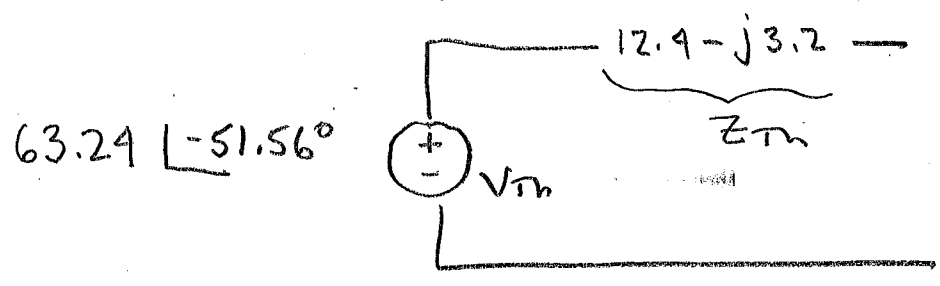


Thevenin Source

$$I_N = \frac{V_{Th}}{Z_{Th}} = \frac{63.24 \angle -51.56^\circ}{12.4 - j3.2} = \frac{39.31 - j49.53}{12.4 - j3.2}$$


$$= \underline{3.94 - j2.98 \text{ A}}$$

and $Z_N = Z_{Th} = 12.4 - j3.2$

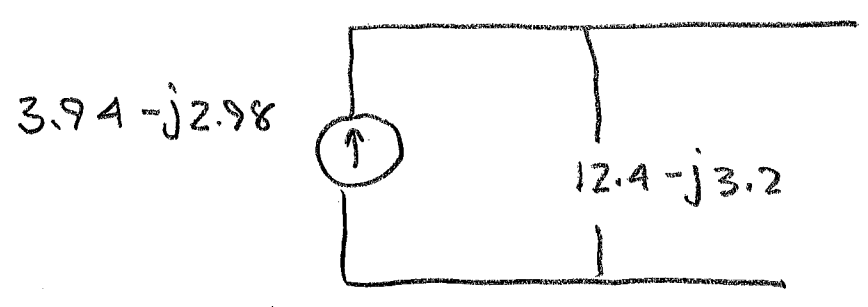

NORTON SOURCE

(Find $V_o(t)$ $i_o(t)$)

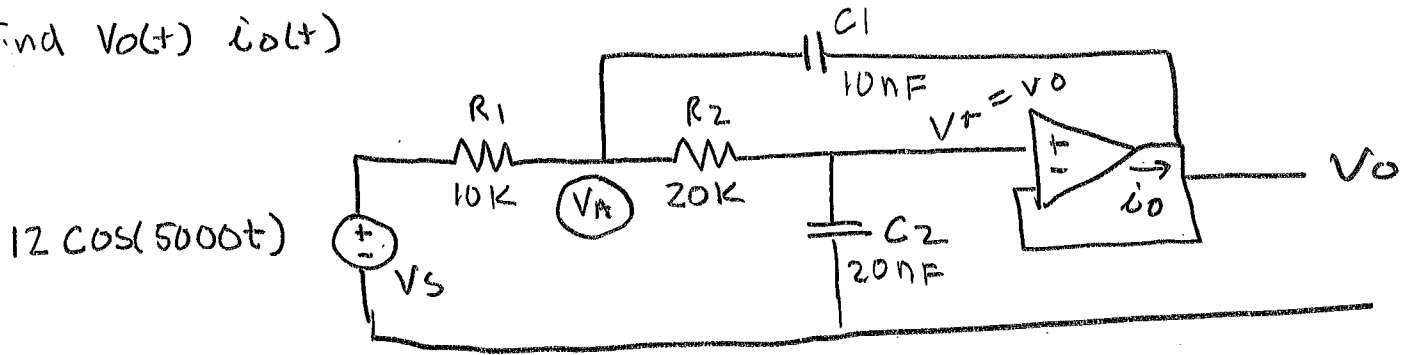

KCL @ node A

$$\textcircled{1} \quad \frac{V_s - V_A}{R_1} + \frac{V_o - V_A}{Z_{C1}} + \frac{V_o - V_A}{R_2} = 0$$

KCL at non-inv terminal

$$\textcircled{2} \quad \frac{V_o - V_A}{R_2} + \frac{V_o}{Z_{C2}} = 0$$

} UNK V_o, V_A

$$\textcircled{1} \downarrow \quad V_A \left[-\frac{1}{R_1} - \frac{1}{Z_{C1}} - \frac{1}{R_2} \right] + V_o \left[\frac{1}{Z_{C1}} + \frac{1}{R_2} \right] = -\frac{V_s}{R_1}$$

$$\textcircled{2} \quad V_A \left[-\frac{1}{R_2} \right] + V_o \left[\frac{1}{R_2} + \frac{1}{Z_{C2}} \right] = 0$$

SO

$$\begin{bmatrix} -\frac{1}{R_1} - \frac{1}{Z_{C1}} - \frac{1}{R_2} & \frac{1}{Z_{C1}} + \frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{Z_{C2}} \end{bmatrix}^{-1} \begin{bmatrix} -\frac{V_s}{R_1} \\ 0 \end{bmatrix} = \begin{bmatrix} V_A \\ V_o \end{bmatrix}$$

$$R_1 = 10K, R_2 = 20K, C_1 = 10nF, C_2 = 20nF$$


$$V_s = 12 \angle 0, Z_{C1} = \frac{1}{j\omega C_1} = \frac{1}{j \times 5000 \times 10nF} = -j20K$$

$$Z_{C2} = \frac{1}{j\omega C_2} = \frac{1}{j \cdot 5000 \times 20nF} = -j10K$$

Substituting in the matrix:

$$V_A = 8 - j4$$

$$V_o = -j4 = 4 \angle -90$$

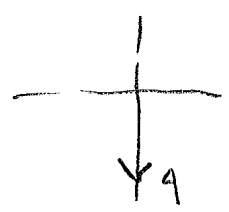

Use 9.25 (Pg 379)

$$V_o = 4 \angle -90 \iff 4 \cos(5000t - 90)$$

$$V_o = 4 \sin(5000t)$$

Now get $i_o(t)$

No current into op-amp terminal V^-

$$\text{So } I_o = \frac{V_o - V_A}{Z_{C1}} \leftarrow \text{See circuit}$$

$$= \frac{-j4 - (8 - j4)}{-j20K} = \frac{-8}{-j20K} = -j400E-6$$

$$= 400E-6 \angle -90$$



$$= 400E-6 \sin(5000t)$$

EASY OP-AMP PROBLEM

Practice Problem 10.12

find Gain and phase shift

↑ ? ↓ ?

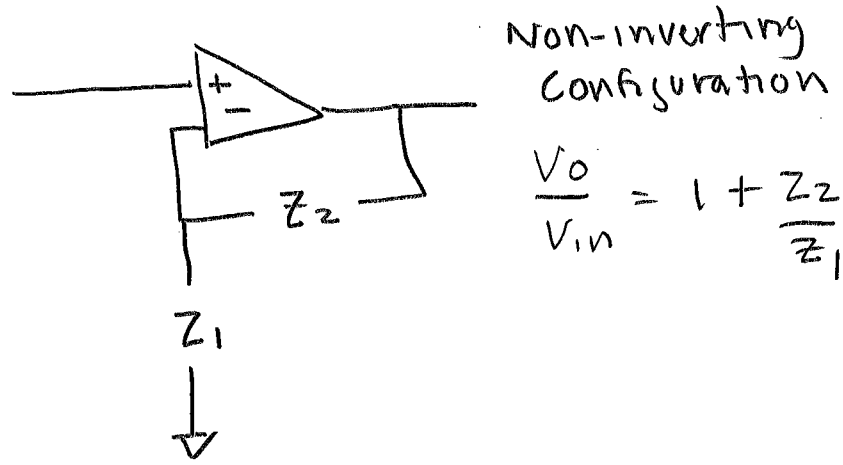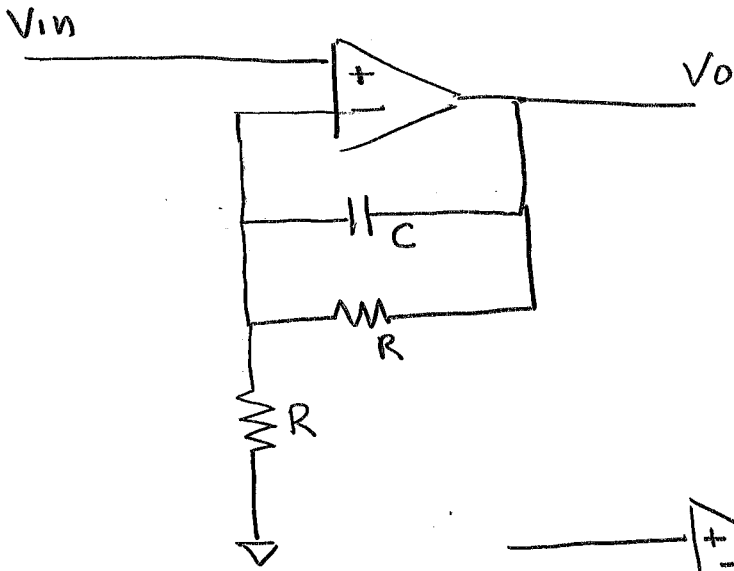

Non-inverting Configuration

$$\frac{V_o}{V_{in}} = 1 + \frac{Z_2}{Z_1}$$

$$Z_2 = Z_R \parallel Z_C$$

$$Z_2 = \frac{R \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} =$$

$$Z_2 = \frac{R}{j\omega RC + 1}$$

$$\text{So } \frac{V_o}{V_{in}} = 1 + \frac{Z_2}{Z_1} = 1 + \frac{R}{\frac{j\omega RC + 1}{R}}$$

$$= 1 + \frac{1}{j\omega RC + 1}$$



With $R = 10K$, $C = 1\mu f$ and $\omega = 1000 \text{ rad/s}$

113

$$\begin{aligned}\frac{V_o}{V_{in}} &= 1 + \frac{1}{j\omega RC + 1} = 1 + \frac{1}{j \times 1000 \times 10K \times 1\mu F + 1} \\ &= 1.0099 - j0.0990 \\ &= 1.0147 \angle -5.6^\circ\end{aligned}$$

"Gain" "Phase"

will |Gain| increase or decrease if frequency increases?

What is the Gain at DC?

What is the gain at $\omega = \omega$?